

# Homework 14

## Chapter 30

Problem 12 Inductance is  $L = \frac{\mu_0 N^2 A}{l} = \frac{\mu_0 N^2 \pi (\frac{d}{2})^2}{l}$

constant:  $\mu_0, l$

changing: diameter  $d' = 2.5d$

$N' = ?$  in general  $l_{\text{wire}} = 2\pi r N = \frac{\pi d N}{2} \Rightarrow N = \frac{l}{\pi d}$

try to get  $L$  in terms of  $d$  (change  $l_{\text{wire}}$ ) with  $\mu_0, l$  (constants)

now  $L_1 = \frac{\mu_0 N_1^2 \pi (\frac{d_1}{2})^2}{l_1}$

$$L_2 = \frac{\mu_0 N_2^2 \pi (\frac{d_2}{2})^2}{l_2}$$

$$\frac{L_2}{L_1} = \frac{\frac{\mu_0 N_2^2 \pi d_2^2}{4l_2}}{\frac{\mu_0 N_1^2 \pi d_1^2}{4l_1}} = \frac{l_1 N_2^2 d_2^2}{l_2 N_1^2 d_1^2} = \left( \frac{N_2 d_2}{N_1 d_1} \right)^2$$


now  $l_{\text{wire}} = N_1 \pi d_1 = N_2 \pi d_2$

$$\frac{N_2}{N_1} = \frac{d_1}{d_2}$$

$$\frac{L_2}{L_1} = \frac{l_1}{l_2} \left( \frac{N_2 d_2}{N_1 d_1} \right)^2$$


$$= \frac{d N_1}{\pi N_2} = \frac{d_2}{d_1} = \boxed{2.5}$$

what is  $l_1 : l_2$ ?

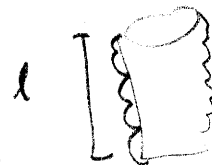


l is diameter of wire  
x # of turns!  
diameter of wire  
is constant  $D$

30-26

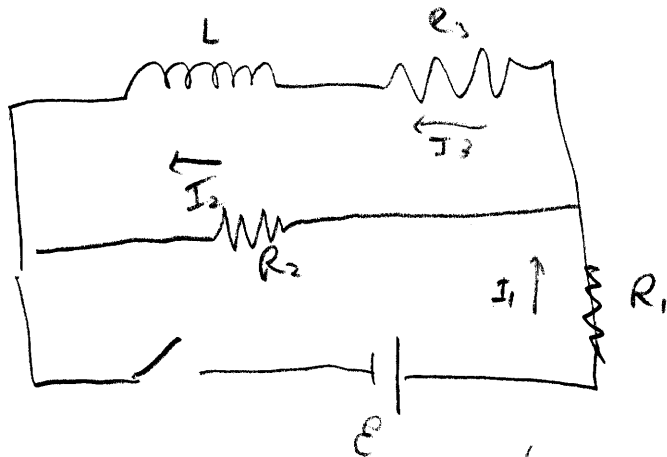

a)


Current in RL circuits :

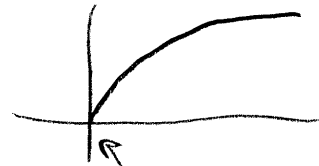

at moment switch is closed, current through L is = 0

so we essentially have:

$$\Rightarrow \boxed{I_3 = 0}$$

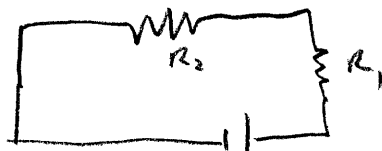


$$\leftarrow R_{eq} = R_1 + R_2$$

$$I_1 = I_2 = \frac{V}{R_{eq}} = \frac{\epsilon}{R_1 + R_2}$$

b)

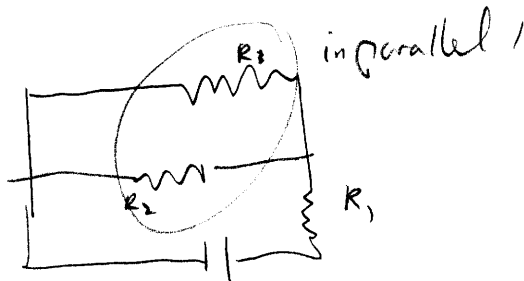the voltage drop across the inductor is  $-L \frac{dI}{dt}$   
 After a long time this rate slows to zero, so the effect of L on the voltage is that it is, after all purposes, not even there.



Junction :  $I_1 = I_2 + I_3$  (1)

Loops  $\epsilon - I_1 R_1 - I_3 R_3 = 0$  (2)

$I_2 R_2 - I_3 R_3 = 0$  (3)

3 eq, 3 unknowns

$$\textcircled{3} \quad \begin{aligned} I_2 R_2 &= I_3 R_3 \\ I_2 &= I_3 \frac{R_3}{R_2} \end{aligned} \rightarrow \text{in (1)} \quad I_1 = I_2 \left( \frac{R_3}{R_2} + 1 \right) = I_3 \left( \frac{R_3 + R_2}{R_2} \right)$$

set equal

$$\textcircled{2} : I_1 = \frac{\epsilon - I_3 R_3}{R_1} = \frac{\epsilon - I_3 R_3}{R_1} = I_3 \left( \frac{R_3 + R_2}{R_2} \right)$$

$$\frac{\mathcal{E}}{R_1} = I_3 \left( \frac{R_3}{R_1} + \frac{R_3}{R_2} + 1 \right)$$

$$I_3 = \frac{\mathcal{E}}{R_1} \left( \frac{1}{\frac{R_3}{R_1} + \frac{R_3}{R_2} + 1} \right)$$

$$I_1 = I_3 \left( \frac{R_3 + R_2}{R_2} \right)$$

$$I_2 = I_1 - I_3$$

30-31  $C = 1350 \times 10^{-12} \text{ F}$

$f = 550 \times 10^3 \text{ Hz}$

w) if  $C = 1600 \times 10^{-12} \text{ Hz}$ ,  $L = ?$

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

assume  $L$  the same

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\frac{f_1}{f_2} = \frac{\sqrt{\frac{1}{LC_1}}}{\sqrt{\frac{1}{LC_2}}} = \sqrt{\frac{C_2}{C_1}}$$

$$\frac{f_1^2}{f_2^2} = \frac{C_2}{C_1} \Rightarrow C_2 = C_1 \frac{f_1^2}{f_2^2} = (1350 \times 10^{-12} \text{ F}) \left( \frac{550}{1600} \right)^2 = 0.16 \text{ nF}$$

30-57  $L = 25 \text{ mH}$   $R = 0.8 \Omega$   $C = ?$

$f = 360 \text{ Hz}$   
 $V = 45 \text{ V}$

phase is  $\phi$

$$\tan \phi = \frac{X_L - X_C}{R}$$


for  $\phi = 0$ ,  $X_L = X_C$

$$X_L = \omega L = 2\pi f L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$2\pi f L = \frac{1}{2\pi f C}$$
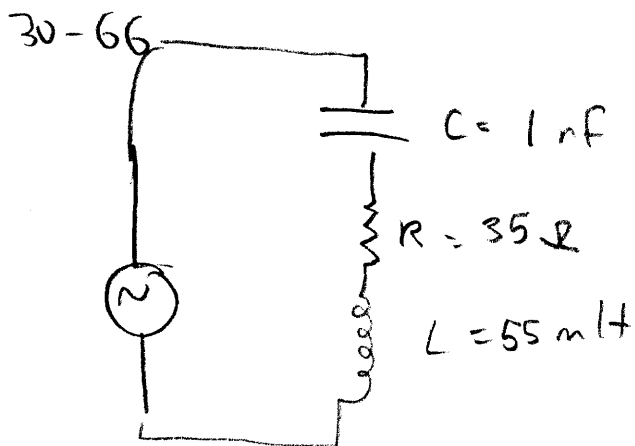
$$C = \frac{1}{4\pi^2 f^2 L} = 7.8 \mu\text{F}$$



$$V = V_0 \sin(2\pi f_0 t + \phi)$$

a) resonant frequency  $\omega_0 = \sqrt{\frac{1}{LC}}$

occurs when <sup>avg</sup> current is a max (see 30-9)

$$\omega = 2\pi f_0$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(55\text{mH})(1\text{nF})}} = 21 \text{ kHz}$$

b)  $V_0 = 2 \text{ V}$  @  $f = f_0$   $V_{C0} = ?$

$$V_C = I_0 X_C \quad I_0 = \frac{V_0}{R} \quad X_C = \frac{1}{\omega C} = \frac{1}{2\pi f_0 C}$$

$$V_{C0} = \frac{V_0 L}{R 2\pi f_0 C} = \frac{(2 \text{ V})}{(35 \Omega) 2\pi (21 \text{ kHz}) (1 \text{ nF})} = 420 \text{ V}$$

c)  $\frac{V_{C0}}{V_0} = \frac{420 \text{ V}}{2.0 \text{ V}} = 210$