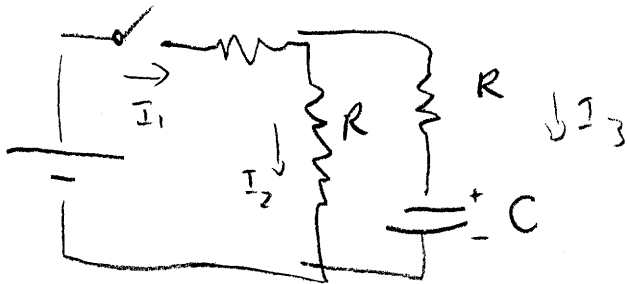


HW 8


26-31

use Kirchoff's rules, + follow strategy. See solutions manual.


26-49



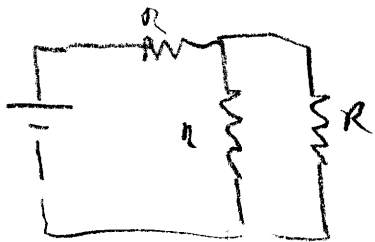
a) simpler circuit: at $t=0$, the capacitor is uncharged and is just like a wire:



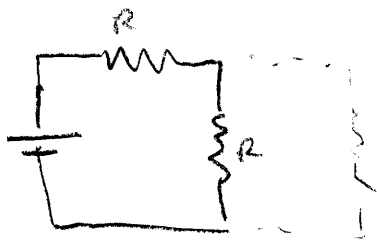b) at $t=\infty$ the capacitor is charged and no current flows through it



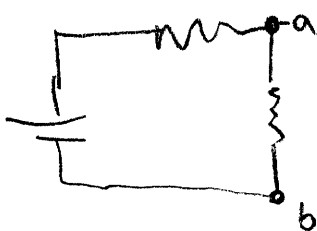c) at $t=\infty$, the potential difference is the same as that between points a and b shown below:



potential
(no drop from resistor when $I=0$)

22-8 The flux is equal to $\frac{Q_{enc}}{\epsilon_0}$
Q enc is the same for both closed surfaces
 ϵ_0 is a constant

\Rightarrow the ratio is 1:1