

Electric Currents + Resistance - Ch 25


We are moving from static \rightarrow dynamic charges in motion!

E field exerts force on electrons to make them move.

E related to V $V = \int \vec{E} \cdot d\vec{l}$ etc



so potential difference needed to make charges move in a wire.

first battery:

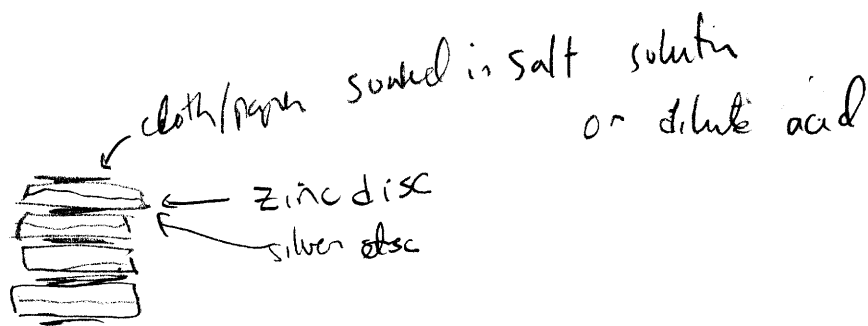


Batteries have + and - terminals

pot'l diff comes from chemical reaction

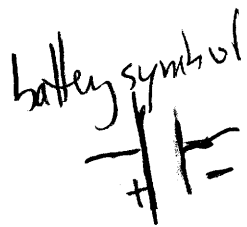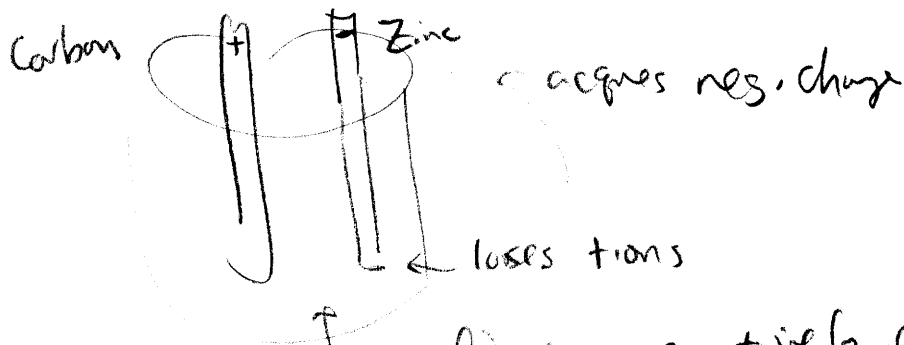

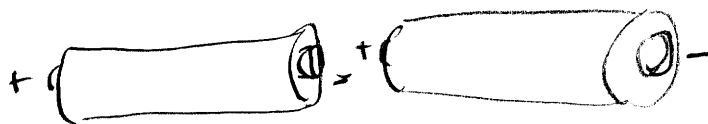↑ solution becomes +vely charged, so carbon loses electrons



voltages add up when multiple batteries used

"in series"

Current - flow of charge



← water flows downhill and does work

↑ mill

Why does water move? Potential difference.

Similarly, charges move because battery or some source creates a potential difference

average $\bar{I} = \frac{\Delta Q}{\Delta t}$

how much charge passing through a region given amt of time


$$I = \frac{dQ}{dt}$$

coloumbs / second = Ampere "Amp" A

$$1A = 1C/s$$

note

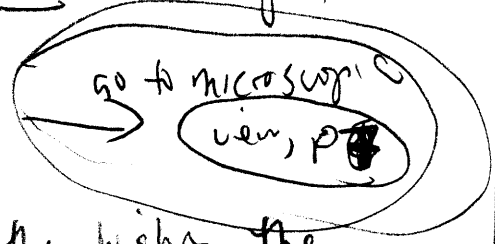charge only flows if circuit is complete. In open circuits, the charge doesn't move.



Ohms Law

$$I \propto V$$

$$I \propto \frac{1}{R}$$

thick mill - the higher the water starts out, the faster it flows. But leaves or friction would also slow down the water

Put together: $I = \frac{V}{R}$

$V = IR$ "Ohms Law"

← actually not, but is what everyone uses

↑ resistance

depends on material

unit of resistance: Ohm Ω (omega)

$$1 \Omega = \frac{1V}{A}$$

example flashlight bulb.

A flashlight draws 300 mA from its 1.5V battery.
What is the resistance of the filament?


$$R = \frac{V}{I} = \frac{1.5V}{0.3A} = 5.0 \Omega$$

what if the battery is weak and is 1.2V? $I = ?$


$$I = \frac{V}{R} = 1.2$$

Resistors in the lab: color coded.

color	#	Multiph	tolerance
black	0	1	
brown	1	10^1	1%
red	2	10^2	2%
orange	3	10^3	
yellow	4	10^4	
green	5	10^5	
Gold		10^{-1}	5%
Silver		10^{-2}	10%
no color			20%

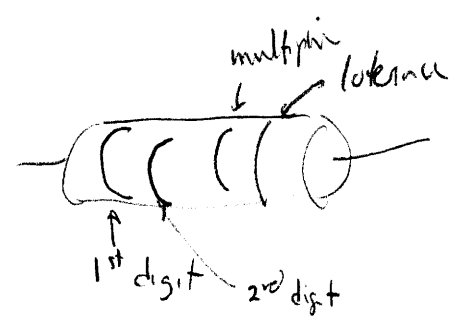

Microscopic View

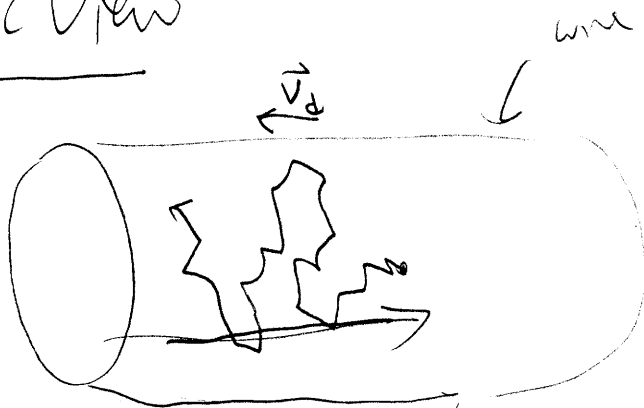


electrons move randomly. when E is "turned on" they begin to accelerate, but they collide with other atoms, etc, and reach velocity \vec{v}_d

define $\vec{j} = \frac{\vec{I}}{A}$ or $I = jA$

\uparrow
current density if j not uniform, $I = \int \vec{j} \cdot d\vec{A}$

what is I ? $I = \frac{\Delta Q}{\Delta t}$

consider small volume

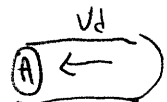

$\Delta Q = v_d \Delta t$

Q passing through this small volume

in time Δt is (number per unit volume) \times (Volume) \times (Charge per particle)

$$\begin{aligned} \Delta Q &= n e A v_d \Delta t \\ &= n e A v_d \Delta t \\ &= n e A v_d \Delta t \end{aligned}$$

$$\therefore \frac{\Delta Q}{\Delta t} = n(-e) A v_d = I$$

$$\vec{j} = \frac{I}{A} = -n e \vec{v}_d$$

~~$I = jA$~~


\leftarrow go back ...

eg: red, green, yellow, silver

resistance of $25 \times 10^4 \Omega \pm 10\%$

Resistivity

for a wire

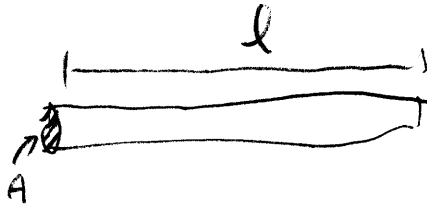

$$R = \rho \frac{l}{A} \quad \rho \text{ is resistivity } (\Omega \cdot \text{m})$$

also conductivity $\sigma = \frac{1}{\rho}$ ($\frac{1}{\Omega \cdot \text{m}}$)

example: stretch a wire, keeping volume constant
say stretch so that $l' = 2l$

$$V = lA$$

$$A = \frac{V}{l} \Rightarrow A' = \frac{V}{l'} = \frac{V}{2l} = \frac{1}{2} A$$

$$R' = \rho \frac{l'}{A'} = \rho \frac{2l}{\frac{1}{2}A} = \boxed{4R}$$

In addition, resistance depends on temperature

Atoms move more at higher temp, and interfere more with "flow of e^- "

$$\rho_T = \rho_0 [1 + \alpha(T - T_0)]$$

ρ_0 is resistivity at T_0 (eg 20°C or 0°C)

α depends on the material, ~~called~~
called the temperature coefficient

→ go to the true Ohm's law


so $\bar{P} = I_{rms}^2 R$

$\bar{P} = \frac{V_{rms}^2}{R}$

I_{rms}, V_{rms} "effective values"

so $\bar{P} = I_{rms} V_{rms}$

Microscopic View

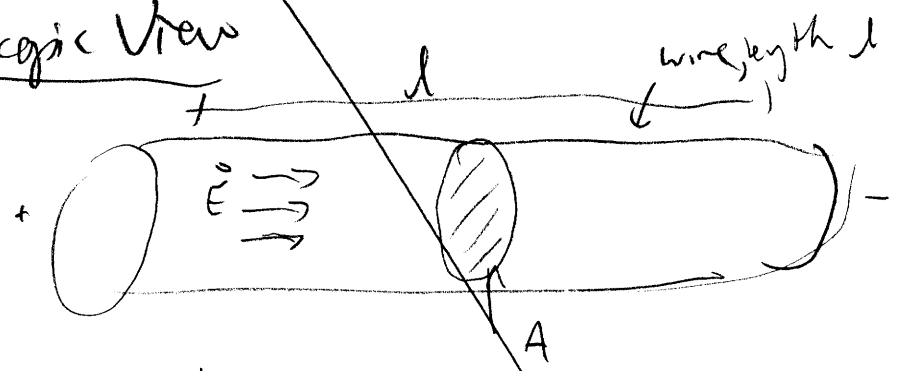

Current density $\vec{j} = \sigma \vec{E}$ = electric current per unit cross-sectional area

σ is the conductivity

$j = \frac{I}{A}$ has units of $\frac{Amp}{m^2}$

$I = jA = (\sigma E)A$
 $jA = \sigma E A$

$j = \sigma E$ This is Ohm's Law \rightarrow Go to Ohm's Law

how is this the same as $V=IR$? (in a wire)

$V = El$ $j = I/A$, so $I = jA$ $R = \rho \frac{l}{A}$

Sub in

$El = (jA) \left(\rho \frac{l}{A} \right)$

$El = j \rho l$

$\frac{E}{\rho} = j$ but $\frac{1}{\rho} = \sigma$

$E\sigma = j$

Electric Power:

how do we use electricity? one way: convert electric energy to thermal energy

$$dU = V dq$$

$$P = \frac{dU}{dt} = V \frac{dq}{dt} + \cancel{q \frac{dV}{dt}} \rightarrow 0$$

$$= VI$$

applies to all devices \rightarrow
 applies to resistors

$$\boxed{P = IV}$$

but $V = IR$, so

$$\boxed{P = I^2 R} \quad \rightarrow I = \frac{V}{R}$$

$$\boxed{R = \frac{V^2}{P}}$$

* hint - be careful which equation you use. eg if V is changing, you can't use $P = I^2 R$

Unit of power? $J/s = \text{watt}$

$$\boxed{1W = 1 J/s}$$

Example: Extension cord: Your 1800-W electric heater is too far away, so you use an extension cord rated at 11A. Is this dangerous?

Outlet: 120 V max 1800 W


$$P = IV$$

$$I = \frac{P}{V} = \frac{1800}{120} = 15A$$

4 'extra' A, could melt insulation of wire!


AC - Alternating Current:

up till now:

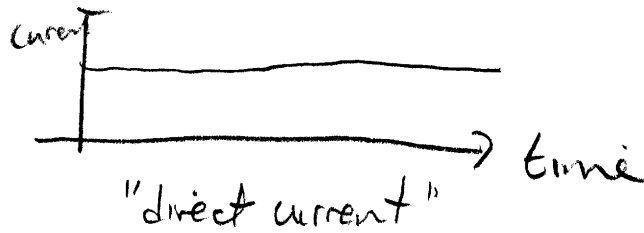

eg battery

now consider:

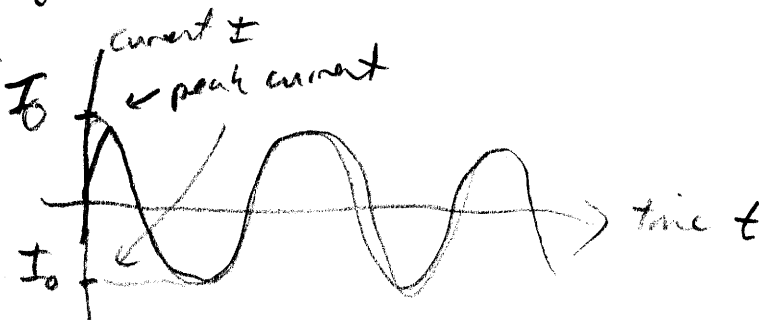


$$V = I = I_0 \sin \omega t \quad (\omega = 2\pi f)$$

$$V = IR = I_0 R \sin \omega t = V_0 \sin \omega t$$

what is the average current? zero
 does this mean no power?

$$P = I^2 R = I_0^2 R \sin^2 \omega t$$

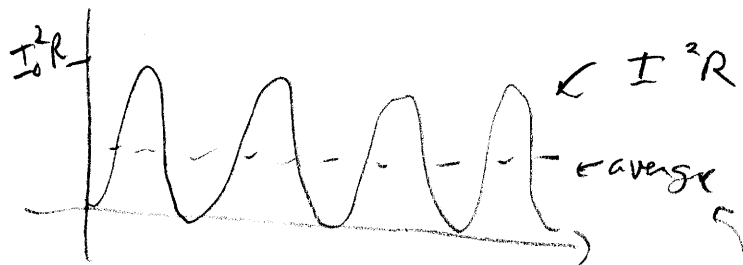\uparrow \uparrow
 I is squared, so always positive



so average power $\bar{P} = \overline{I^2 R} = \frac{1}{2} I_0^2 R$

useful quantities

$$I_{rms} = \sqrt{\overline{I^2}} = \frac{I_0}{\sqrt{2}} \text{ root of the mean of the square}$$

$$V_{rms} = \sqrt{\overline{V^2}} = \frac{V_0}{\sqrt{2}}$$

$$\begin{aligned}
 \text{So that } \bar{P} &= I_{\text{rms}} V_{\text{rms}} \\
 &= \frac{1}{2} I_0^2 R = I_{\text{rms}}^2 R \\
 &= \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{\text{rms}}^2}{R}
 \end{aligned}$$

switch order
for clarity

Problem: Calculate the peak current in a $2.7 \text{ k}\Omega$ resistor connected to a 220-V rms ac source

find I_0 given R, V_{rms}

$$\frac{1}{2} I_0^2 R = \frac{V_{\text{rms}}^2}{R}$$

$$I_0^2 = 2 \frac{V_{\text{rms}}^2}{R^2}$$

$$I_0 = \frac{\sqrt{2} (220 \text{ V})}{\sqrt{2.7 \text{ k}\Omega^2}}$$

~~$$V = IR$$~~

~~$$V = I^2 R^2$$~~

~~$$V_{\text{rms}} = I_{\text{rms}} R_{\text{rms}}$$~~