
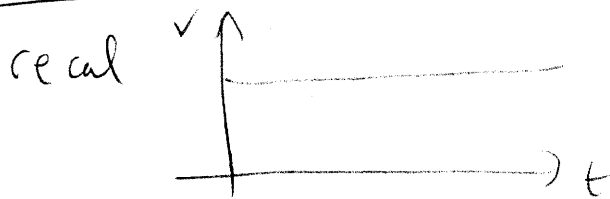


Ch 26 - DC Circuits

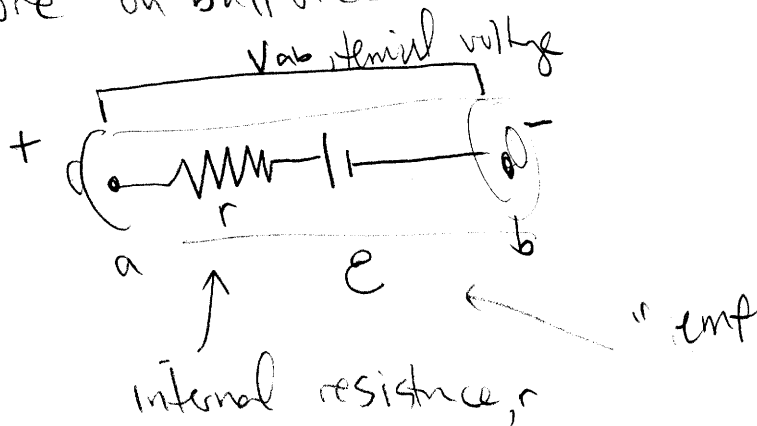

DC or AC?

More on batteries' internal resistance:



- batteries maintain a potential difference
- batteries do not necessarily need a fixed current

resistance causes a voltage drop:

$$V = IR \text{ (Ohm's law)}$$


$$\text{So } V_{ab} = \mathcal{E} - Ir$$

↑ what the battery is rated at

emf: units of volts (it's a pot'l diff)

stands for electromotive force discuss

example (26-1) A 65.0Ω resistor...

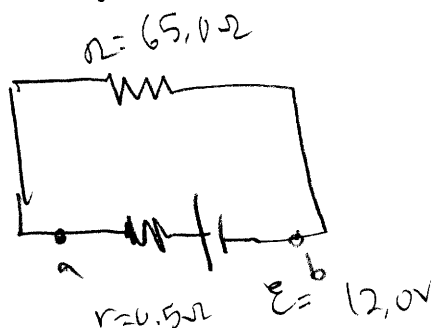

Find a) current in the circuit

b) terminal voltage

c) power dissipated in R and r

$$V = IR$$

$$I = \frac{V}{R} \quad V = V_{ab} = \mathcal{E} - Ir$$

$$I = \frac{\mathcal{E} - Ir}{R}$$

$$IR = \mathcal{E} - Ir$$

$$I(R+r) = \mathcal{E}$$

$$I = \frac{\mathcal{E}}{R+r} = 0.183 \text{ A}$$


b) $V_{ab} = \mathcal{E} - Ir = 11.9 \text{ V}$

c) $P_R = I^2 R = 2.18 \text{ W}$

$$P_r = I^2 r = 0.02 \text{ W}$$

$$\begin{aligned}
 IR &= \mathcal{E} - Ir \\
 I(R+r) &= \mathcal{E} \\
 I &= \frac{\mathcal{E}}{R+r}
 \end{aligned}$$

Resistors in series + parallel:

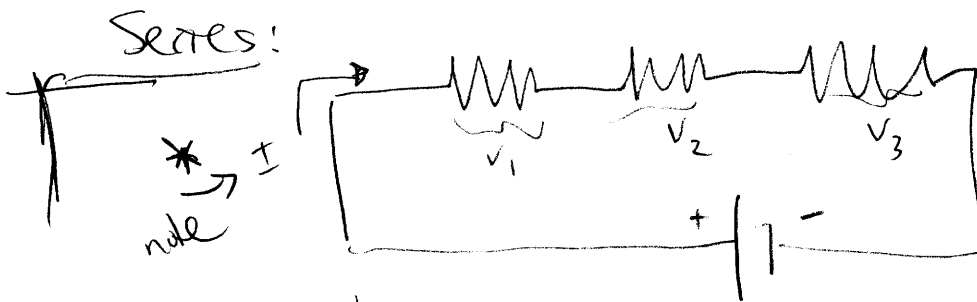

resistance causes a drop in potential $V = IR$

$$V = V_1 + V_2 + V_3$$

$$= IR_1 + IR_2 + IR_3$$


$$= I(R_1 + R_2 + R_3)$$

$$= I R_{eq}$$

$$R_{eq} = R_1 + R_2 + R_3$$

* I the same - otherwise current would "pile up"
think water pipe

In Parallel:

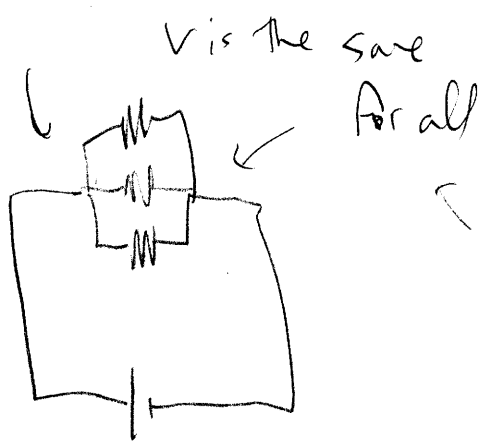

think pipes
fan dam,
slow it back

because charge is

conserved, $I = I_1 + I_2 + I_3$

but $I = \frac{V}{R}$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

parallel resistors

one final tool needed to analyze circuits:

→ Kirchhoff's Rules ←

↳ application of charge + energy conservation

Junction rule: at any pt, the sum of all currents entering a junction must equal the sum of all currents leaving

" $I_{in} = I_{out}$ "


Loop rule: the sum of changes in potential energy around any closed loop must be zero

" what goes up must come down "

practice:




discuss:

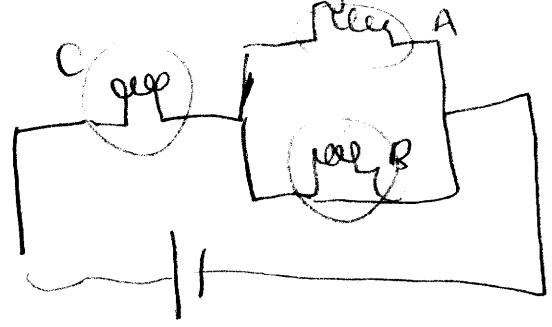

which is brightest? 2nd brightest?

what if I disconnect S?

given

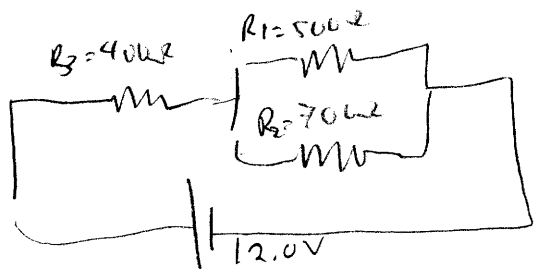

find current through the 500Ω resistor

* give
from time
to solve!

solution:

$$V_1 = I R_1$$

$$V_1 = 12.0V - V_3 \quad (-V_{ab} + V_3 - V_1 = 0)$$

$$V_3 = I R_3 \quad I = ?$$

$$V = I R_{eq}$$

$$R_{eq} = R_3 + R_{12} = \frac{1}{R_3} + \frac{1}{R_{12}} = \frac{1}{R_3} + \frac{1}{R_1 + R_2} = \frac{R_1 + R_2 + R_3}{R_1 R_2}$$

$$I = \frac{V}{R_{eq}} = \frac{1}{12.0V} \left(R_3 + \frac{R_1 R_2}{R_1 + R_2} \right)$$

$$V_3 = \frac{1}{12.0V} \left(R_3 + \frac{R_1 R_2}{R_1 + R_2} \right) R_3 = 7.0V$$

$$V_1 = 12.0V - 7.0V = 5.0V$$


$$I_1 = \frac{V_1}{R_1} = \frac{5.0V}{500\Omega} = 1.0 \times 10^{-2} A = 10mA$$

Strategy for complex circuits:


1. Label the currents
2. Identify unknowns (+ num # of eqns)
3. Apply junch rule
4. Apply loop rule
5. Do algebra

} see ex 26-9

Practice:

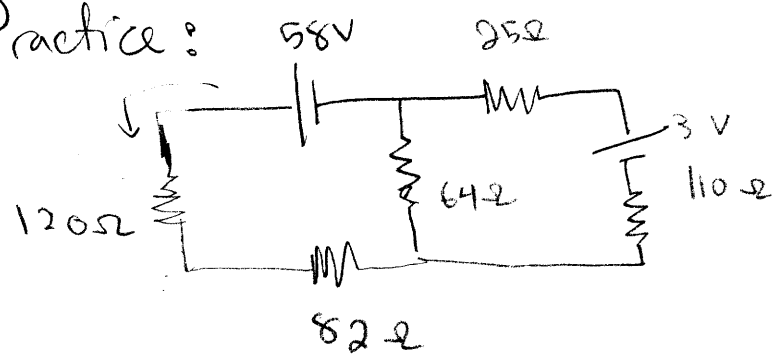

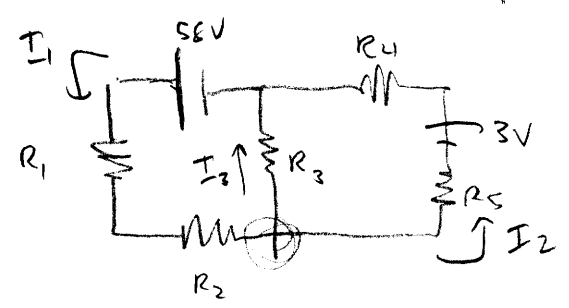find the current through the middle resistor



find I_1, I_2, I_3
(unknowns)

junch rule: $I_2 = I_1 - I_3$
 $I_1 = I_2 + I_3$

} 3 eqns, 3 unknowns

① loop rule: left loop: $58V - I_1 R_1 - I_2 R_2 - I_3 R_3 = 0$

② right loop: $3V - I_2 R_4 + I_3 R_3 - I_2 R_5 = 0$

① $58V - (I_2 + I_3)(R_1 + R_2) - I_3 R_3 = 0 \rightarrow 58V - I_2(R_1 + R_2) - I_3(R_1 + R_2 + R_3) = 0$

② $3V - I_2(R_4 + R_5) + I_3 R_3 = 0$

from ① $I_2 = \frac{58V - I_3(R_1 + R_2 + R_3)}{(R_1 + R_2)}$


$$I_2 = \frac{3V + I_3 R_2}{R_4 + R_5}$$

$$\frac{58V - I_3(R_1 + R_2 + R_3)}{(R_1 + R_2)} = \frac{3V + I_3 R_2}{(R_4 + R_5)}$$

$$[58V - I_3(R_1 + R_2 + R_3)](R_4 + R_5) = (3V + I_3 R_2)(R_1 + R_2)$$

$$I_3 = \dots$$

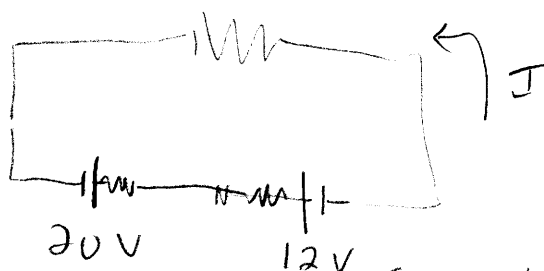Q How does a battery charger work? (discuss)



← charged ✓


RC Circuits

↑ resistor ↑ capacitor

used in - windshield wiper
- traffic lights
camera flashes
pacemakers
etc

Voltage + charge on cap. change w/ time

Consider a RC circuit:

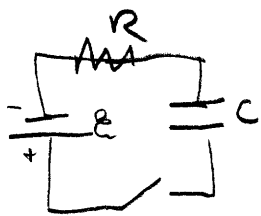

close switch at $t=0$

$$\text{loop rule } \mathcal{E} - IR - \frac{Q}{C} = 0$$

$$\mathcal{E} = IR + \frac{Q}{C}$$

R, C constants
 I, Q changing

$$\mathcal{E} = \frac{dQ}{dt} R + \frac{Q}{C}$$

rearrange

$$\mathcal{E}C = \frac{dQ}{dt}RC + Q$$

$$\mathcal{E}C - Q = \frac{dQ}{dt}RC$$

$$\frac{dt}{RC} = \frac{dQ}{\mathcal{E}C - Q}$$

integrate

$$\frac{1}{RC} \int_0^t dt = \int_0^Q \frac{dQ}{\mathcal{E}C - Q}$$

$$\begin{aligned} \frac{t}{RC} &= \ln(\mathcal{E}C - Q)(-1) \Big|_0^Q \\ &= -\ln(\mathcal{E}C - Q) - (-\ln \mathcal{E}C) \end{aligned}$$

$$-\frac{t}{RC} = \ln\left(\frac{\mathcal{E}C - Q}{\mathcal{E}C}\right)$$

$$-\frac{t}{RC} = \ln\left(1 - \frac{Q}{\mathcal{E}C}\right)$$

raise both sides

$$e^{-t/RC} = 1 - \frac{Q}{\mathcal{E}C}$$

$$Q = \mathcal{E}C(1 - e^{-t/RC})$$


$$V_C = \frac{Q}{C} = \mathcal{E}(1 - e^{-t/RC})$$

capacitor charging up

define $\tau = RC$ time to reach $1 - e^{-1} = 0.63$ or 63% of its full charge and voltage

$$\text{units: } RC = \Omega \cdot F = \left(\frac{V}{A}\right)\left(\frac{Q}{V}\right) = \frac{C}{C/s} = s$$

now consider discharge:

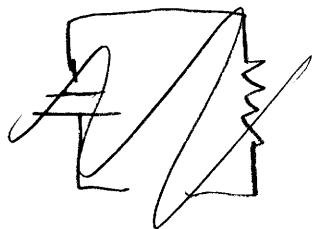

no battery

$$Q/C - IR = 0$$

$$IR = \frac{Q}{C} = 0$$

rate is negative
become α

$$\rightarrow -\frac{dQ}{dt} R = \frac{Q}{C}$$

$$\frac{dQ}{Q} = -\frac{dt}{RC}$$

$$\int_{Q_0}^Q \frac{dQ}{Q} = - \int_0^t \frac{dt}{RC}$$


$$\ln\left(\frac{Q}{Q_0}\right) = -\frac{t}{RC}$$

$$\frac{Q}{Q_0} = e^{-t/RC}$$

$$Q = Q_0 e^{-t/RC}$$

$$V_c = V_0 e^{-t/RC}$$
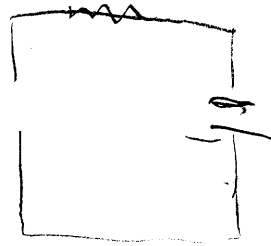
$$I = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} = I_0 e^{-t/RC}$$



* loss of charge in cap =
neg of current through
resistor

$$I = -\frac{dQ}{dt}$$