

Physics 114 - February 24, 2015


- IF you've not yet picked up your exam
they are here ---- ↓

Last
Time

$$dW = v' dq'$$

$$dW = \frac{q'}{C} dq'$$
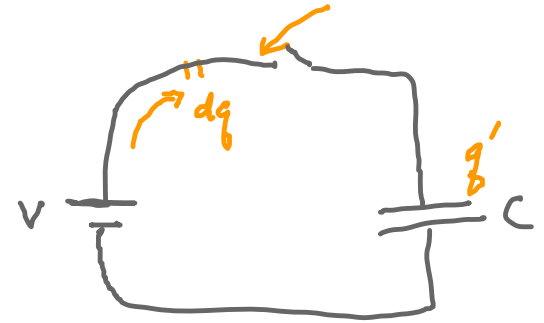
$$W = \int dW = \int_0^Q \frac{1}{C} q' dq' = \frac{1}{2C} Q^2$$




$$\text{Energy required to charge capacitor} = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{QV}{2}$$

(Stored)

$$U_E = \frac{\epsilon_0}{2} E^2$$

Energy density
in electric field

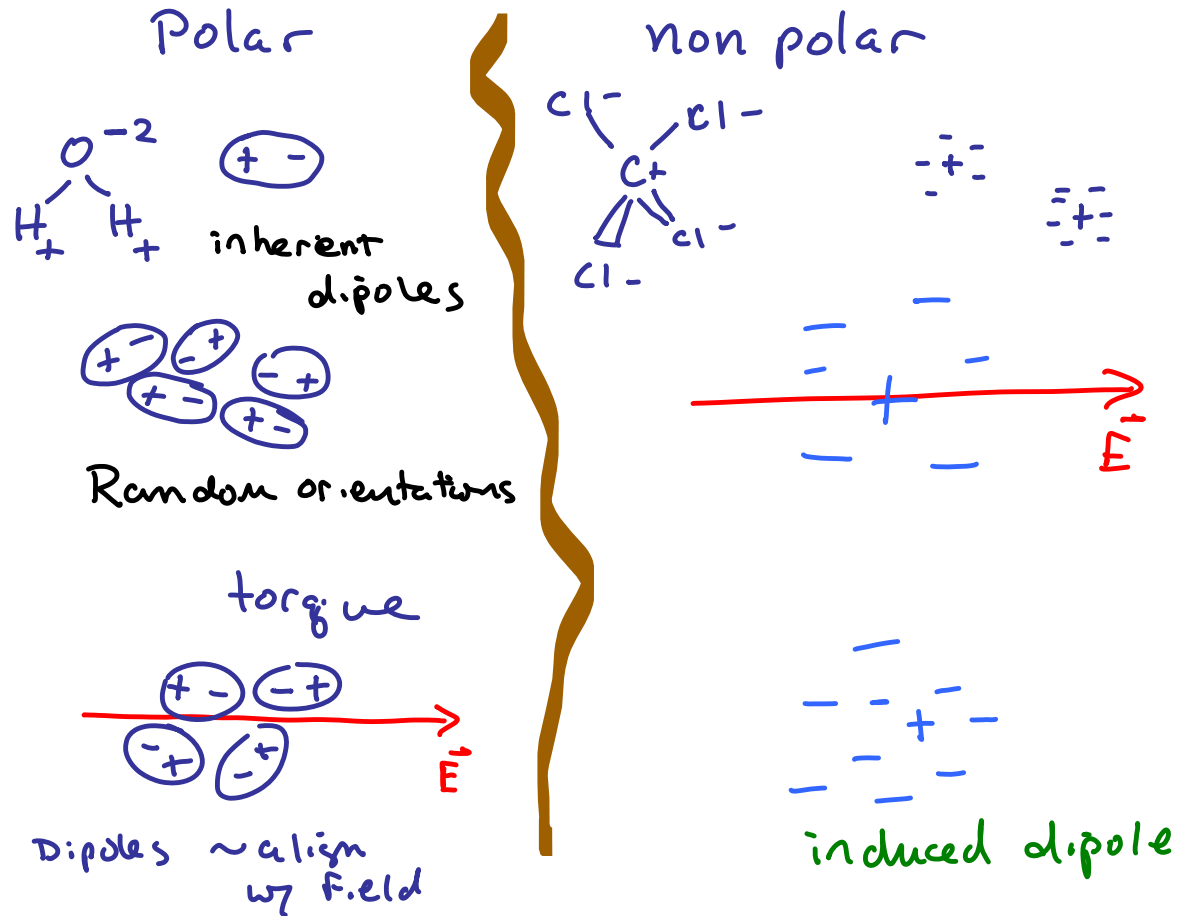\vec{E} in materials - "dielectric" (nonconductor)



Linear Dielectric

$$\vec{E} \propto \vec{E}_0$$

$$\vec{E} = \frac{\vec{E}_0}{K}$$

$K \equiv$ Dielectric constant


$$K > 1$$

$$K_{\text{water}} = 80.4$$

$$K_{\text{vacuum}} = 1$$

$$K_{\text{air}} = 1.00054$$

$$K_{\text{oil}} = 4.5$$

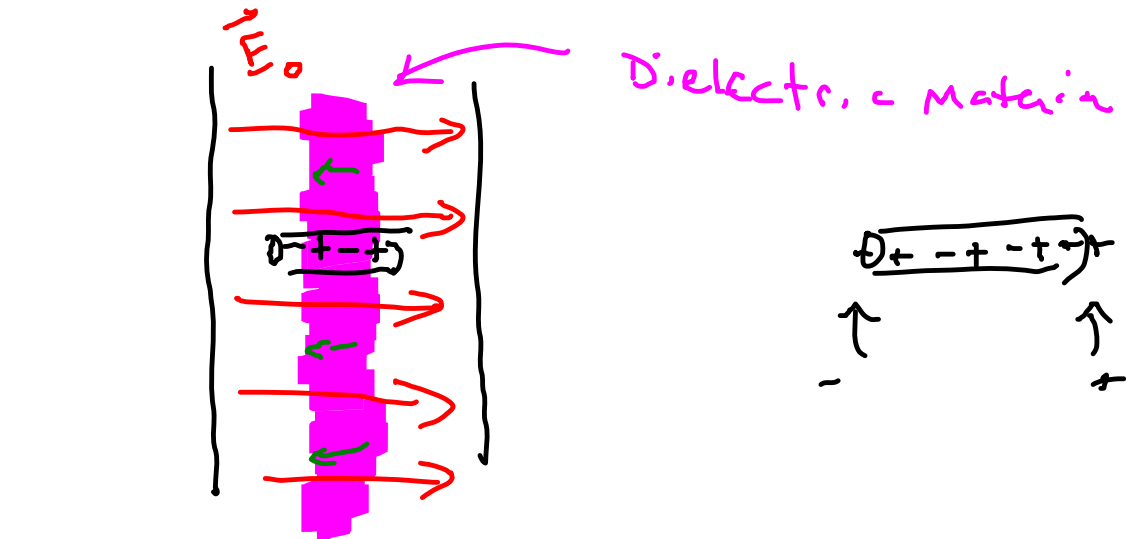

$\leftarrow = E$ from induced dipole charge sep inside dielectric

$\vec{E}_0 \rightarrow \vec{E}$ which is weaker than \vec{E}_0


$$k \epsilon_0 \equiv \epsilon$$

↑ Permittivity of free space ↑ Permittivity



$$\mathbf{E}_0 = \frac{\sigma}{\epsilon_0}$$
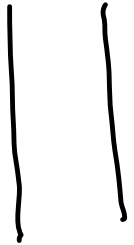
$$\mathbf{E} = \frac{\mathbf{E}_0}{k} = \frac{\sigma}{k \epsilon_0} = \frac{\sigma}{\epsilon}$$



$$Q = CV$$

NO Dielectric



Have dielectric


$$\frac{V}{K}$$

$$C \rightarrow C' = KC = K \frac{\epsilon_0 A}{d} = \frac{\epsilon A}{d}$$

$$Q = C' \frac{V}{K}$$

$$C \left(\frac{Q}{V} \right) = \frac{C'}{K}$$

i is direction of charge flow

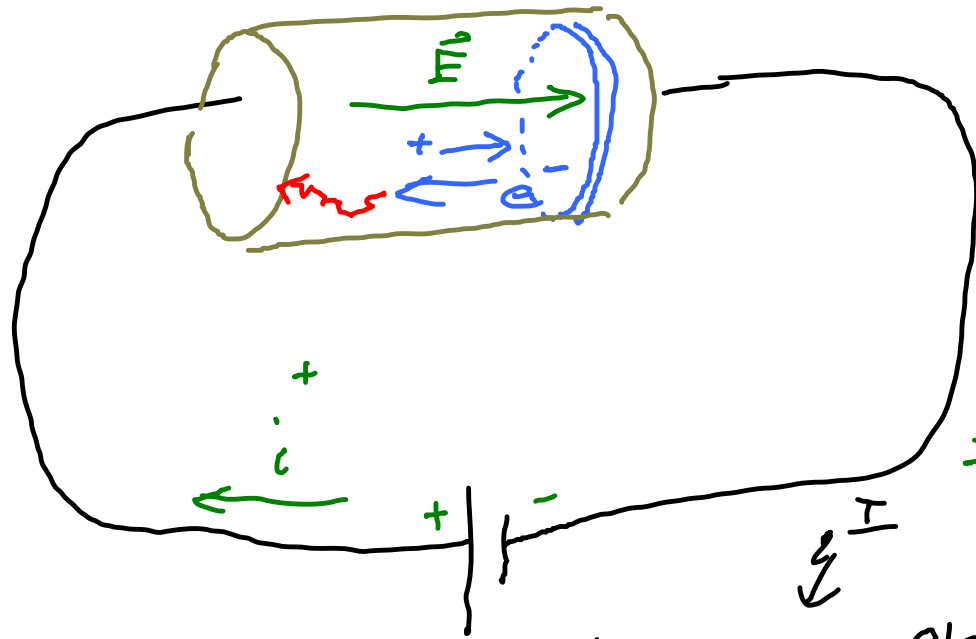

Resistance to movement of the electrons



charges will flow = $\frac{dq}{dt} = i \equiv$ electric current

units of $\frac{\text{Coulombs}}{\text{Second}} \equiv$ Amperes



André Marie Ampère
(1775 - 1836)

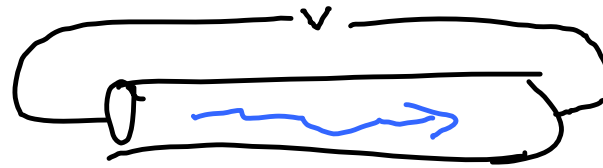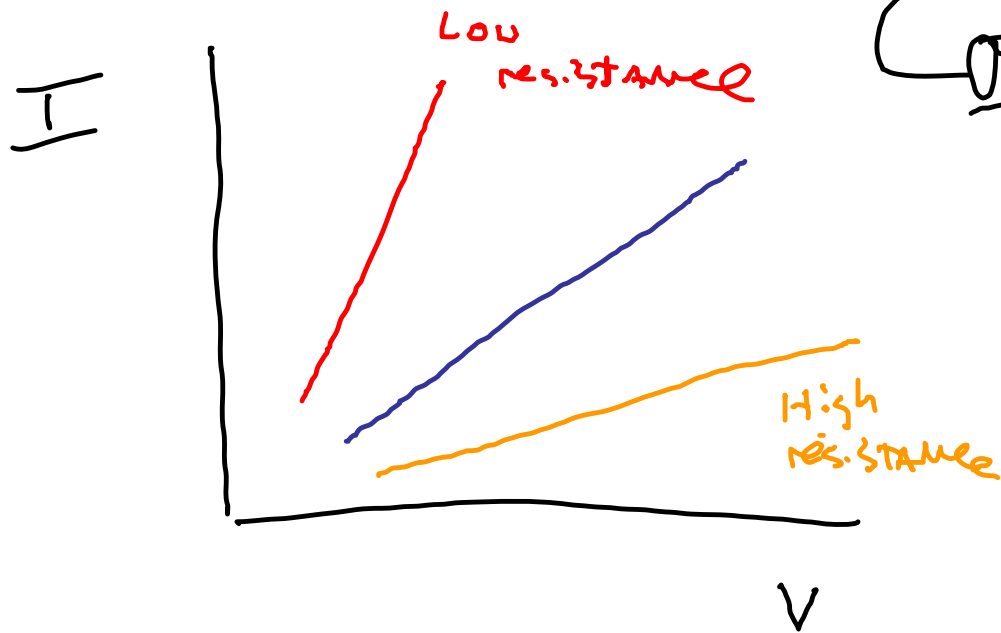French { mathematician
 { chemist
 { physicist



$$V \propto I$$

$$V = RI$$

↑
resistance

$$R = \text{ohm} = \Omega$$

$$V = IR$$

ohm's Law

RESISTANCE
Measured
in
Ohms

$$1 \text{ ohm} = 1 \frac{\text{volt}}{\text{Ampere}}$$

Ω

Georg
Ohm




1789-1854

German

$$V = iR$$

$$V = \frac{W}{q}$$

$$W = qV$$

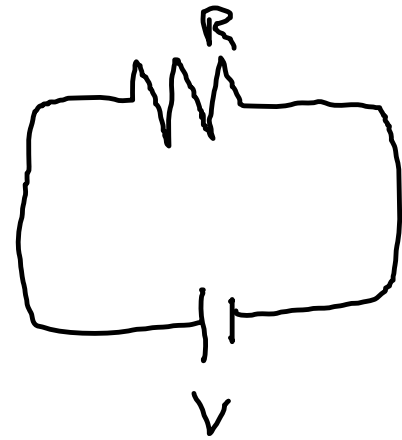

$$P = \frac{dW}{dt} = \frac{dq}{dt} V = iV$$

↑
Power


current

rate at which work is done to send i thru resistor

Power spent in resistor \rightarrow heat
and or light

$$P = iV = i^2 R = \frac{V^2}{R}$$

$$V = iR$$

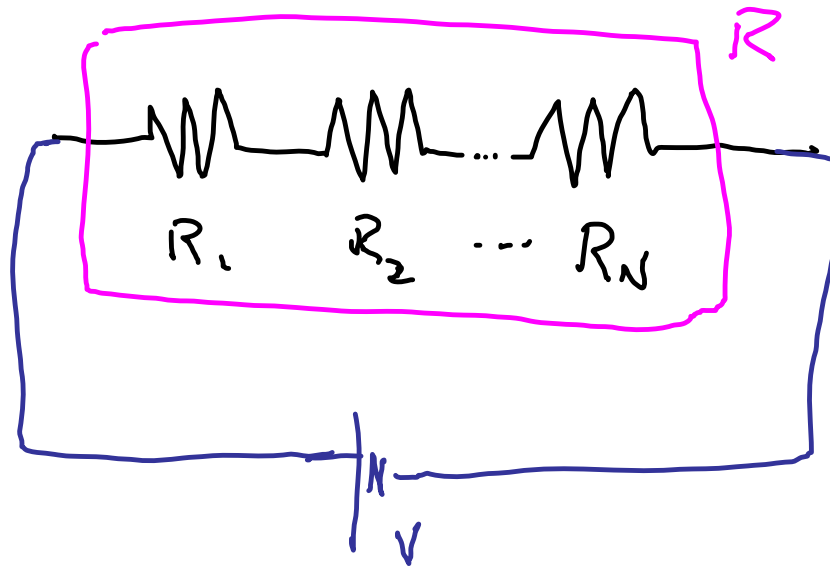


Resistors
in
series

$$V = V_1 + V_2 + \dots + V_N = iR_1 + iR_2 + \dots + iR_N$$

$$V = i(R_1 + \dots + R_N)$$

$$V = i \left[\sum_j R_j \right]$$

$$R = \sum_j R_j$$

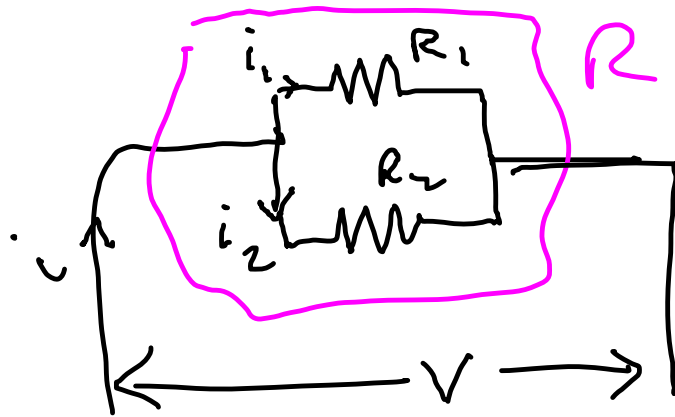

Resistors in //

$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \sum_j \frac{1}{R_j}$$

Parallel

Capacitors

$$C = \sum_i C_i$$


Resistors

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

Series

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

$$R = \sum_i R_i$$

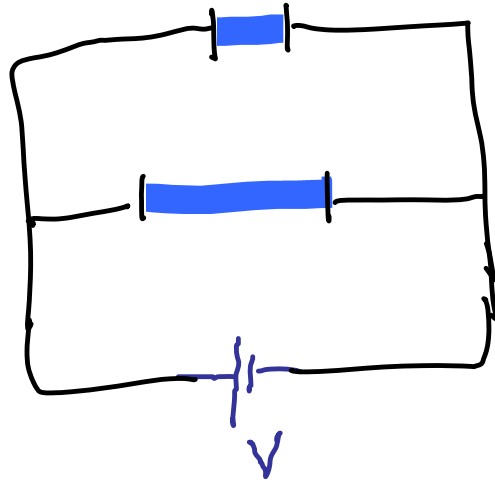


Make V large.

Which nail melts first?

(a) Short

(b) long

(c) Both at same time

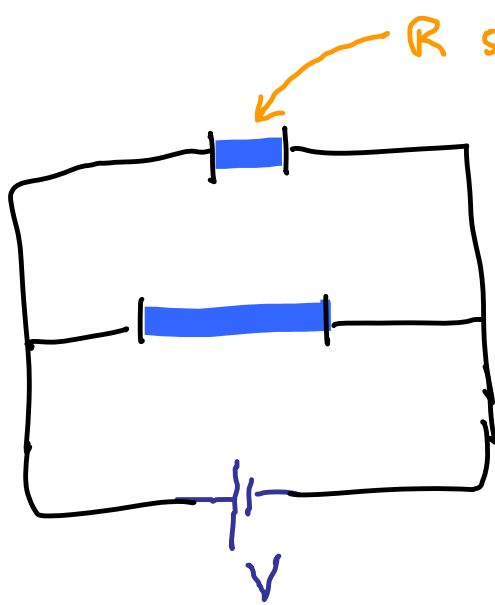

R smaller, i larger

$$V = iR$$

$$P = i^2 R$$

Resistive heating \sim Power

Make V large.

Which nail melts first?

- (a) Short
- (b) long
- (c) Both at same time