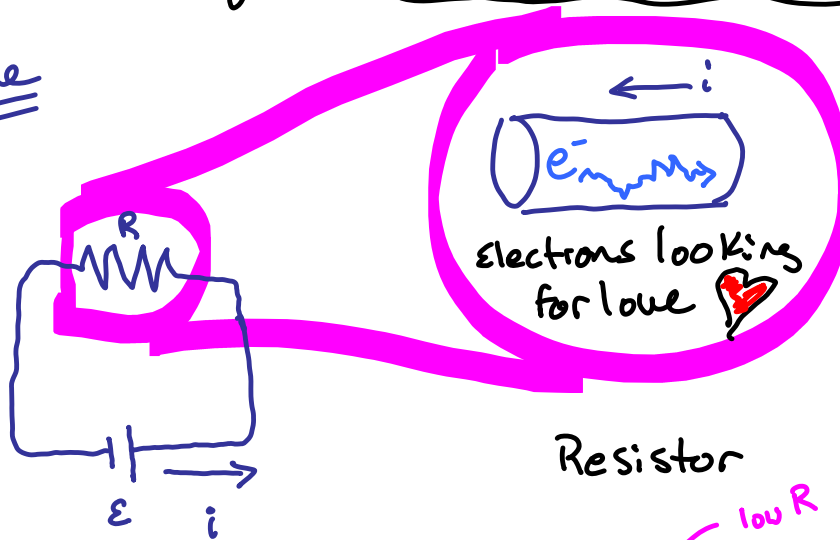


Physics 114 - February 26, 2015

LAST TIME





Resistor

RESISTANCE

$$\epsilon = iR$$
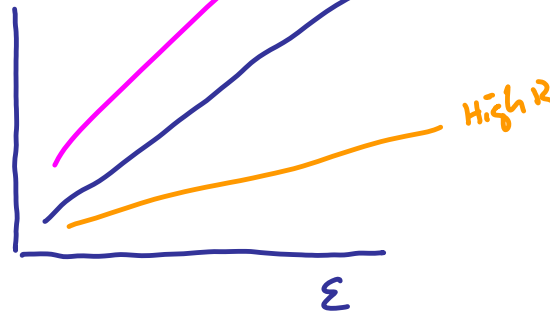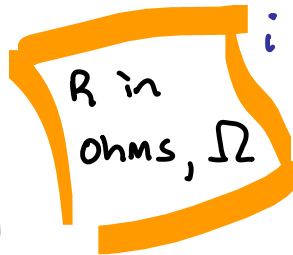
$$\begin{pmatrix} \epsilon \\ v \end{pmatrix} = \begin{pmatrix} i \\ I \end{pmatrix} \begin{pmatrix} R \\ r \end{pmatrix}$$



Current, i or I , Amperes $\equiv A \equiv \frac{\text{Coul}}{\text{sec}}$

$$I = dq/dt$$

$$V = iR$$

$$P = iV = i^2 R = V^2/R$$



Resistors in series


$$R = \sum_i r_i$$




Resistors in parallel


$$\frac{1}{R} = \sum \frac{1}{r_i}$$

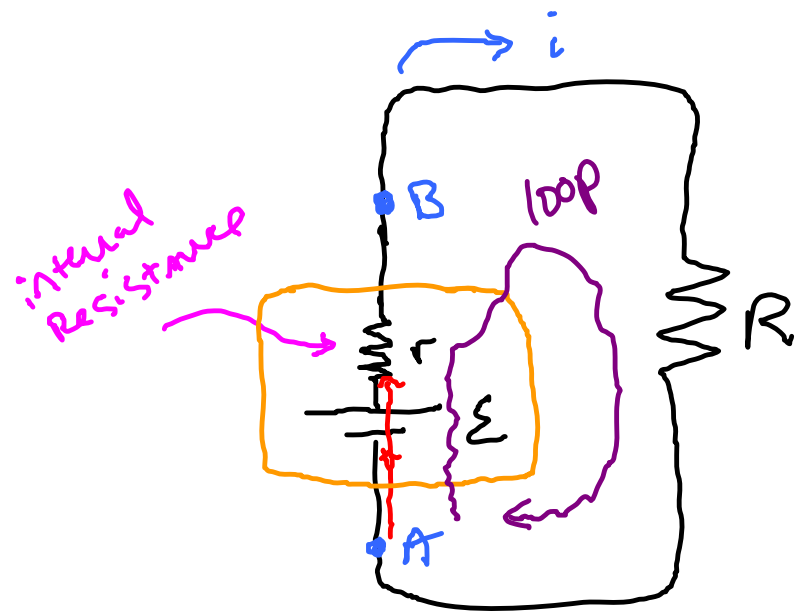How the potential changes as we
Move around a closed loop in the circuit




Define $V_A = 0$

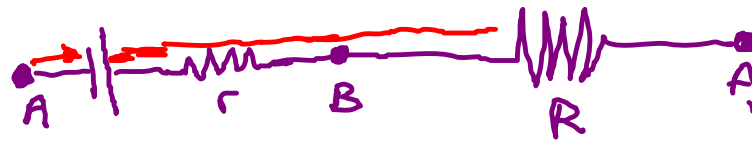

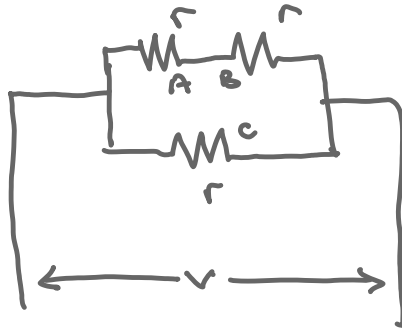

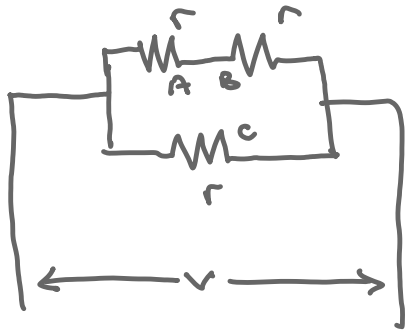
3 lightbulbs Arranged
as shown
order the brightnes of the
Bulbs



3 lightbulbs Arranged
as shown
order the brightness of the
Bulbs

Brightness
ordering

$C > A = B$

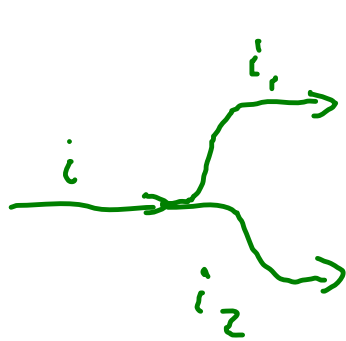


i same in A, B

$$P = i^2 r = vi$$

Top	$V = i(2r)$	$i_t = \frac{V}{2r}$	$P = \frac{V^2}{4r^2} r$
Bot	$V = i r$	$i_b = \frac{V}{r}$	$P = \frac{V^2}{r}$


$$\frac{V^2}{4r}$$



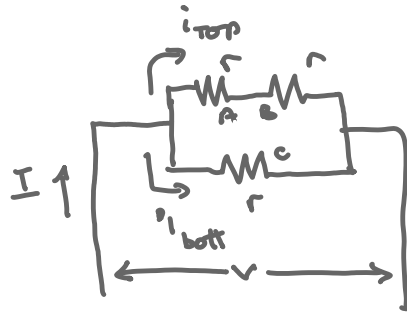

3 lightbulbs arranged
as shown

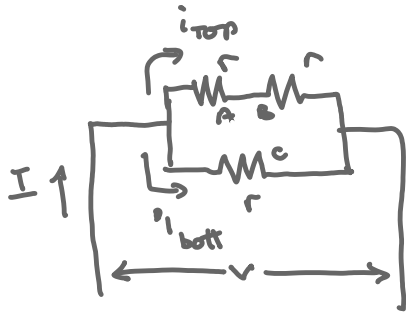What happens to the brightness
of C if bulb A is unscrewed?




3 lightbulbs Arranged
as shown

What happens to the brightness
of c if bulb A is unscrewed




Does what?

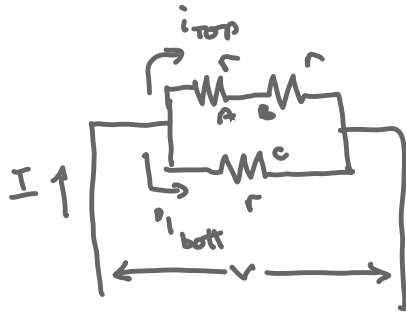


3 lightbulbs Arranged
as shown

What happens to the brightness
of c if bulb A is unscrewed

Becomes

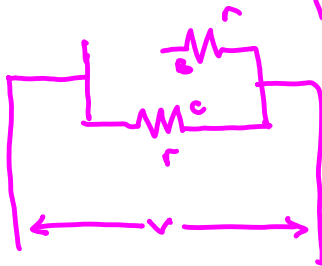


means

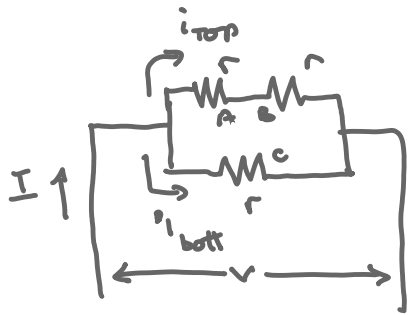

3 lightbulbs Arranged
as shown

What happens to the brightness
of c if bulb A is unscrewed

Becomes

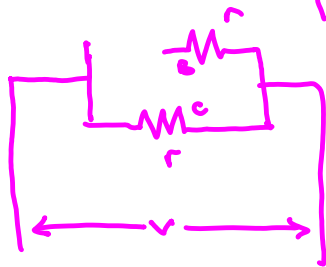


Means that
part of circuit is
broken

V across bulb c is unchanged \rightarrow i through bottom branch
is unchanged
 \rightarrow Brightness of C is unchanged

Current No longer flows thru top branch

R in circuit changes, total I changes $\rightarrow I = i_{top} + i_{bottom} \rightarrow I = i_{bottom}$

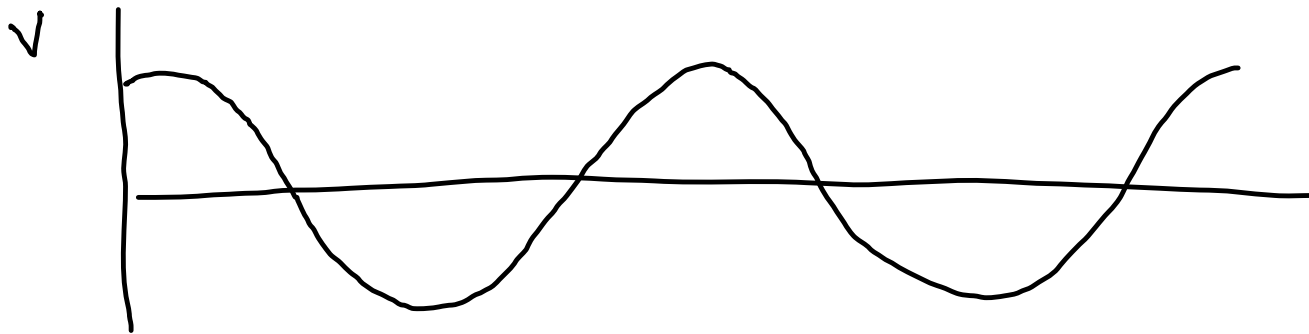Direct current — DC \mathcal{E} fixed and unchanging



Alternating current AC

Kirchoff's Rules

① $\sum V = 0$ around closed loop

② $\sum i = 0$ at junctions

Apply to independent loops and junctions.

Derive N independent eqns
can solve for N indep. unknowns.

guts + Conventions + Consistency



determined Kirchoff's
Laws at age 21

played for ZZ Top
in the early days




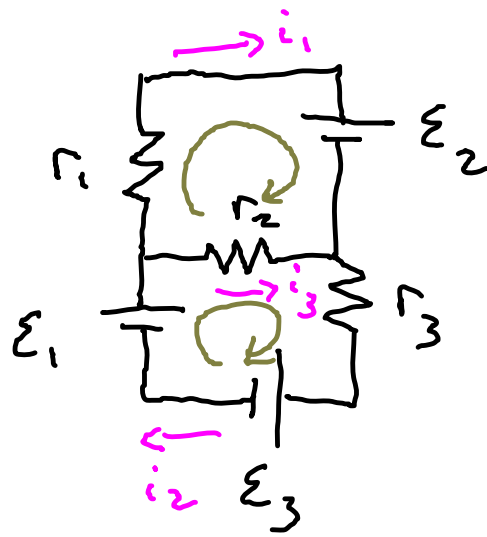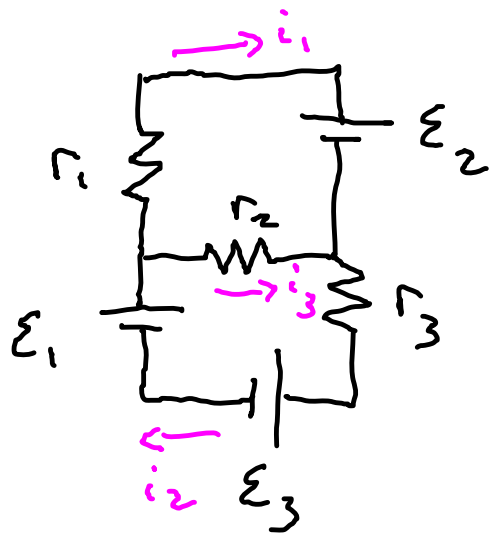
Gustav Robert Kirchoff
Germany (1824-1887)






Sum ΔV as walk around each loop

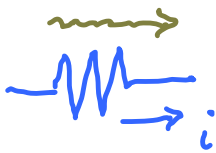ΔV is $-$ if 

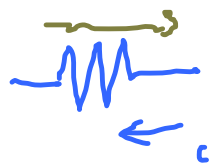ΔV is $+$ if 

$$\Delta V \text{ is } + \text{ if } \begin{array}{c} \text{--->} \\ | \\ \text{--->} \end{array}$$

$$\Delta V \text{ is } - \text{ if } \begin{array}{c} \text{--->} \\ | \\ \text{--->} \end{array}$$

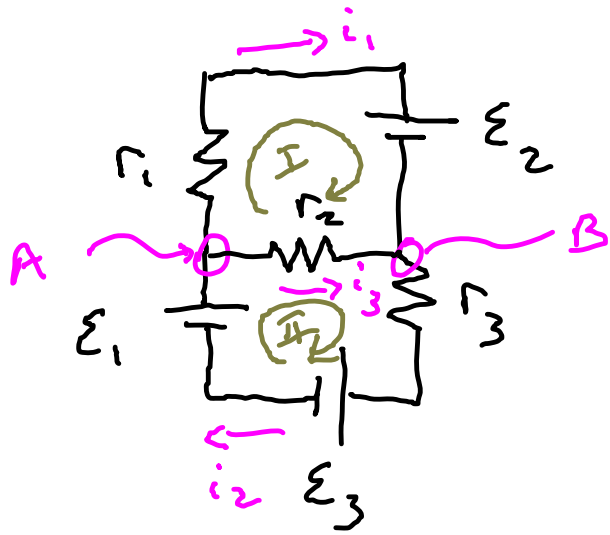

$$\sum i_{\text{junction}} = 0$$

Junction A

$$i_2 - i_1 - i_3 = 0$$

$$i_2 = i_1 + i_3$$

Junction B
NOT indep info

$\Delta V = 0$ for Loop I

$$-i_1 r_1 - E_2 + i_3 r_2 = 0$$

Loop II

$$E_1 - i_3 r_2 - i_2 r_3 - E_3 = 0$$