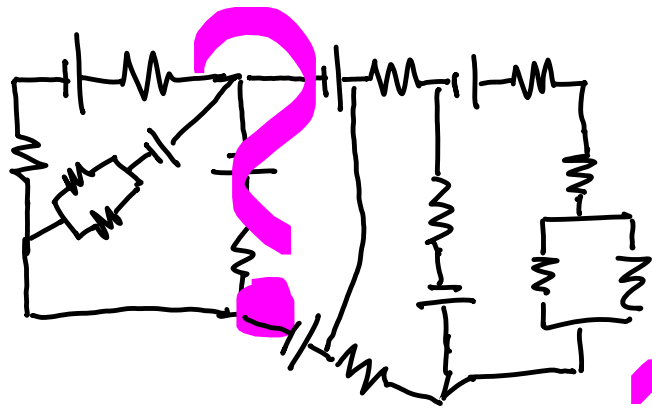



Physics 114 - March 3, 2015

Last Time

Kirchoff's Rules:



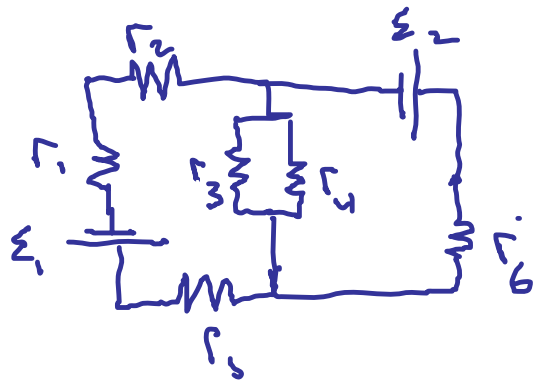
- Assign currents
- Select independent loops
- $\sum i = 0$ at junctions
- $\sum v = 0$ around loops
- N equations, N unknowns
 - Solve algebra for unknowns






How Many independent currents?

How Many independent loop equations?

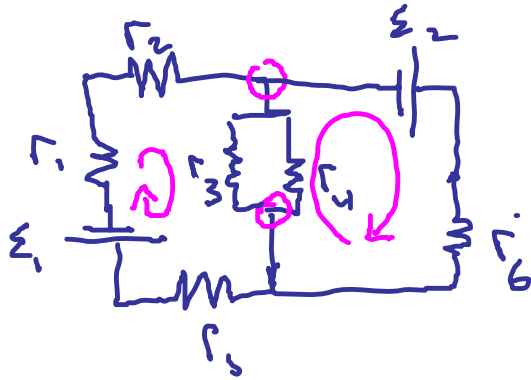How Many independent current junction equations




Conventions

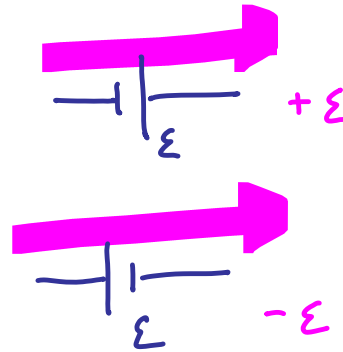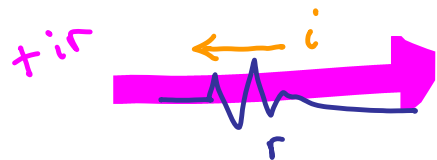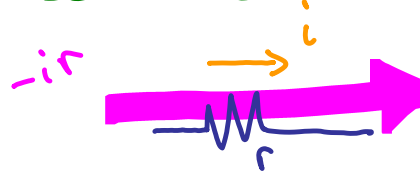


Be consistent
Be careful

RC circuits

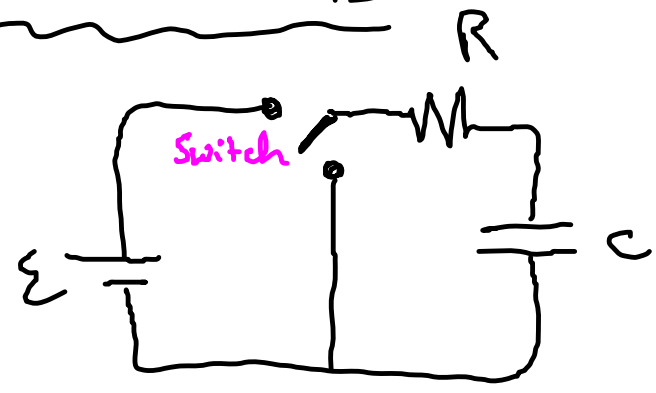

charging RC circuit

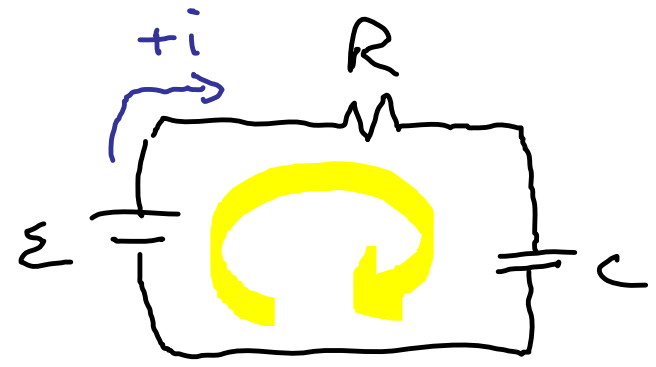

$$Q = CV$$

$$\sum V = 0$$

$$0 = \mathcal{E} - \underbrace{iR}_{V_R} - \underbrace{q/C}_{V_C}$$




$$0 = \varepsilon - \frac{dq}{dt} R - q/c$$

$$q \rightarrow q(t)$$


$$q(t) = c\varepsilon(1 - e^{-t/RC})$$


First order
ordinary
differential
equation

$$g(t) = C \mathcal{E} (1 - e^{-t/RC})$$

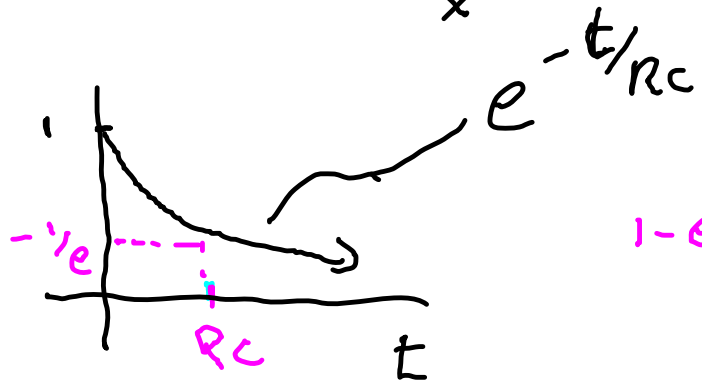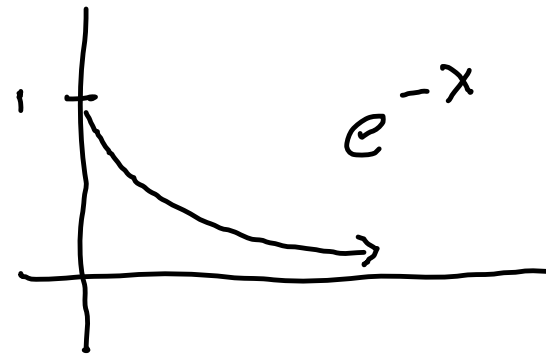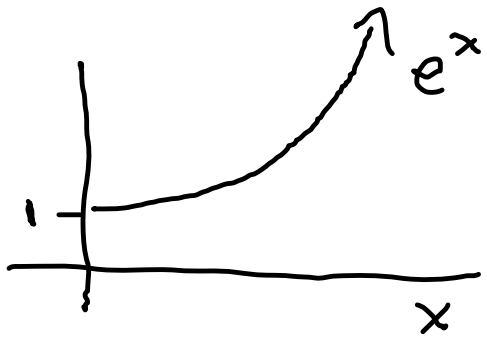



$1 - e^{-1}$

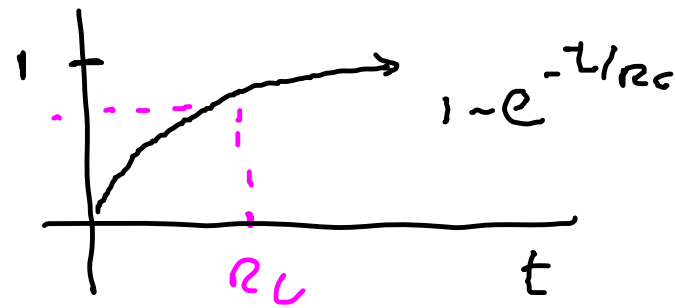

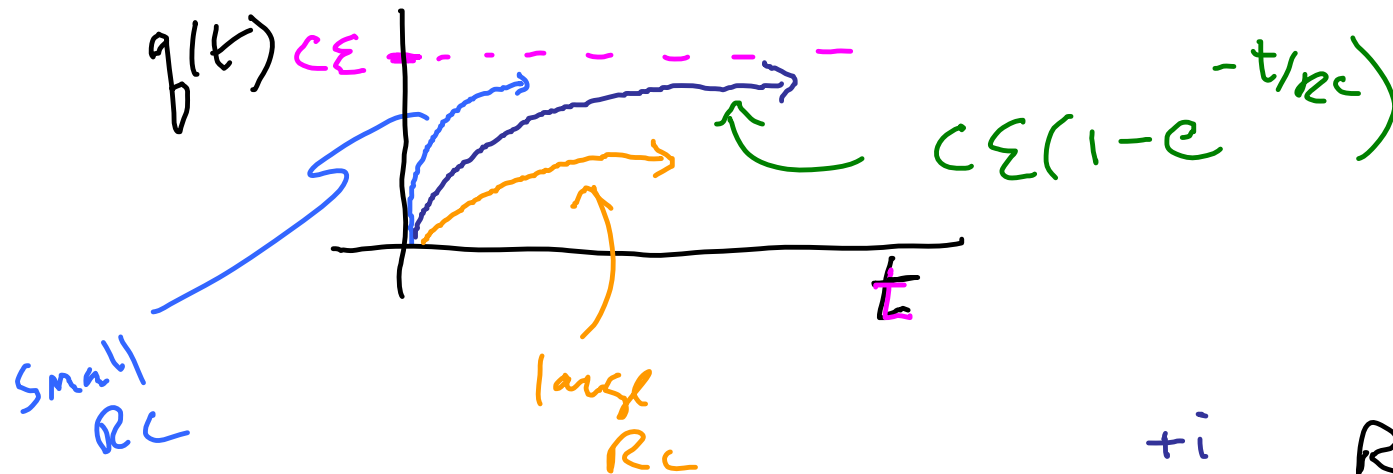

$RC \equiv$ "Time constant"

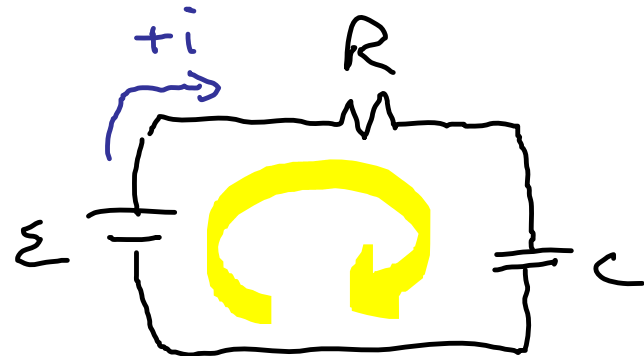

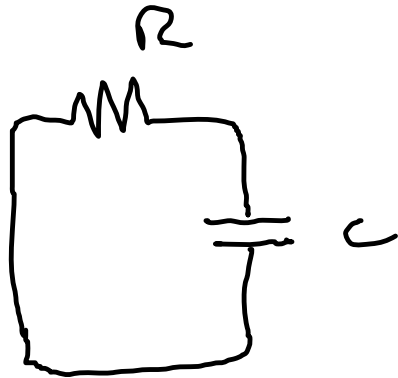

Fully charged C at $t=0$

$$Q_0 = CE$$

discharging RC circuit

$$0 = \cancel{\varepsilon} - iR - q/C$$

\swarrow
0

$$\frac{dq}{dt} = -\frac{q}{RC}$$


$$\frac{dq}{q} = -\frac{1}{RC} dt$$

$$\int_{g_0}^{g(t)} \frac{dg}{g} = \int_0^t \left(-\frac{1}{RC}\right) dt$$



$$\ln \frac{g}{g_0} = -\frac{t}{RC}$$

$$\frac{g}{g_0} = e^{-t/RC}$$

$$g(t) = g_0 e^{-t/RC}$$

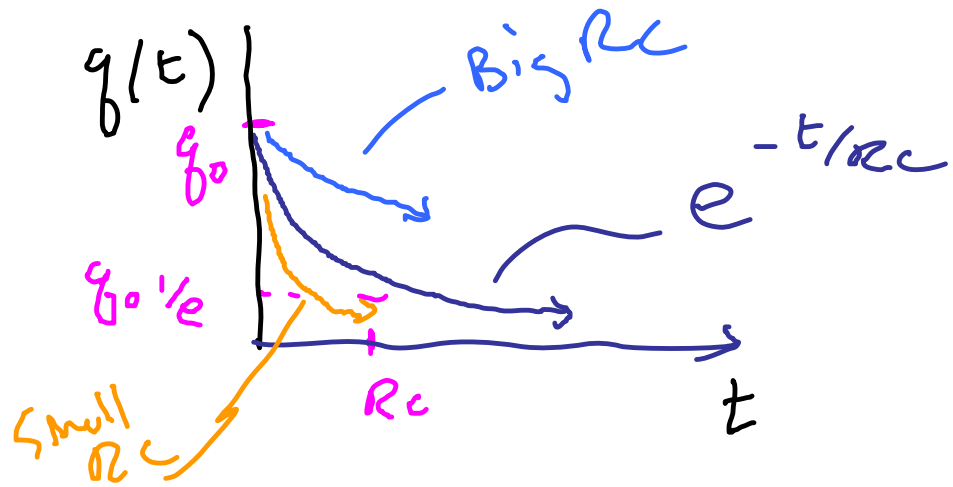


Magnetism

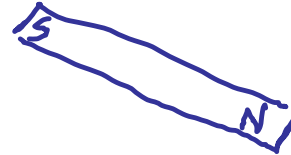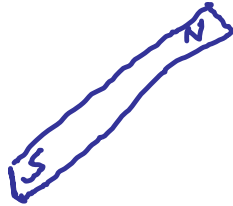


Lorentz
Force law
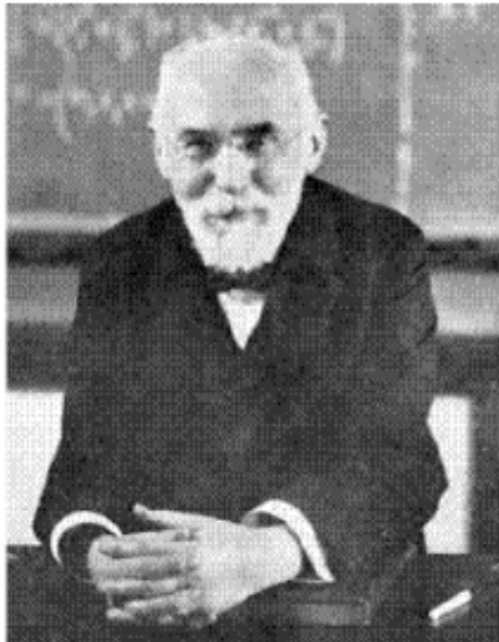
$$\vec{F} = q \vec{E} + q \vec{v} \times \vec{B}$$




Hendrik Antoon Lorentz
(1853 - 1928)

Dutch - 1902 Nobel Prize

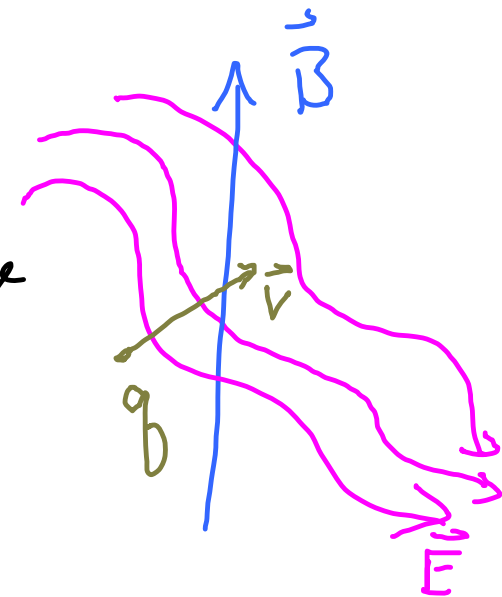

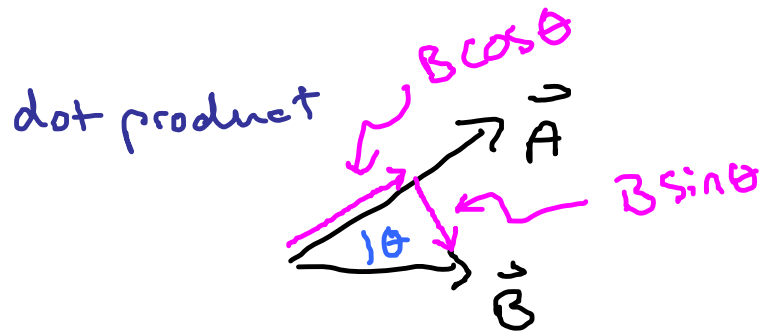What is a "cross-product", i.e., $\vec{V} \times \vec{W}$




$$\vec{A} \cdot \vec{B} = |\vec{A}| |\vec{B}| \cos \theta$$

$$\vec{A} \cdot \vec{B} = A_x B_x + A_y B_y + A_z B_z$$

Scalar

#, NOT a vector

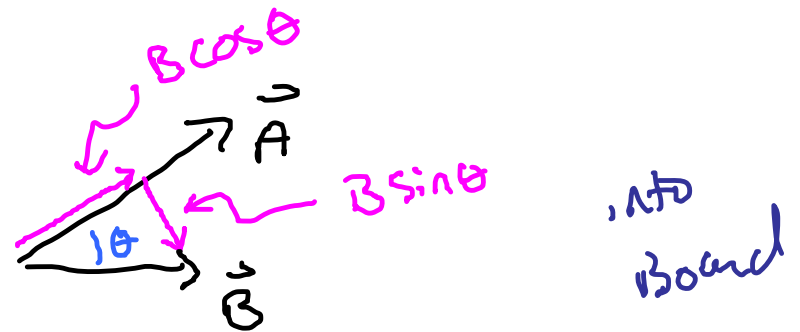

$$|\vec{A} \times \vec{B}| = |\vec{A}| |\vec{B}| \sin \theta$$

Vector direction
is given by
right-hand rule