

Physics 142 - October 5, 2010

■ Exam I - 0800 Thursday B+L 109

■ Q+A session Today, B+L 106, 4:30 pm

Last
Time

Energy stored in a capacitor

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV$$

Energy
Density
in \vec{E} field

general
Result

$$u_E = \frac{\epsilon_0}{2} |\vec{E}|^2$$

Energy density in Electric field $u_E = \frac{\epsilon_0}{2} |\vec{E}|^2$



if know \vec{E}

$$U = \int_{Vol} u_E dV$$

(linear) Dielectrics

\vec{E} in materials


$$\vec{E} = \frac{\vec{E}_0}{K}$$

$K \equiv$ Dielectric constant


$$K > 1$$

K material dependent
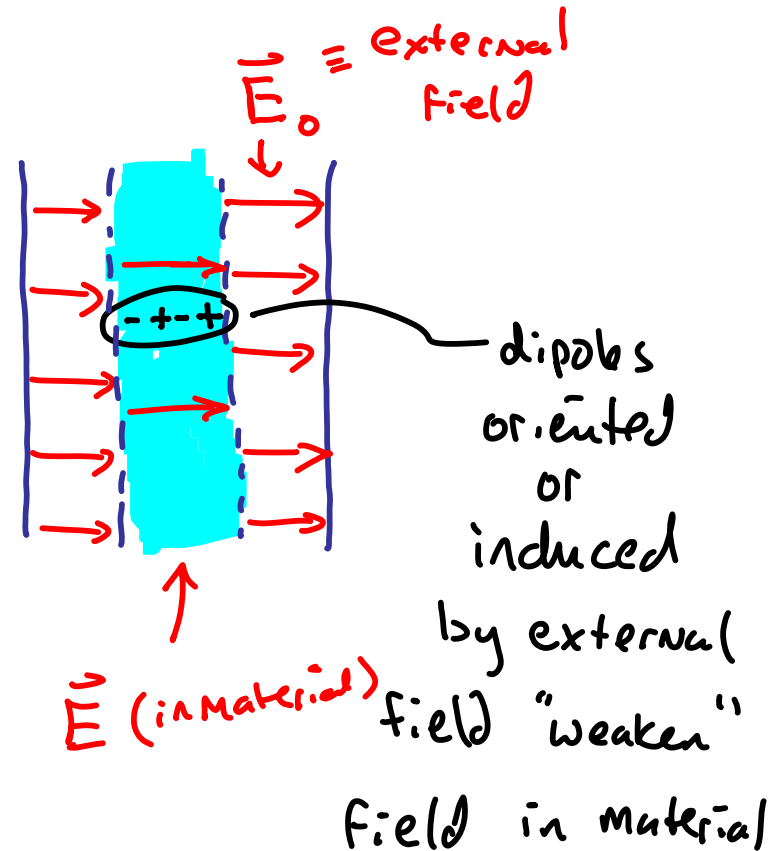
$$\frac{1}{K} \equiv \epsilon \equiv \text{permittivity}$$



Currents and Resistance

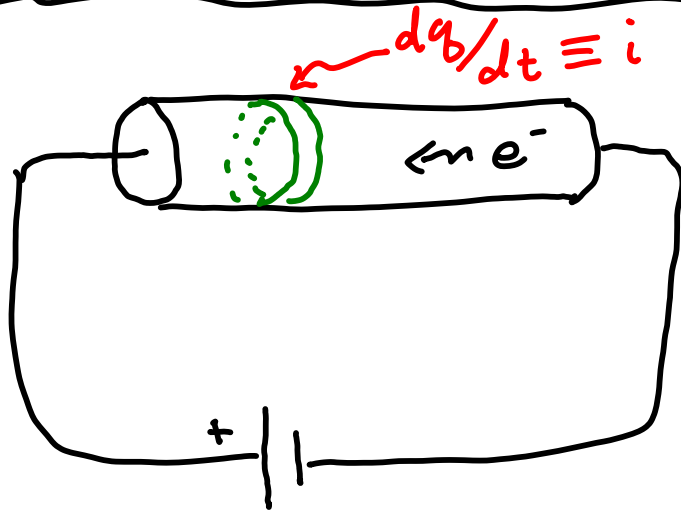

+ current flow
is direction
+ charge
would move

"Resistance"
impedes electrons
looking for low

$i \equiv \frac{dq}{dt}$ in units $\frac{\text{Coul}}{\text{Sec}} \equiv \text{Ampere}$





$i \propto V$

$V = iR$

\equiv Resistance

Ohm's law

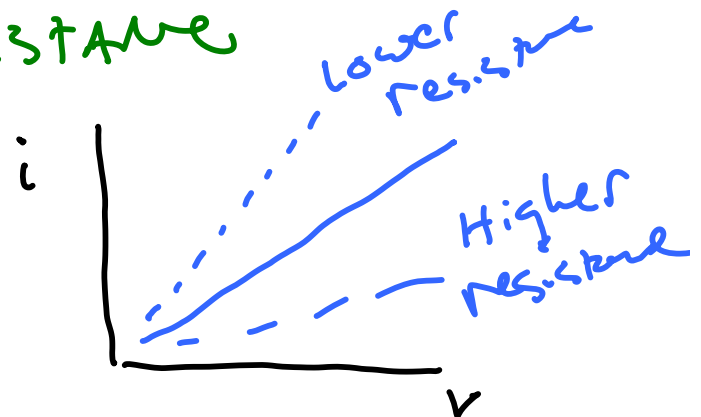

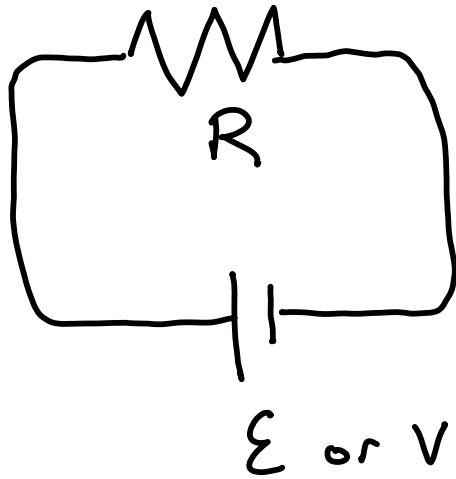

R units
are ohms


$$V = \frac{w}{q}$$

$$w = qV$$

$$\text{Power} = \frac{dw}{dt} = dq \frac{V}{dt} = iV$$

$$V = iR$$

$$P = iV = \frac{V^2}{R} = i^2 R$$

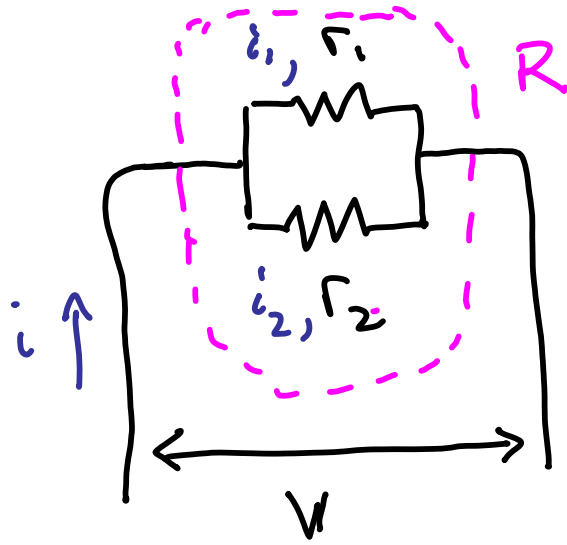

Resistors in Parallel

$$V = i_1 r_1$$

$$V = i_2 r_2$$

$$V = i R$$

$$i = i_1 + i_2$$


$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{r_1} + \frac{V}{r_2}$$

→

$$\frac{1}{R} = \frac{1}{r_1} + \frac{1}{r_2}$$
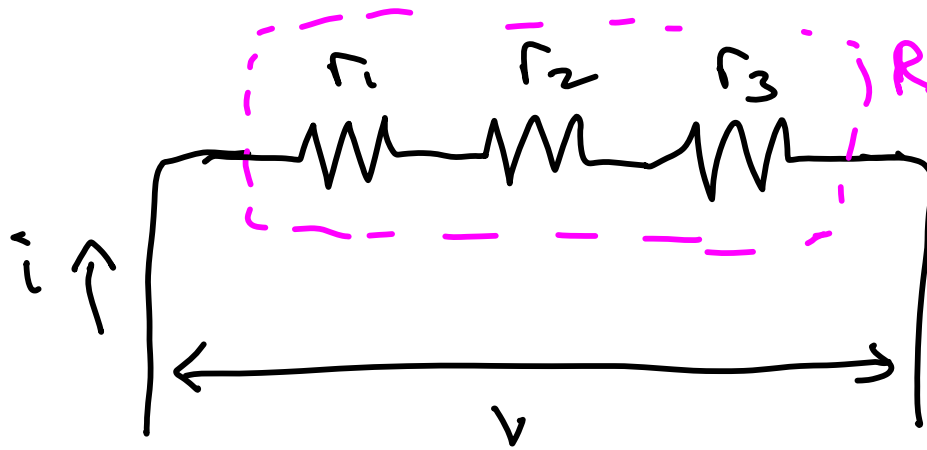
$$\frac{1}{R} = \sum_{i=1}^n \frac{1}{r_i}$$



Resistors
in
Series


$$V = iR$$

$$V = V_1 + V_2 + V_3$$


$$iR = i r_1 + i r_2 + i r_3$$


$$R = r_1 + r_2 + r_3$$

$$R = \sum_i r_i$$

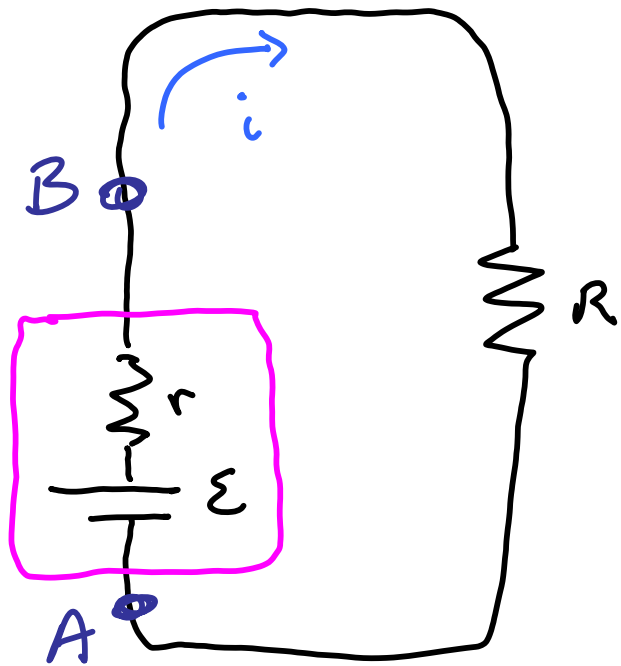

Potential

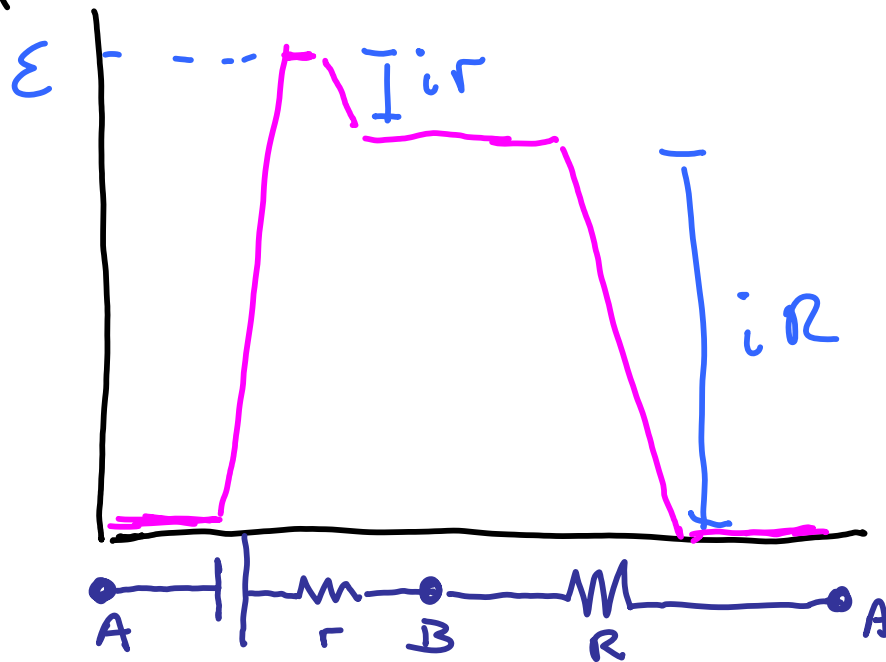

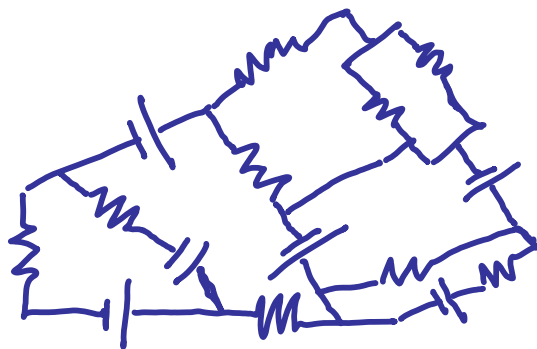

Suppose you meet
a circuit
in a dark
Alley one
night ...

... And the electrons are
NOT looking for love ...

Kirchoff's Rules:

- ① $\sum V = 0$ around closed loop in circuit
- ② current is conserved at any
BRANCH point in circuit

-
- use these rules to create N independent equations to solve for N unknowns
 - Choose independent loops
 - Use sign conventions consistently + with care


Convention [told this is opposite that of ECE 210]
↳ no matter if consistent


Choose currents in each branch (arbitrary)

Sum ΔV across each circuit component as you go around an imaginary closed loop in the circuit

$\Delta V -$ if 

$\mathcal{E} +$ if 


$\Delta V +$ if 

$\mathcal{E} -$ if 

Get N eqns, N unknowns and solve

Tedious \rightarrow must be careful and consistent
↳ Conventions and signs

use only independent loops

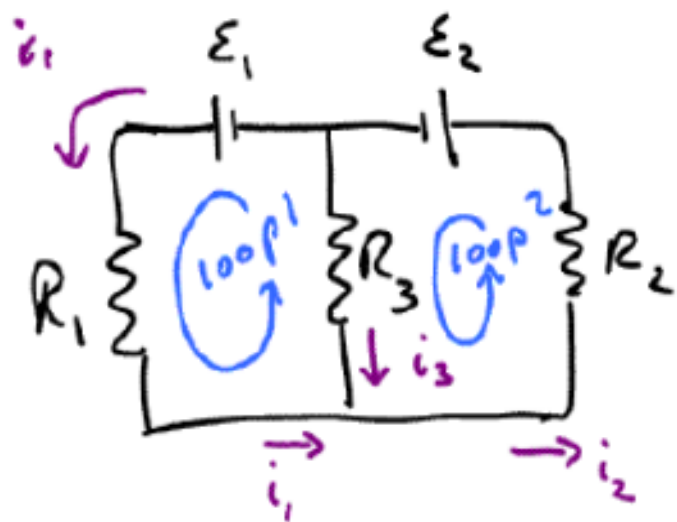

Know $\mathcal{E}_1, \mathcal{E}_2$
 R_1, R_2, R_3

Solve for current
 thru out
 circuit

Kirchoff's 2ND rule $i_1 + i_3 = i_2$ (I)

$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$ (II)

$-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$ (III)

