

# Physics 142 - November 2, 2010

Note Title

11/2/2010

- Presentation Group updates
- Spokes person
- Meeting

Remember  
to  
Vote

# Induction

$$\Phi_m = \int_{\text{loop}} \vec{B} \cdot d\vec{A}$$

$$\mathcal{E} = \int_{\text{loop}} \vec{E} \cdot d\vec{l} = -\frac{d\Phi_m}{dt}$$

↑  
induced EMF


All very  
Important

Lenz's Law - An induced current in a closed conducting loop will appear in such a way as to oppose the change that created it

Gives the direction of induced effect

# Superconductors + induction



loop moving in B field

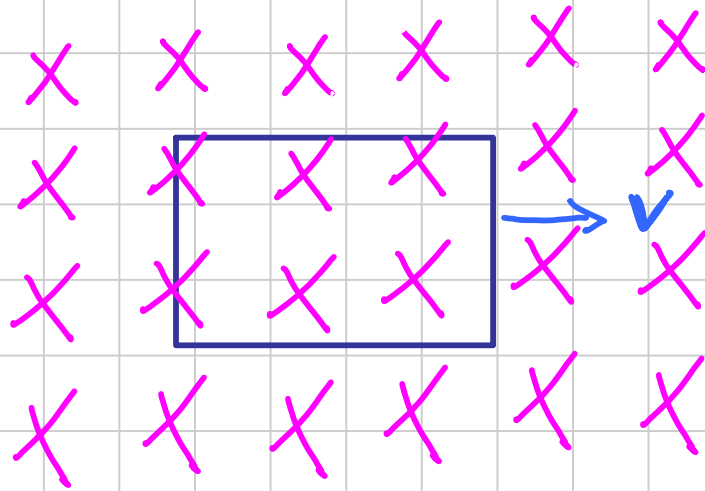


check out  
the induction

java applet

on class  
website

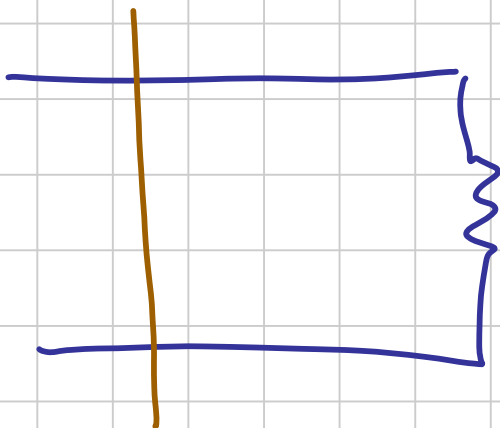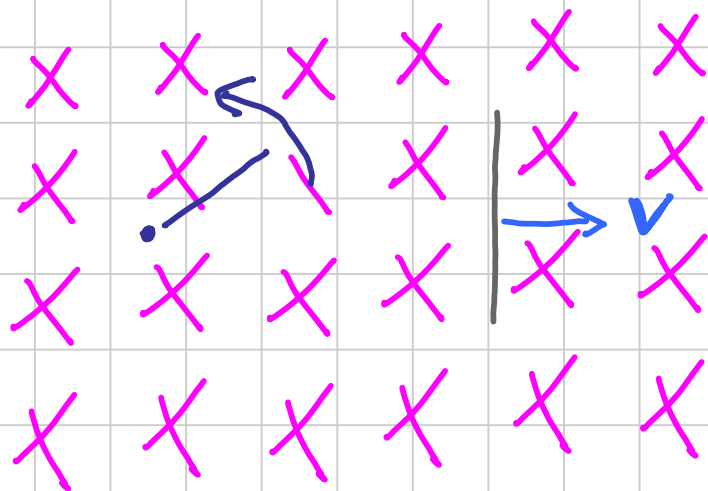


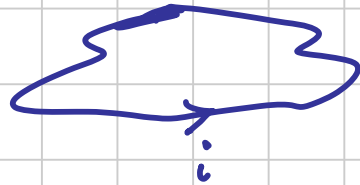

$$\Phi_m = L i$$

$L \equiv$  CONSTANT of Self-inductance
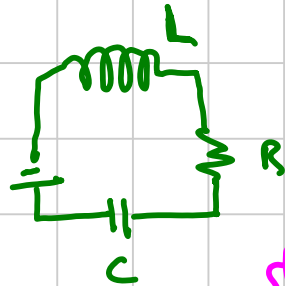
$$\mathcal{E} = - \frac{d\Phi_m}{dt} = - L \frac{di}{dt}$$



$\text{units } \text{Henry's}$

$$\mathcal{E} = - L \frac{di}{dt}$$



$$\Phi_{m(2)} = M i_{(1)}$$

$$\Phi_{m(1)} = M i_{(2)}$$

SAME "M" Cross-Talk dictated by Geometry

$M \equiv$  CONSTANT of Mutual inductance

$$\mathcal{E}_{(2) \text{ by } (1)} = - M \frac{di_{(1)}}{dt}$$

$$\mathcal{E}_{(1) \text{ by } (2)} = - M \frac{di_{(2)}}{dt}$$

unless problem is specifically about mutual inductance ... usually treat inductance in a circuit as self-inductance

Energy density in the fields:

$$u_E = \frac{\epsilon_0 E^2}{2} \quad u_B = \frac{B^2}{2\mu_0}$$

general — Says nothing about  
circuits or sources  
or boundary  
conditions!


Energy in Inductor

$$U = \frac{1}{2} L I^2$$

similar to  $U_{\text{capacitor}} = \frac{1}{2} C V^2$


LR circuit

$\sum V = 0$  around circuit

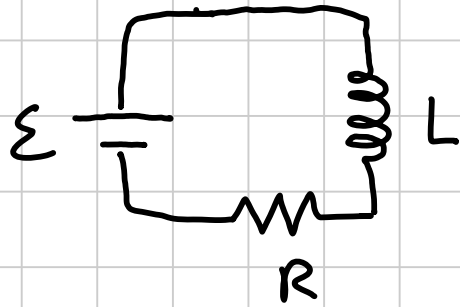

$$\varepsilon - L \frac{di}{dt} - iR = 0$$
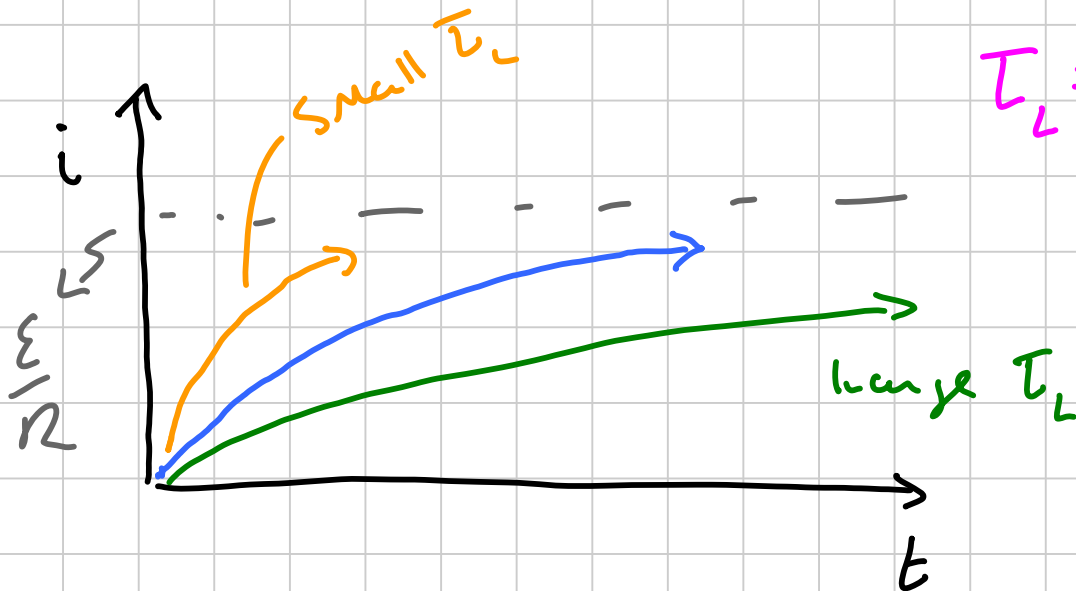
$$i = \frac{\varepsilon}{R} (1 - e^{-tR/L}) = \frac{\varepsilon}{R} (1 - e^{-t/\tau_L})$$




$\tau_L \equiv$  inductive  
Time constant

$$\tau_L = L/R$$

$$V = iR$$


$$V = \mathcal{E}(1 - e^{-t/\tau_L})$$

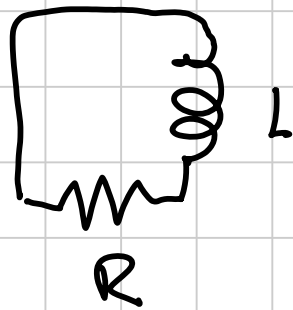AT some time  $t$  later, Short  $L$  across  $R$



$$0 = iR + L \frac{di}{dt}$$
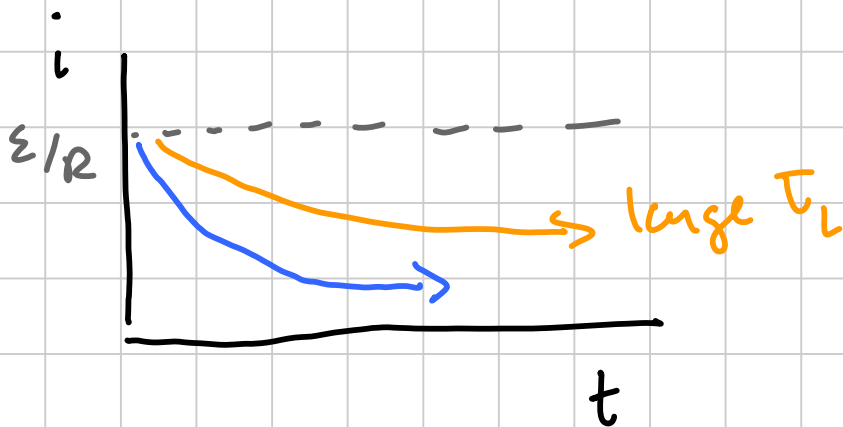
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L}$$






LC circuit

Fully charged capacitor

at  $t=0$

$R \rightarrow 0$

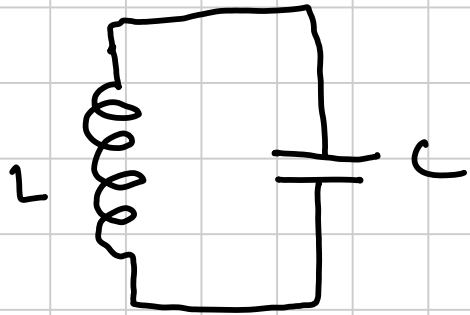

No resistor

$$U = U_E + U_B = \frac{q^2}{2C} + \frac{Li^2}{2}$$

$$\frac{1}{2} CV^2 = \frac{1}{2} \frac{q^2}{C}$$

$$\frac{dU}{dt} = 0 = \frac{dU_E}{dt} + \frac{dU_B}{dt} = \frac{2q}{2C} \frac{dq}{dt} + \frac{L}{2} 2i \frac{di}{dt}$$

$$0 = L \frac{di}{dt} + \frac{q}{C}$$

$$0 = \frac{d^2 q}{dt^2} + \frac{1}{LC} q \quad \text{SHM}$$

SHM  $\Rightarrow \omega = \frac{1}{LC}$   
 $q(t)$

$$q(t) = Q \cos(\omega t + \phi)$$

$$\omega^2 = \frac{1}{LC}$$

phase angle  
↓

$$F = -kx$$

$$m \frac{d^2 x}{dt^2} + kx = 0$$

$$\sin \omega t$$

$$\omega = \pm \sqrt{\frac{k}{m}}$$

$$i(t) = \frac{dq(t)}{dt} = -\omega Q \sin(\omega t + \phi)$$

Look at energy flow

$$U_E = \frac{q^2}{2c} = \frac{Q^2}{2c} \cos^2(\omega t + \phi)$$

E stored in  
C or  
elect. field  
as fn of time


$$U_B = \frac{1}{2} Li^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \phi)$$


$$\omega^2 = \frac{1}{LC}$$

$$\cancel{\frac{L}{2}} \frac{Q^2}{\cancel{c}}$$

↑  
E stored in  
B (inductor)  
as fn of  
time

# LC Oscillations

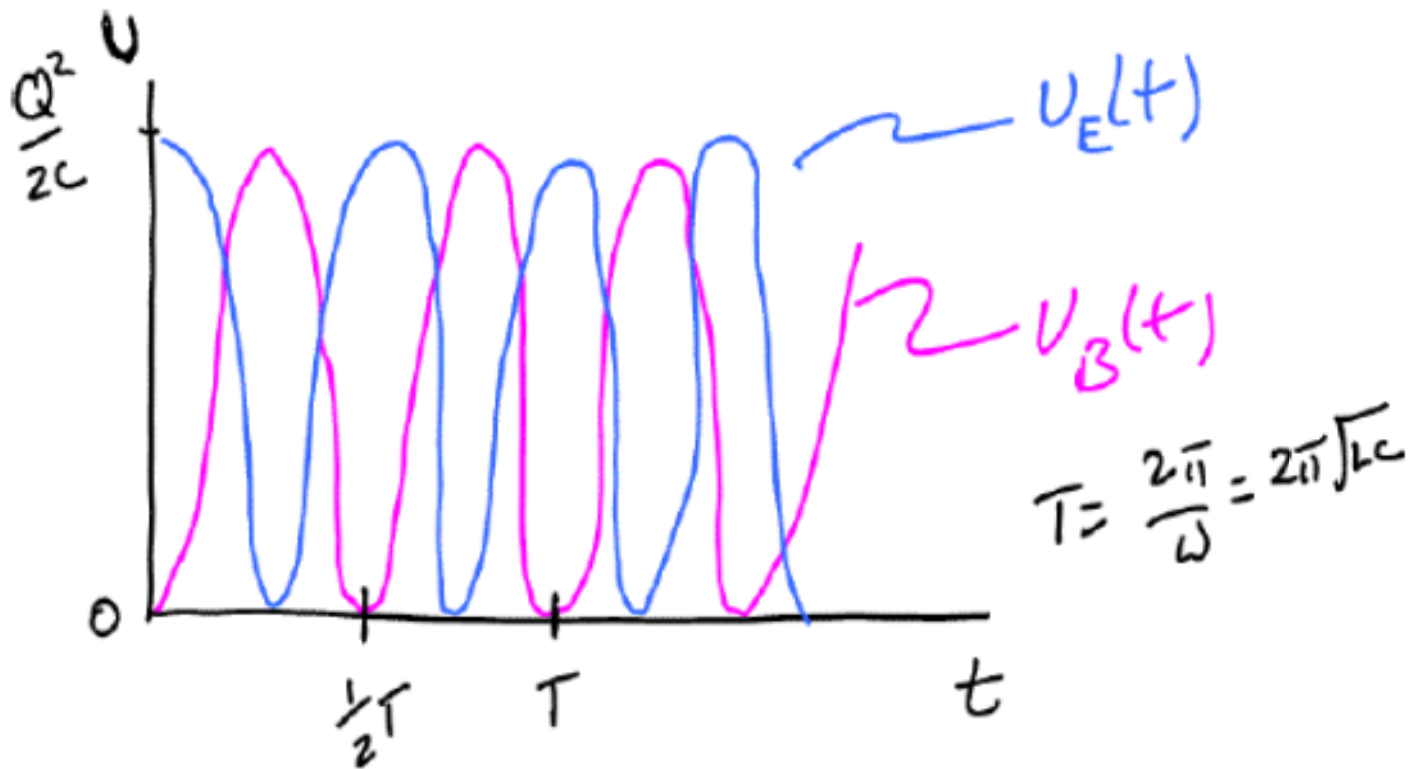


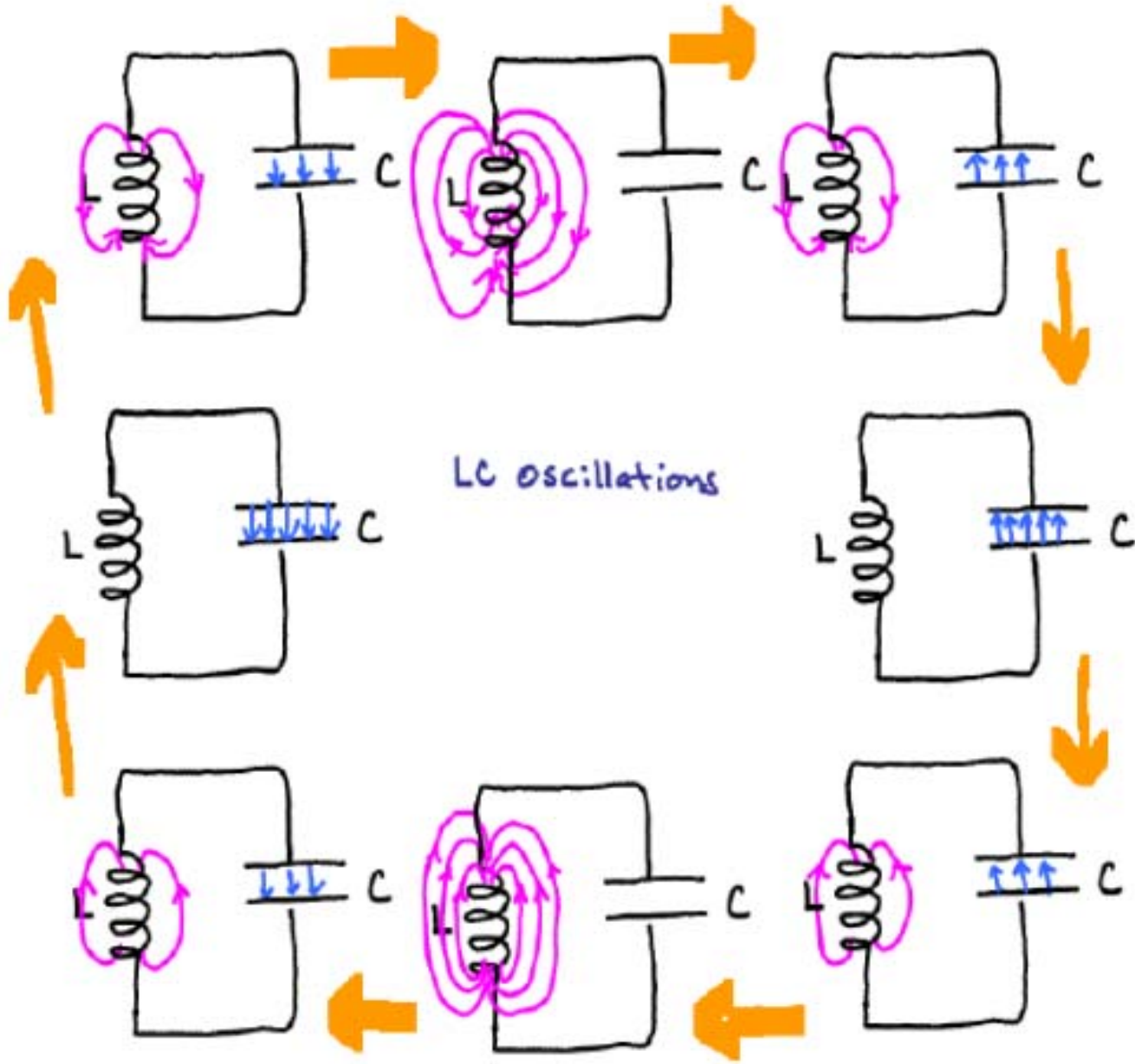

LC Oscillations

# AC circuits

Alternating current

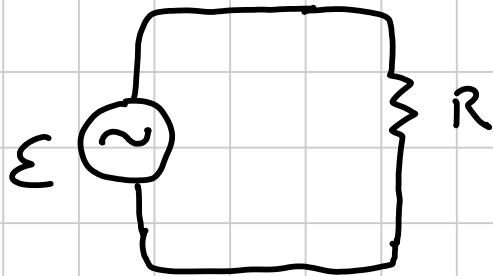

$$\varepsilon = \varepsilon_{\max} \sin \omega t$$


Kirchoff

$$\varepsilon - IR = 0$$

$$I = \frac{\varepsilon}{R} = \frac{\varepsilon_{\max} \sin \omega t}{R}$$

Inst. Power dissipation
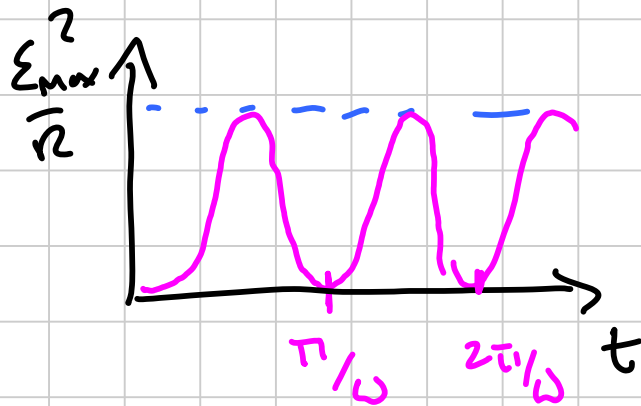
$$P = IV = I \varepsilon = \frac{\varepsilon_{\max}^2}{R} \sin^2 \omega t$$



$$\overline{\sin^2 \omega t} = \frac{1}{2}$$

$$\overline{P} = \frac{\varepsilon_{\max}^2}{2R}$$