

Physics 142 - November 4, 2010

Note Title

11/4/2010

Exam 2 looms

Nov 16, 2010 0800 Location TBA

Same drill as last time



Info concerning material coverage soon

Material coverage begins
after Exam 1 Material

- Presentation groups - Meet
Do a bit of work
Elect contact
Meet with me


Last Time -

LR circuit

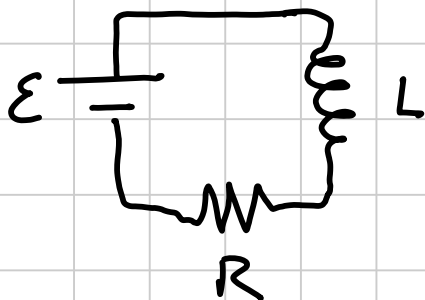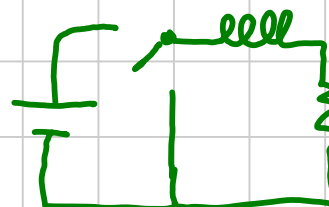


small L
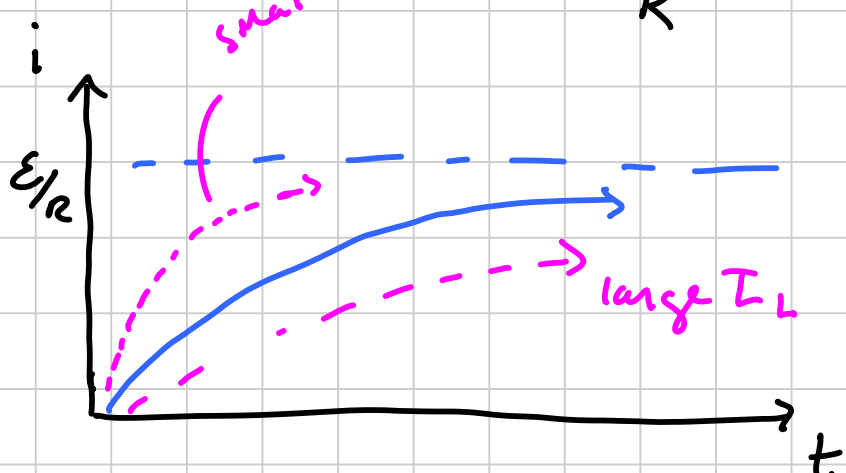
$$i = \frac{\epsilon}{R} (1 - e^{-tR/L}) = \frac{\epsilon}{R} (1 - e^{-t/\tau_L})$$




Induction time
constant
|||

$$\frac{L}{R} = \tau_L$$

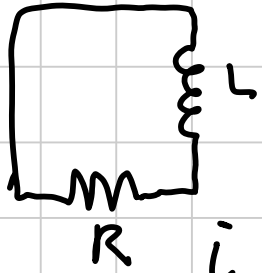

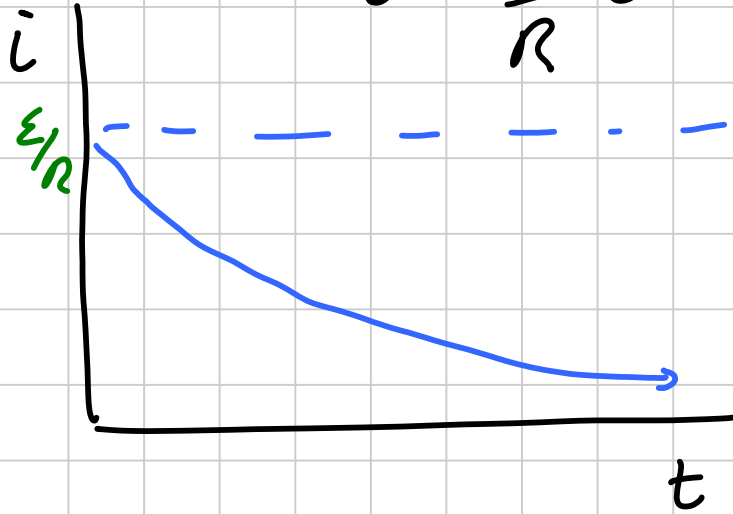
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$




LC Circuit

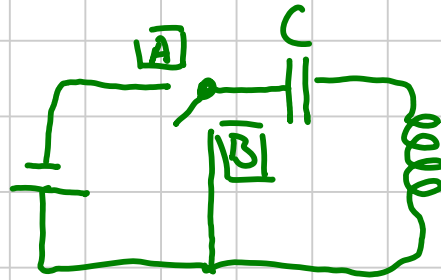Charge capacitor fully with switch in position **A**



Switch to position **B**
Then analyze Energy
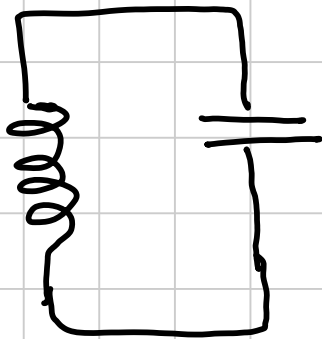
$$U = U_B + U_E = \frac{1}{2} L i^2 + \frac{q^2}{2C}$$



Look at $\frac{dq}{dt}$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

diff eqn

$$q(t) = Q \cos(\omega t + \varphi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$


HARMONIC

Energy flow

$$U_E = \frac{q^2}{2C} = \frac{Q^2 \cos^2(\omega t + \varphi)}{2C}$$

$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \varphi)$$

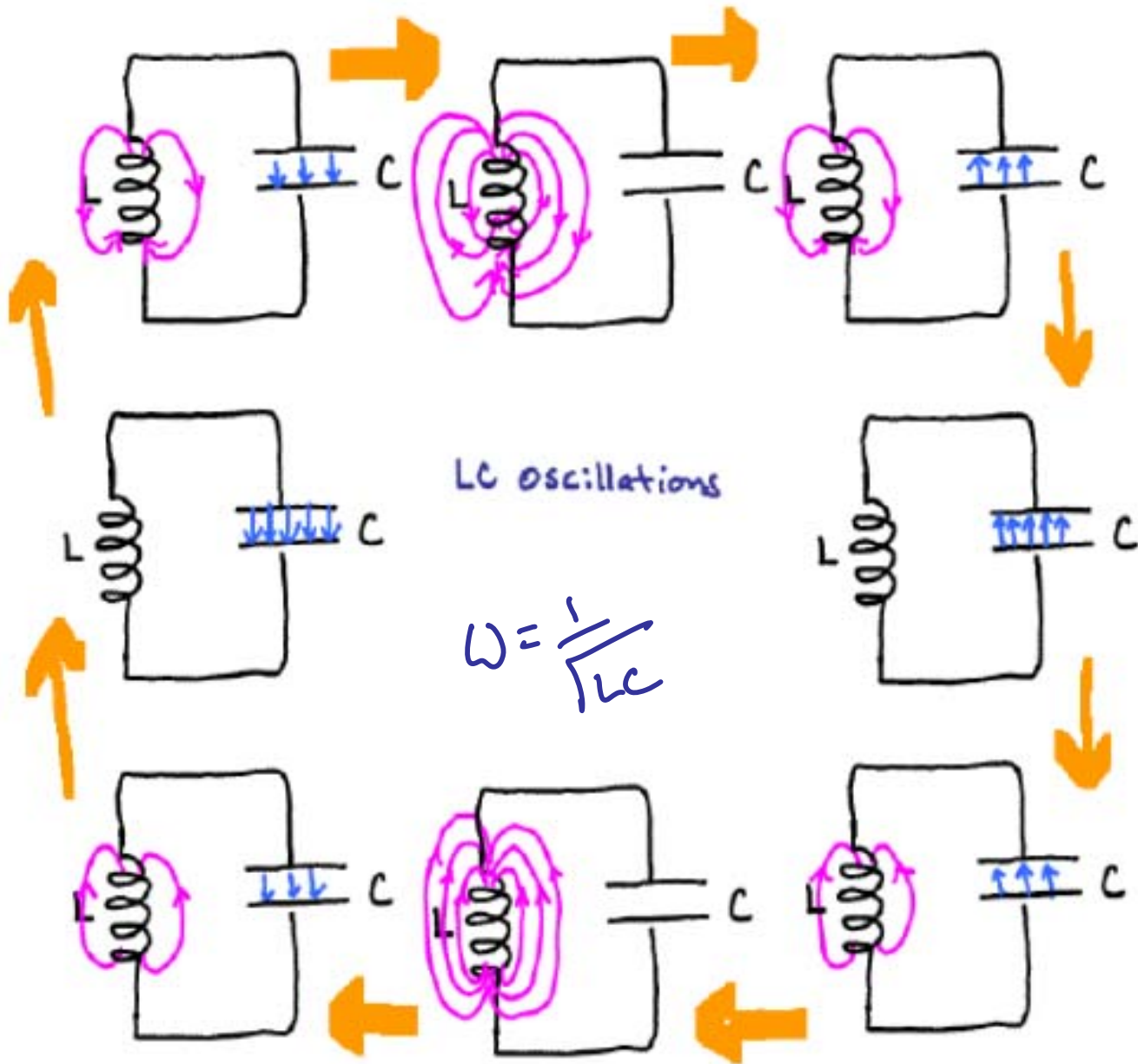
Energy flows from capacitor to inductor + back
(E field) (B field)




LC oscillations

$$\omega = \frac{1}{\sqrt{LC}}$$

DEMO

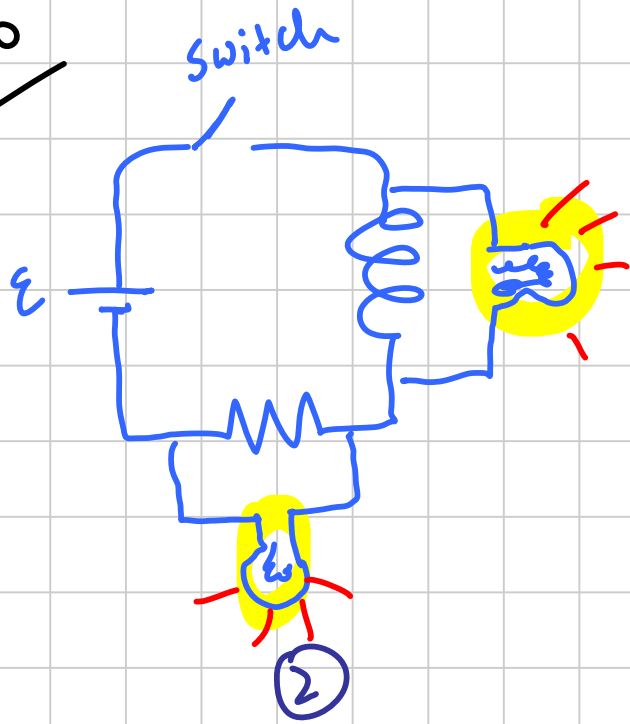

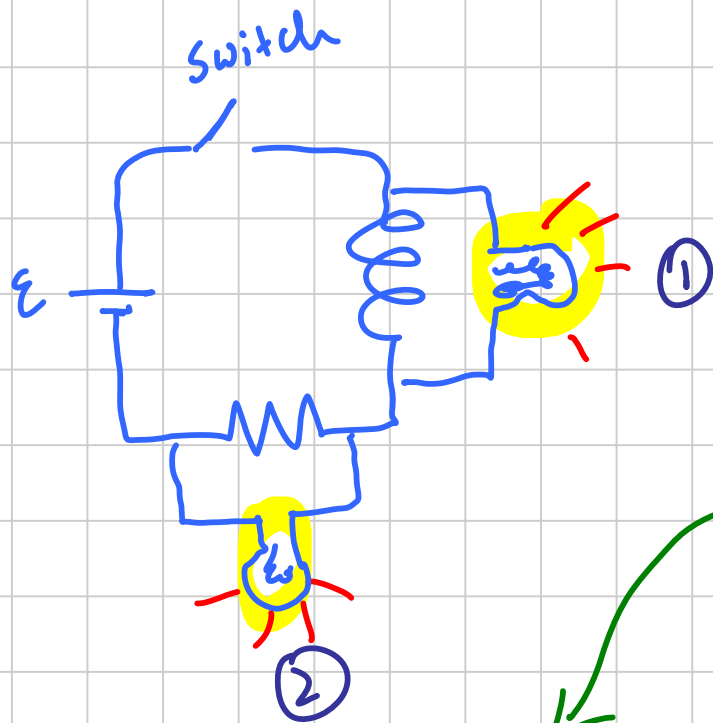

did demo -

Turn switch on
what happens to
light bulbs?

Turn switch off
what happens
to light bulbs?

early time
switch on $i=0$, $\frac{di}{dt}$ big \rightarrow ② off ① bright
 some time later i increases ② gets brighter
 $\frac{di}{dt}$ less ① dims

~ follows Ohanian's Treatment

AC Circuits




$$\epsilon = \epsilon_{\text{max}} \sin \omega t$$

Kirchoff $\epsilon - IR = 0$

$$I = \frac{\epsilon}{R} = \frac{\epsilon_{\text{max}} \sin \omega t}{R}$$




INSTANTANEOUS
Power
Dissipation
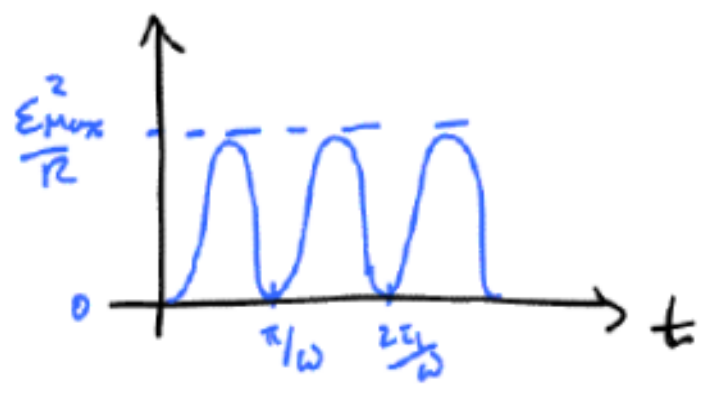
$$P = IV = I\epsilon = \frac{\epsilon_{\text{max}}^2}{R} \sin^2 \omega t$$




$$\overline{\sin^2 \theta} \rightarrow \frac{1}{2}$$
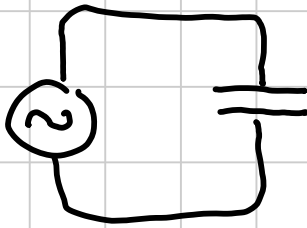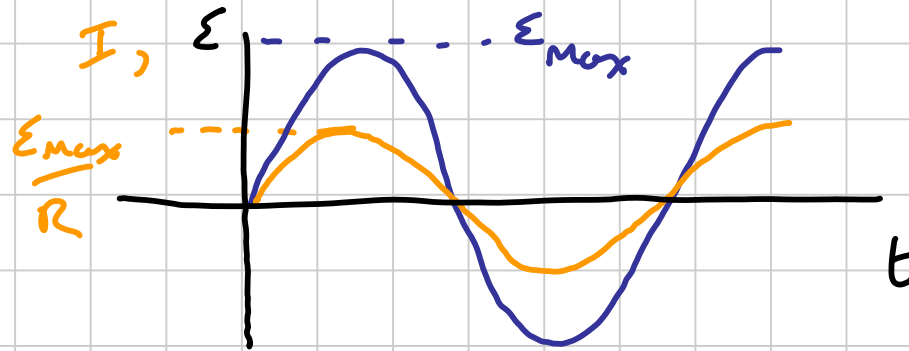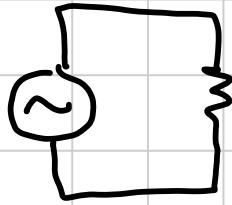
$$\text{AVE POWER} \quad \overline{P} = \frac{\epsilon_{\text{max}}^2}{2R}$$



$$Q = C\epsilon = C\epsilon_{max} \sin \omega t$$
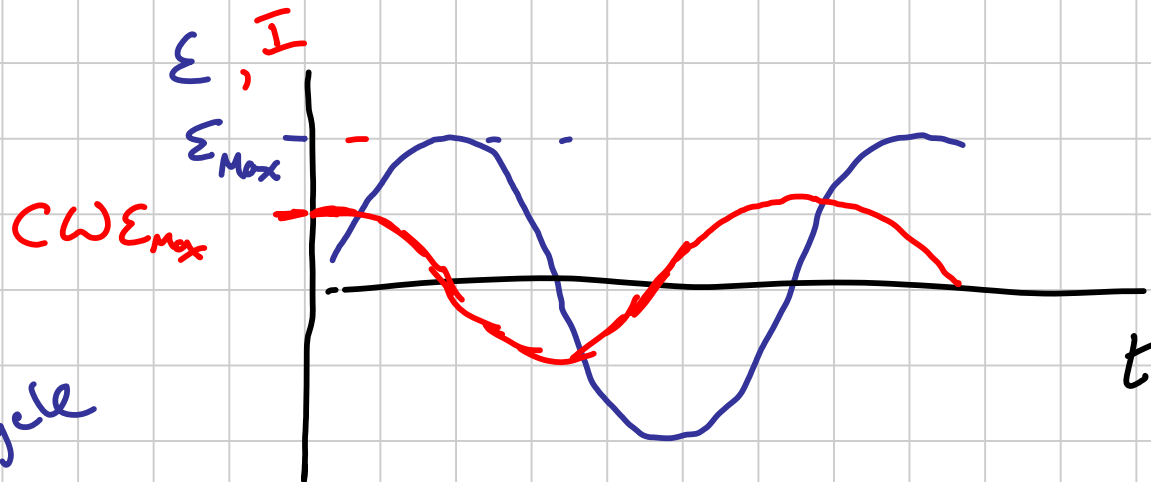
$$I = \frac{dQ}{dt} = C\omega\epsilon_{max} \cos \omega t$$



I "leads" ϵ
by $\frac{1}{4}$ cycle

$$V = IR$$

$$I = \frac{V}{R}$$

$$\frac{1}{\omega C} I = I_{\max} \cos \omega t$$


plays role of resistance

in Capacitive

AC circuit

≡ Capacitive


Reactance ≡ X_c

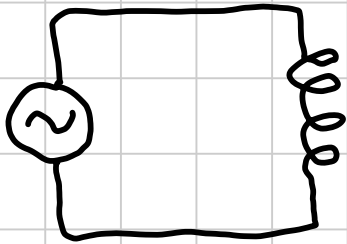

$$\mathcal{E} - L \frac{dI}{dt} = 0$$


$$\frac{dI}{dt} = \frac{\mathcal{E}_{\max} \sin \omega t}{L}$$
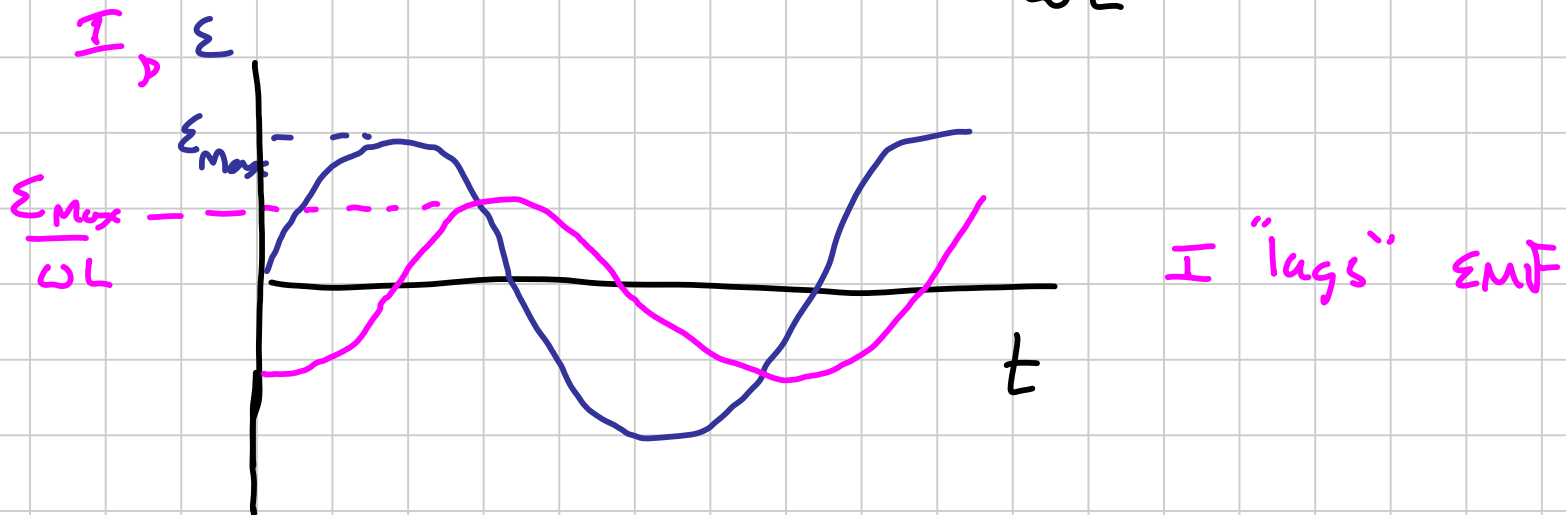
$$I = - \frac{\mathcal{E}_{\max}}{\omega L} \cos \omega t$$



ωL acts like resistance in inductive AC circuit

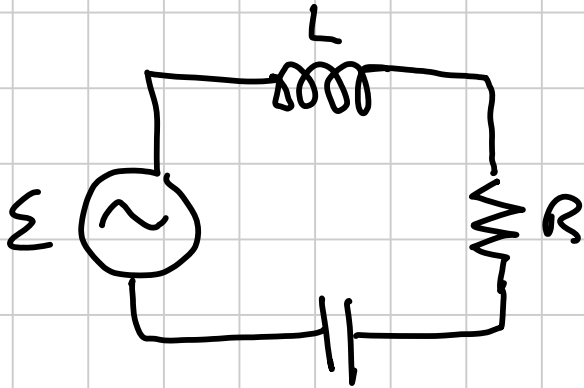$\omega L \equiv X_L$
Inductive Reactance



LRC circuit

$$\varepsilon = \varepsilon_{\max} \sin \omega t$$


Assume

$$I = I_{\max} \sin(\omega t + \phi)$$

?
What are these?

Graph to illustrate
relative phases and signs
of EMF terms

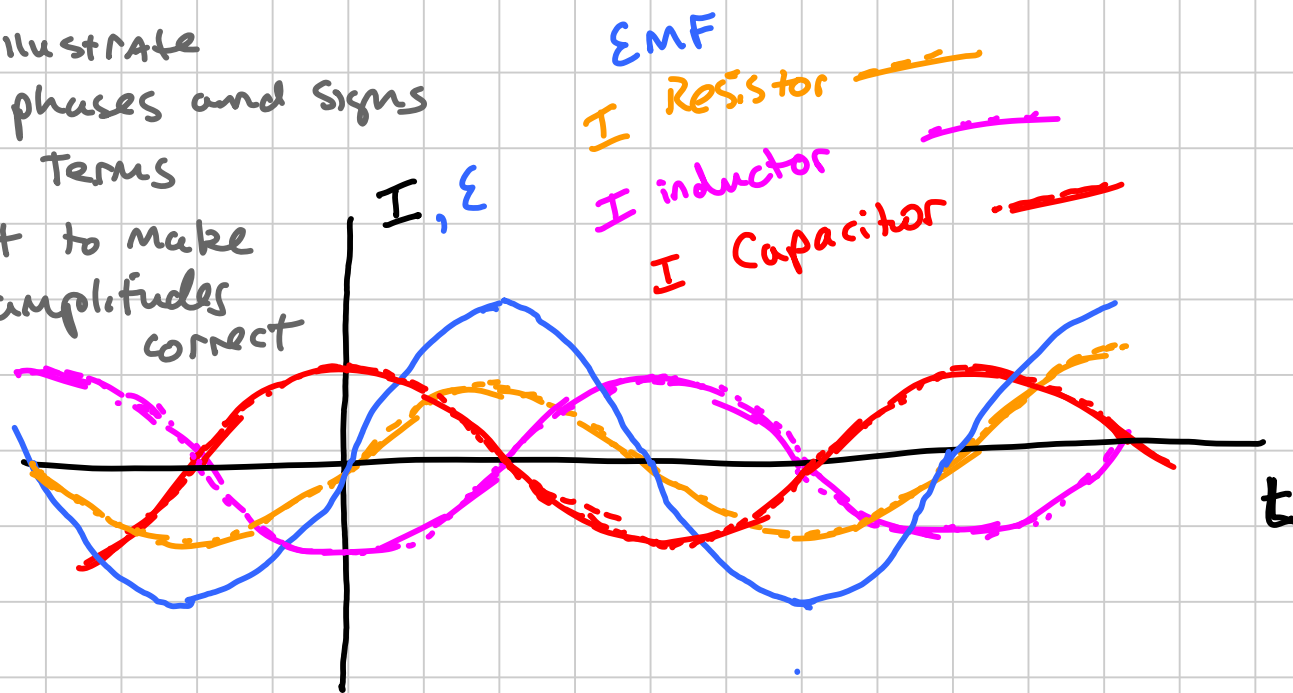No attempt to make
relative amplitudes
correct



$$\epsilon = \underbrace{\Delta V_R}_{R I_{\max} \sin(\omega t + \phi)} + \underbrace{\Delta V_C}_{X_C I_{\max} \cos(\omega t + \phi)} + \underbrace{\Delta V_L}_{-X_L I_{\max} \cos(\omega t + \phi)}$$

often people use a graphical analysis
with I and ϵ vectors rotating
in a plane \rightarrow phasors [see Ohanian p.1047]

I think earlier edition of Ohanian did a nice treatment
using Math + Trig I/O's \rightarrow get

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$I_{\max} = \frac{E_{\max}}{\sqrt{R^2 + (X_L - X_C)^2}}$$

≡ Impedance ≡ Z

⊂ → Frequency ω

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$


$$\omega \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

Plays
Role
of
Resistance
in LRC
Circuit

$$Z = \sqrt{R^2 + \left(\frac{1}{\sqrt{Lc}} - \frac{\sqrt{Lc}}{c} \right)^2}$$

0

Minimize Z
Maximize I

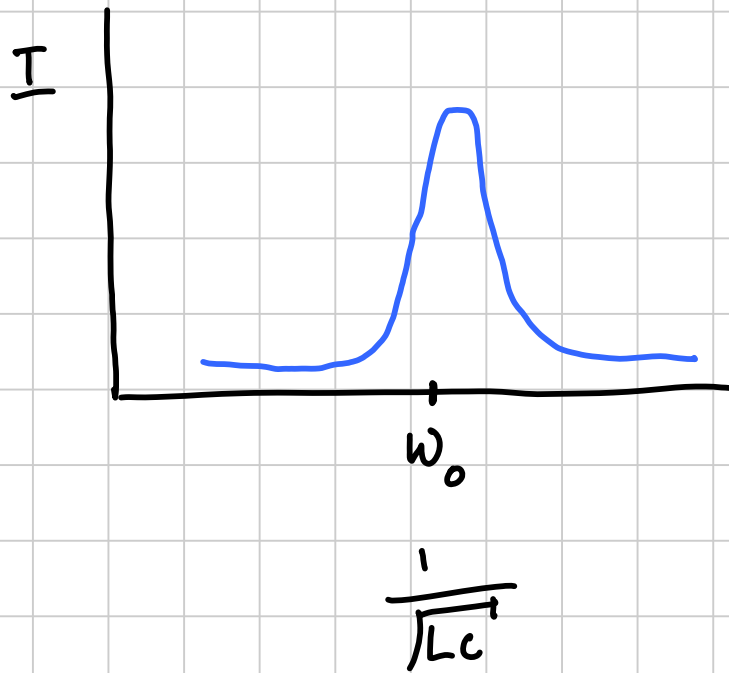

Resonance