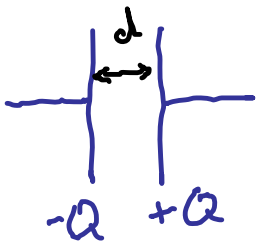


## Physics 142 - October 2, 2014

- Exam 1 next Tuesday - here - During lecture  
organizational questions/issues?
- Q + A session Monday at 5:30 B + L 109
- Workshops go on as usual next week  
... as do problem sets  
both shorter than usual

Last Time


Capacitance of parallel plate capacitor



$$C = \frac{\epsilon_0 A}{d}$$


geometry only  
Different for different systems

Capacitors in parallel

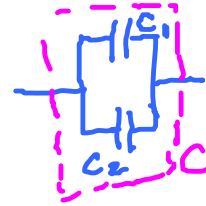

$$C = \sum_i C_i$$

Capacitors in series

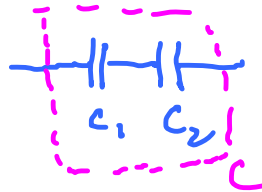

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

Energy stored in a capacitor

$$U = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} QV$$

Energy density in Electric field

$$u_E = \frac{\epsilon_0}{2} |E|^2$$



$$u_E = \frac{\epsilon_0}{2} |E|^2$$



if know  $\vec{E}$

$$U = \int_{Vol} u_E dv$$
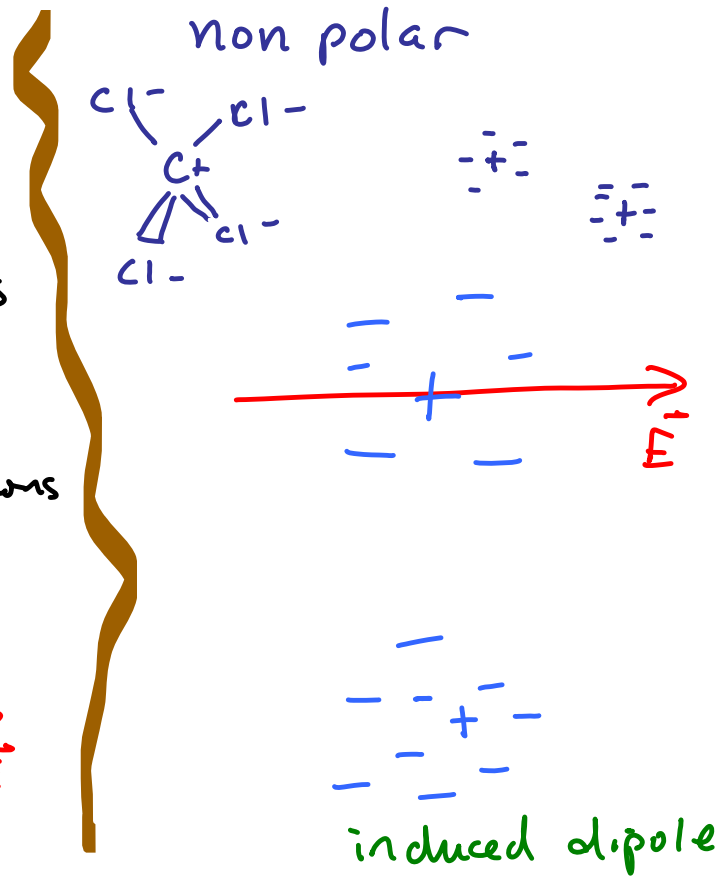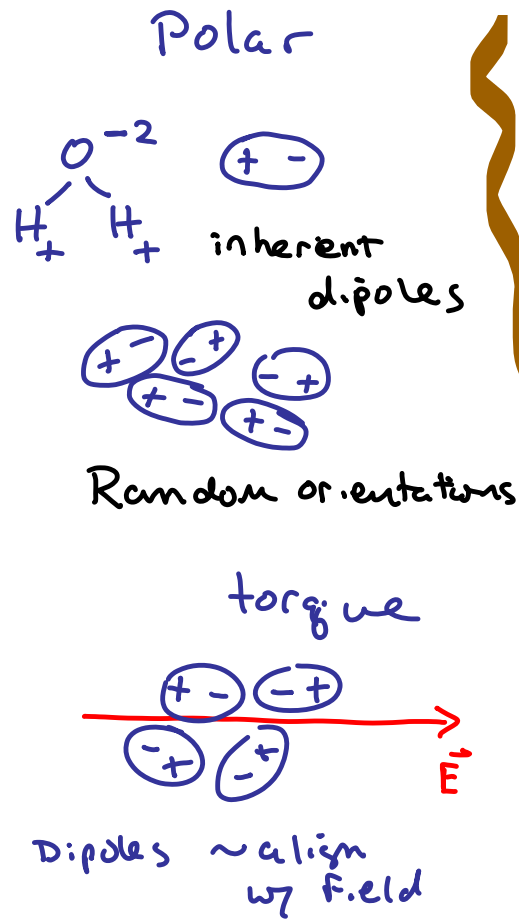
# $\vec{E}$ in materials - dielectric (nonconductor)



(linear) Dielectrics

$\vec{E}$  in materials

linear

$$\vec{E} \propto \vec{E}_0$$

$$\vec{E} = \frac{\vec{E}_0}{\kappa}$$

$\kappa \equiv$  Dielectric constant (varies by material)


$\kappa > 1$

$$\kappa_{\text{water}} = 80.4$$

$$\kappa_{\text{air}} = 1.00054$$


$$\kappa_{\text{vacuum}} = 1$$

$$\text{oil} = 4.5$$

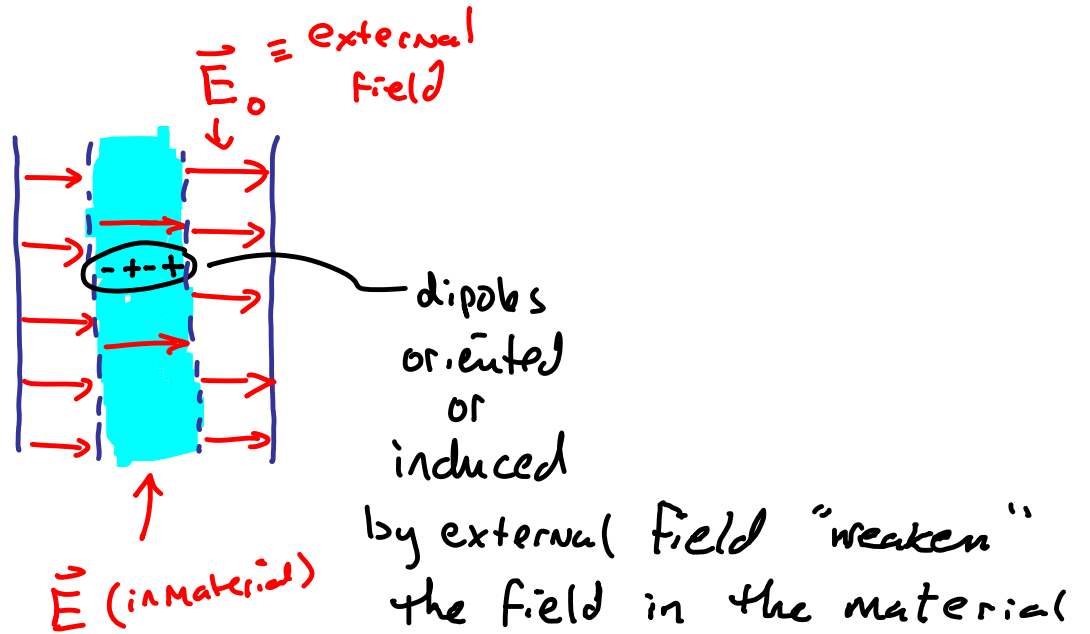

$$\kappa \epsilon_0 \equiv \epsilon$$

↑  $\equiv$  Permittivity

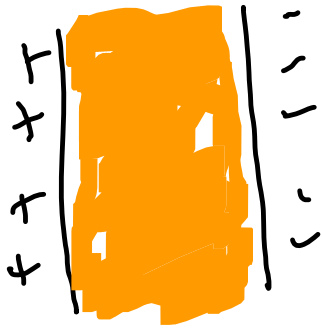

$$\vec{E}_0 = \frac{\sigma}{\epsilon_0}$$

$$\vec{E} = \frac{\vec{E}_0}{\kappa} = \frac{\sigma}{\kappa \epsilon_0} = \frac{\sigma}{\epsilon}$$

||

$$Q = CV$$


No dielectric                      with dielectric

$$V \longrightarrow \frac{V}{K}$$

$$C \longrightarrow Kc = K \frac{\epsilon_0 A}{d} = \frac{\epsilon A}{d}$$


$Q = C' \frac{V}{K} \rightarrow \left[ \frac{Q}{V} \right] K = C'$

Currents and resistance

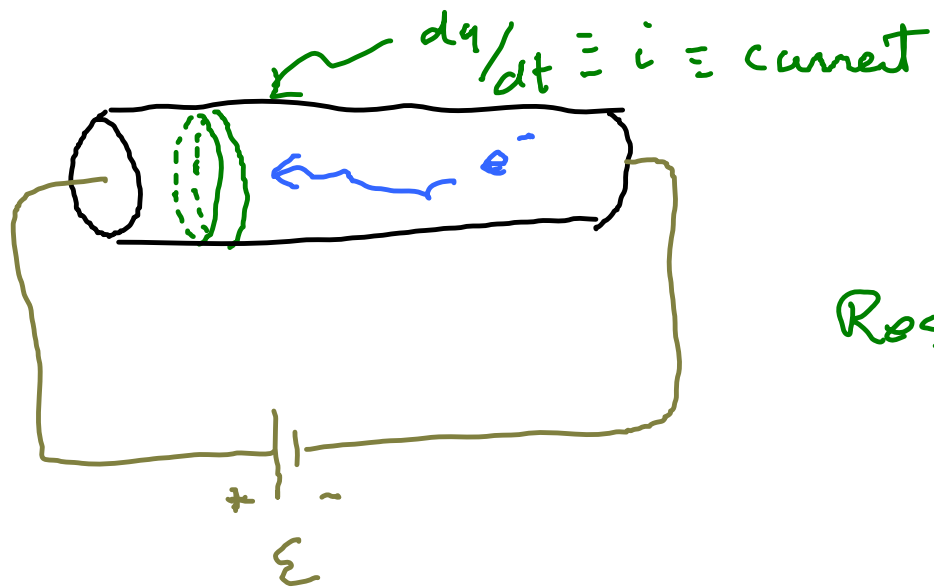

$$\frac{dq}{dt} \equiv i \equiv \text{current}$$

+ Current flow  
is direction  
+ charge would move

Resistance impedes electrons  
as they look for lower 

$$i \equiv \frac{dq}{dt} \quad \text{in units of} \quad \frac{\text{Coulombs}}{\text{sec}} \equiv \text{Ampere}$$



$$i \propto V$$

$$V = iR$$

Resistance  
Ohm's Law

units  
Ohm's



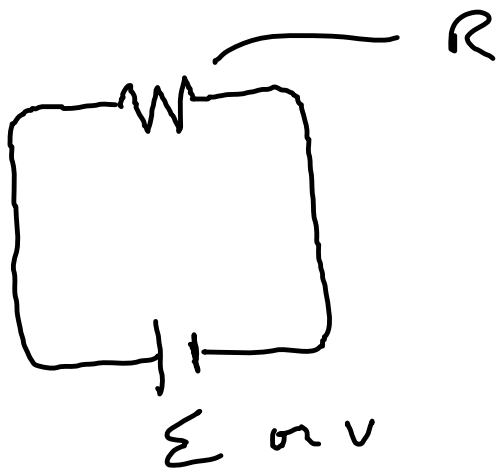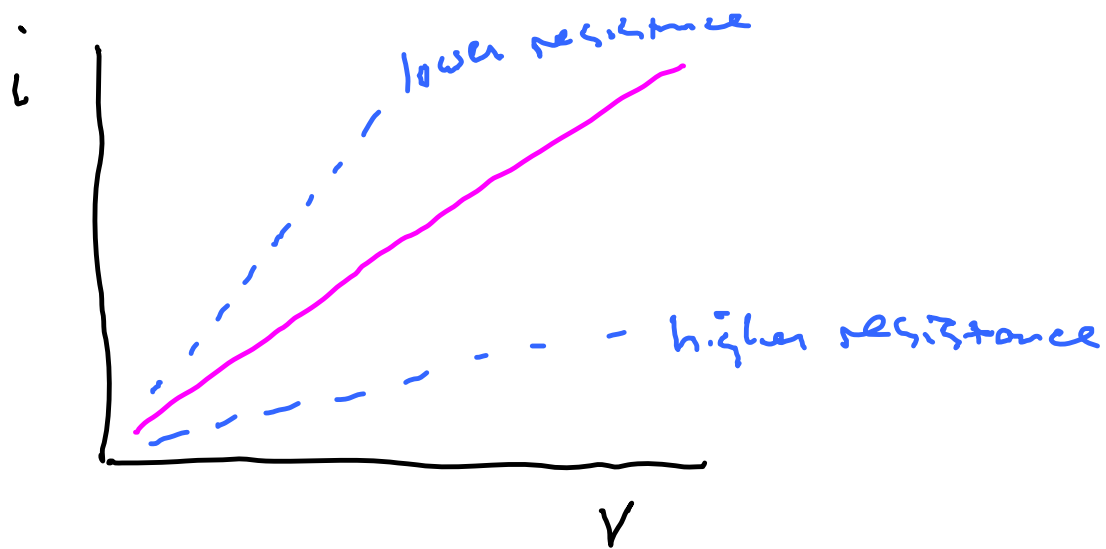


$$V = \frac{\omega}{g}$$

$$\omega = gV$$

$$\frac{d\omega}{dt} = \frac{dg}{dt} V = iV \equiv \text{Power} = P$$

$$P = iV = \frac{V^2}{R} = i^2 R$$

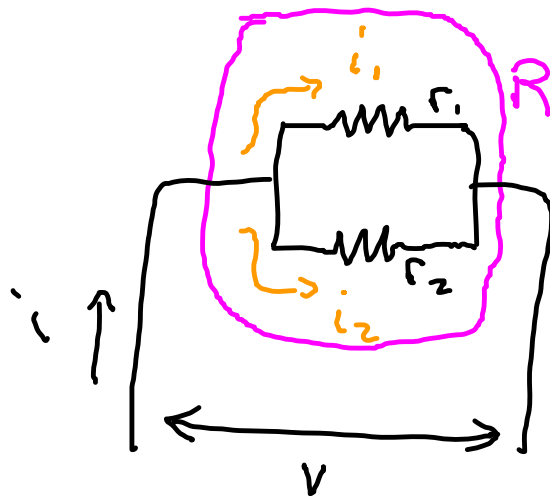

Resistors in parallel

$$V = iR$$

$$V = i_1 r_1$$


$$V = i_2 r_2$$

$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{r_1} + \frac{V}{r_2}$$

$$\frac{1}{R} = \sum_i \frac{1}{r_i}$$
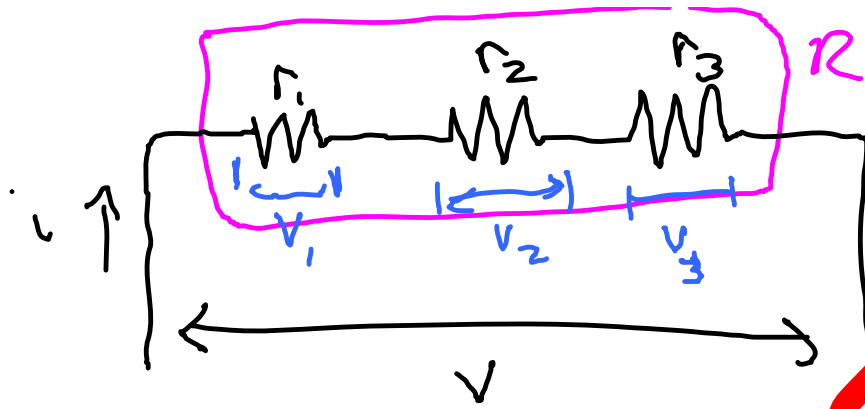
$$\frac{1}{R} = \frac{1}{r_1} + \frac{1}{r_2}$$



$$R = \sum_i r_i$$

## Resistors in series

$$V = iR$$

$$V = V_1 + V_2 + V_3$$

$$iR = ir_1 + ir_2 + ir_3$$

$$R = r_1 + r_2 + r_3$$

Parallel

Capacitors

$$C = \sum_i C_i$$

Resistors

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

Series

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

$$R = \sum_i R_i$$

Convention [told This is opposite that of ECE 210]  
↳ no matter if consistent

Choose currents in each branch (arbitrary)  
Sum  $\Delta V$  across each circuit component as you go  
around an imaginary closed loop in the circuit

$\Delta V -$  if   $\mathcal{E} +$  if 

$\Delta V +$  if   $\mathcal{E} -$  if 

Get Negs, N unknowns and Solve

Tedious  $\rightarrow$  must be careful and consistent  
↳ Conventions and Signs

use only independent loops