

Physics 142 - October 9, 2014


- Hope to have EXAM graded + Back to you NEXT week
- Will send email about "projects" soon

Last Time

electrons impeded
as they
look for 


$$V = iR$$

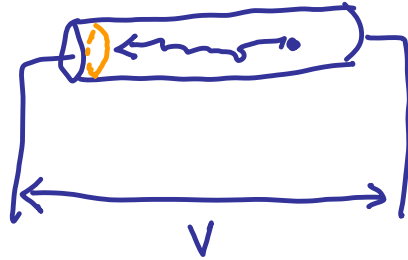R in Ohms, R depends on material + geometry



$$i = \frac{dq}{dt}$$

i in Amperes

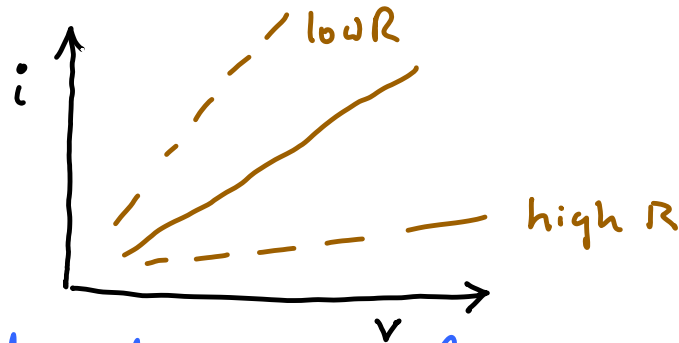



André Marie Ampère
(1775 - 1836)

French { mathematician
 { chemist
 { physicist

$$V = IR$$

ohm's Law



Georg
Ohm

RESISTANCE
Measured
in
Ohms

$$1 \text{ Ohm} = 1 \frac{\text{volt}}{\text{Ampere}}$$

Ω

1789-1854

German

Energy lost
to resistance
↳ heat

$$P = iV = \frac{V^2}{R} = i^2 R$$

"Resistive heating"

Resistors

Parallel

$$\frac{1}{R} = \sum \frac{1}{r_i}$$


Series

$$R = \sum_i r_i$$


Capacitors

$$C = \sum_i c_i$$

$$\frac{1}{C} = \sum_i \frac{1}{c_i}$$

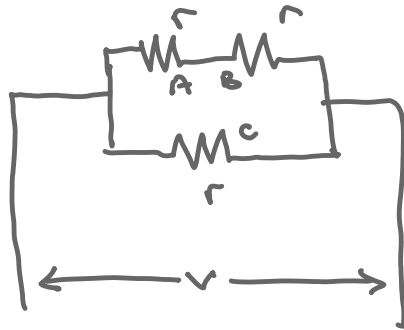

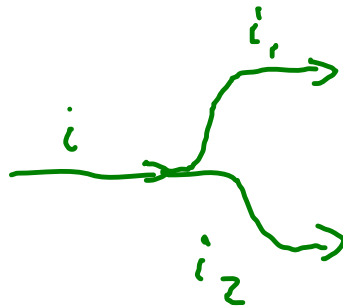3 lightbulbs Arranged
as shown
order the brightness of the
Bulbs



$$P = i^2 r$$

Top $V = i(2r)$


$$i_t = \frac{V}{2r}$$

$$P = \frac{V^2}{4r^2} r \left] \frac{V^2}{4r}\right.$$

Bot $V = i r$

$$i_b = \frac{V}{r}$$



$$P = \frac{V^2}{r}$$

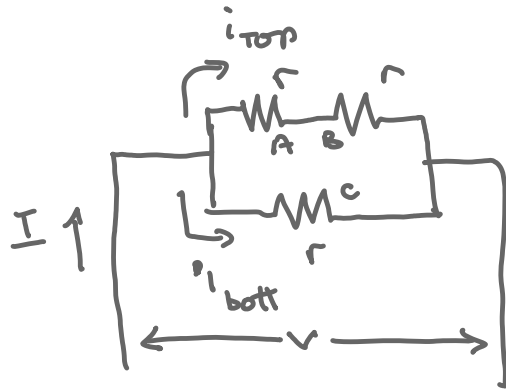

3 lightbulbs Arranged
as shown


What happens to the brightness
of c if bulb A is unscrewed

STAYS The SAME
V un changed across C

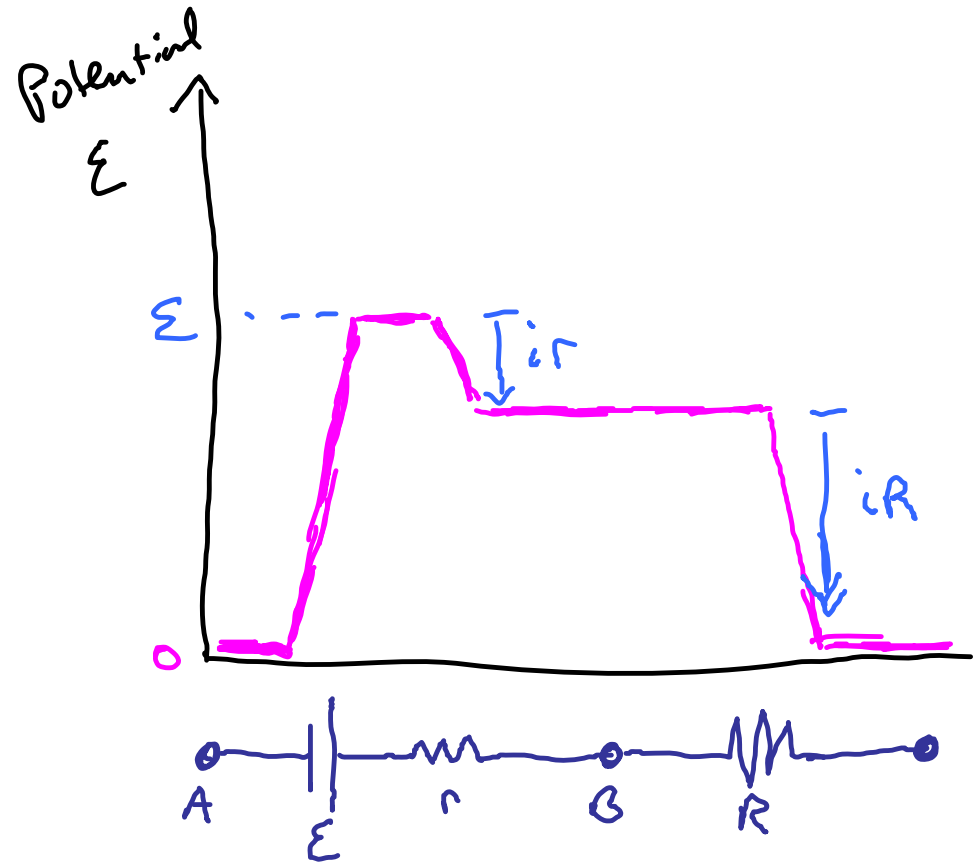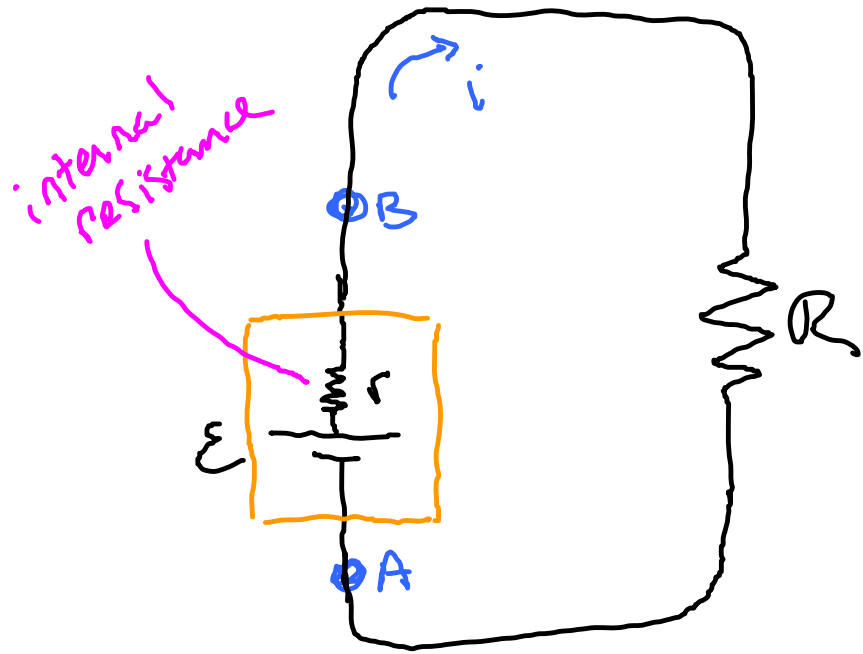



Direct current or DC

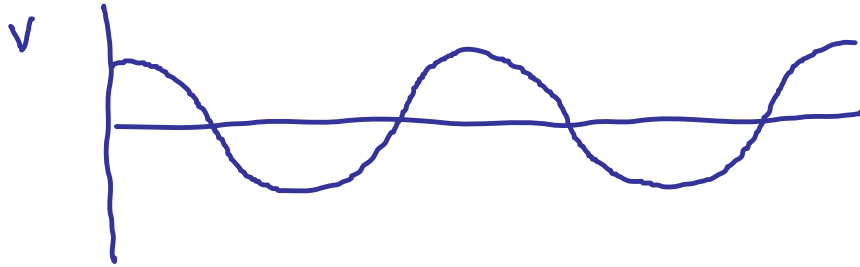

Alternating
current
AC

Kirchoff's Rules

① $\sum V = 0$ around closed loop

② $\sum i = 0$ at junctions

Apply to independent loops and junctions.

Derive N independent eqns
can solve for N indep. unknowns.

guts + Conventions + Consistency

determined Kirchoff's
Laws at age 21

played for ZZ Top
in the early days



GUSTAV ROBERT KIRCHOFF
Germany (1824-1887)



Convention [told This is opposite that of ECE 210]
↳ no matter if consistent

Choose currents in each branch (arbitrary)
Sum ΔV across each circuit component as you go
around an imaginary closed loop in the circuit


$\Delta V -$ if  $\mathcal{E} +$ if 

$\Delta V +$ if  $\mathcal{E} -$ if 

Get N eqns, N unknowns and solve

Tedious \rightarrow must be careful and consistent
↳ Conventions and signs

use only independent loops

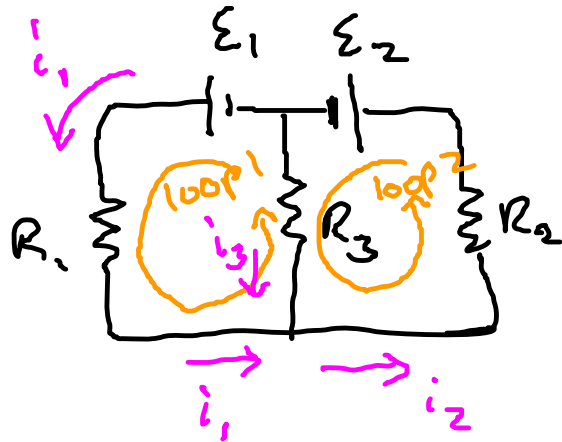

know ϵ_1, ϵ_2

R_1, R_2, R_3

Solve for current
through circuit

Current conservation

1 indep. equation

$$i_1 + i_3 = i_2 \quad \text{I}$$

$\sum V = 0$


loop 1

$$\epsilon_1 - i_1 R_1 + i_3 R_3 = 0 \quad \text{II}$$


loop 2


$$-\epsilon_2 - i_3 R_3 - i_2 R_2 = 0 \quad \text{III}$$

Direct Current

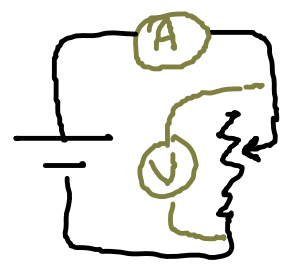

RC circuit

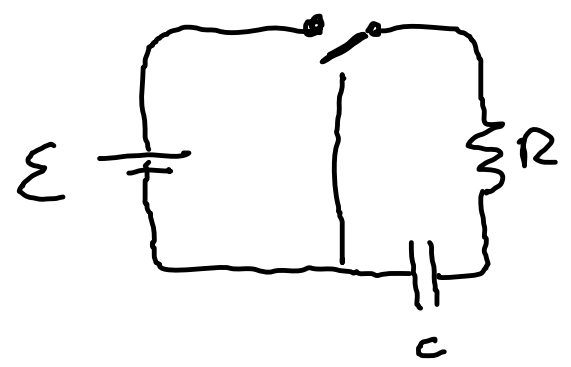

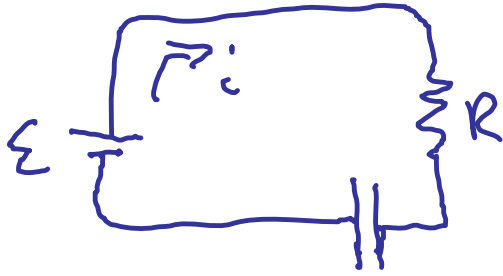

differential
Equation

$$\sum \Delta V = 0$$

$$\mathcal{E} - iR - \frac{q}{C} = 0$$

$$\mathcal{E} - \frac{dq}{dt}R - \frac{q}{C} = 0$$

$$q(t) = C\mathcal{E}(1 - e^{-t/RC})$$