

## Physics 142 - November 6, 2014

- Meet w/ your project group
- Begin to formulate a plan
- Contact person to contact me and set up a time for group to meet w/ me

LAST TIME



$$\phi_m = Li$$


$L \equiv$  CONSTANT OF SELF-INDUCTANCE

$$\mathcal{E} = -\frac{d\phi_m}{dt} = -L \frac{di}{dt}$$



units Henrys

$$\mathcal{E} = -L \frac{di}{dt}$$

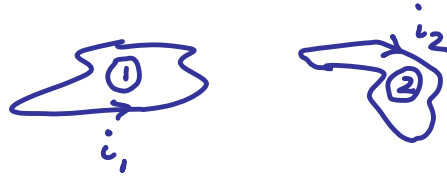

$$\phi_{m(2)} = M i_{(1)}$$

$$\phi_{m(1)} = M i_{(2)}$$

SAME "M" Cross-Talk dictated by Geometry

$M \equiv$  CONSTANT OF MUTUAL INDUCTANCE

$$\mathcal{E}_{(2) \text{ by } (1)} = -M \frac{di_{(1)}}{dt}$$

$$\mathcal{E}_{(1) \text{ by } (2)} = -M \frac{di_{(2)}}{dt}$$

unless problem is specifically about mutual inductance ... usually treat inductance in a circuit as self-inductance

Energy density in the fields:


$U_E = \frac{\epsilon_0 E^2}{2}$	$U_B = \frac{B^2}{2\mu_0}$
----------------------------------	----------------------------

general — says nothing about  
circuits or sources  
or boundary  
conditions!


Energy in Inductor

$$U = \frac{1}{2} L I^2$$

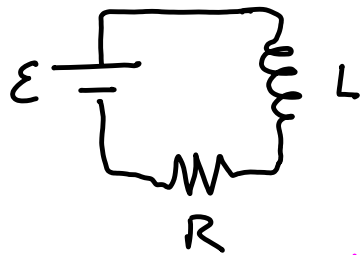similar to  $U_{\text{capacitor}} = \frac{1}{2} C V^2$




LR circuit

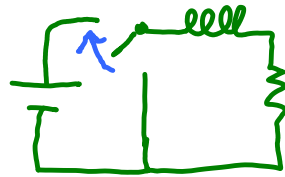


$$\varepsilon - L \frac{di}{dt} - iR = 0$$

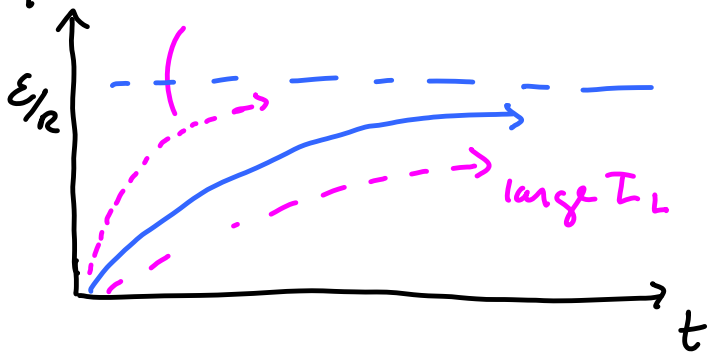
small  $\tau_L$   $i = \frac{\varepsilon}{R} (1 - e^{-tR/L}) = \frac{\varepsilon}{R} (1 - e^{-t/\tau_L})$



Induction time  
constant  
||  
 $\frac{L}{R} = \tau_L$

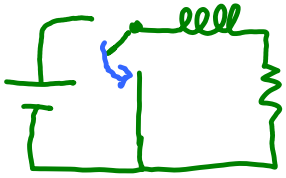


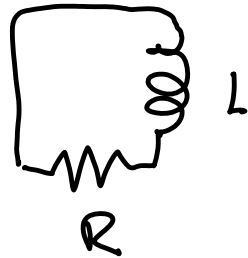At some time  $t$  later, Short  $L$  across  $R$




$$0 = iR + L \frac{di}{dt}$$
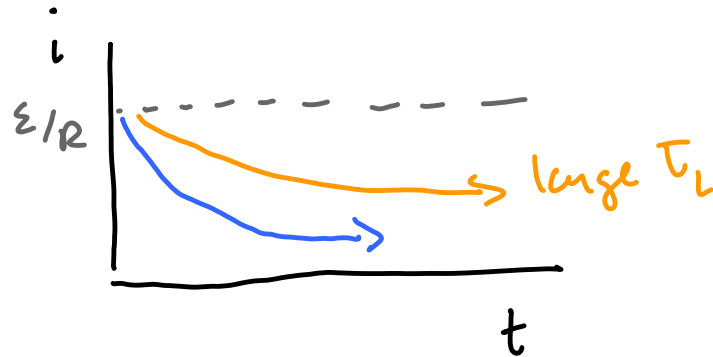
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L}$$




DEMO

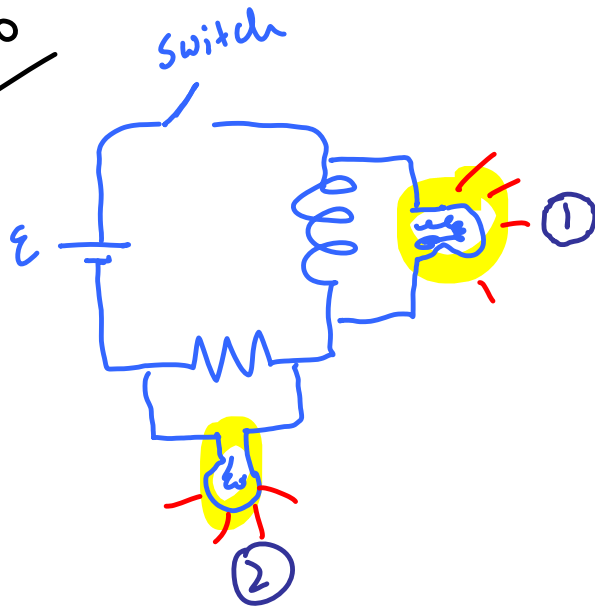

close switch ... what happens ?

LC circuit

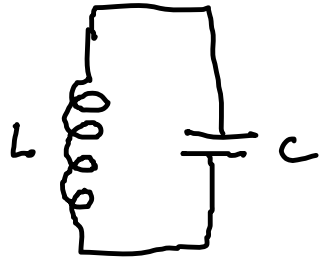

Fully charged capacitor

at  $t=0$

$R \rightarrow 0$

$$U = U_E + U_B = \frac{q^2}{2C} + \frac{Li^2}{2}$$

$$0 = \frac{dU}{dt} = \frac{dU_E}{dt} + \frac{dU_B}{dt} = \frac{2q}{2C} \frac{dq}{dt} + \frac{L2i}{2} \frac{di}{dt}$$

$$0 = L \frac{di}{dt} + \frac{q}{C}$$

$\frac{dq}{dt}$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

SHM  
in  
 $q(t)$

$$\omega^2 = \frac{1}{LC}$$

$$q(t) = Q \cos(\omega t + \phi)$$

$$i(t) = \frac{dq(t)}{dt} = -\omega Q \sin(\omega t + \phi)$$

$$0 = \frac{d^2 q}{dt^2} + \frac{1}{LC} q$$

SHM!



Look at energy flow

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$


E stored in  
Capacitor  
or  
E field


$$U_B = \frac{1}{2} L i^2 = \frac{1}{2} L Q^2 \omega^2 \sin^2(\omega t + \phi)$$

E stored in  
Inductor  
or B field


$$\omega^2 = \frac{1}{LC} = \frac{1}{2} \frac{Q^2}{LC} = \frac{1}{2} \frac{Q^2}{C}$$

## LC Oscillations

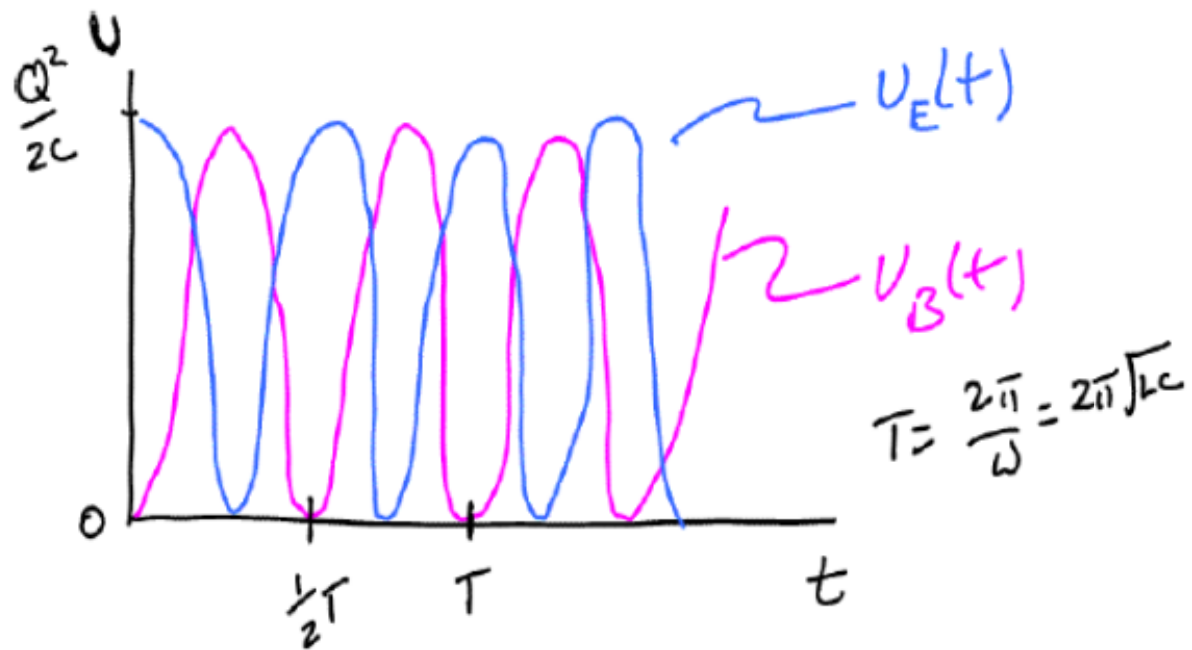

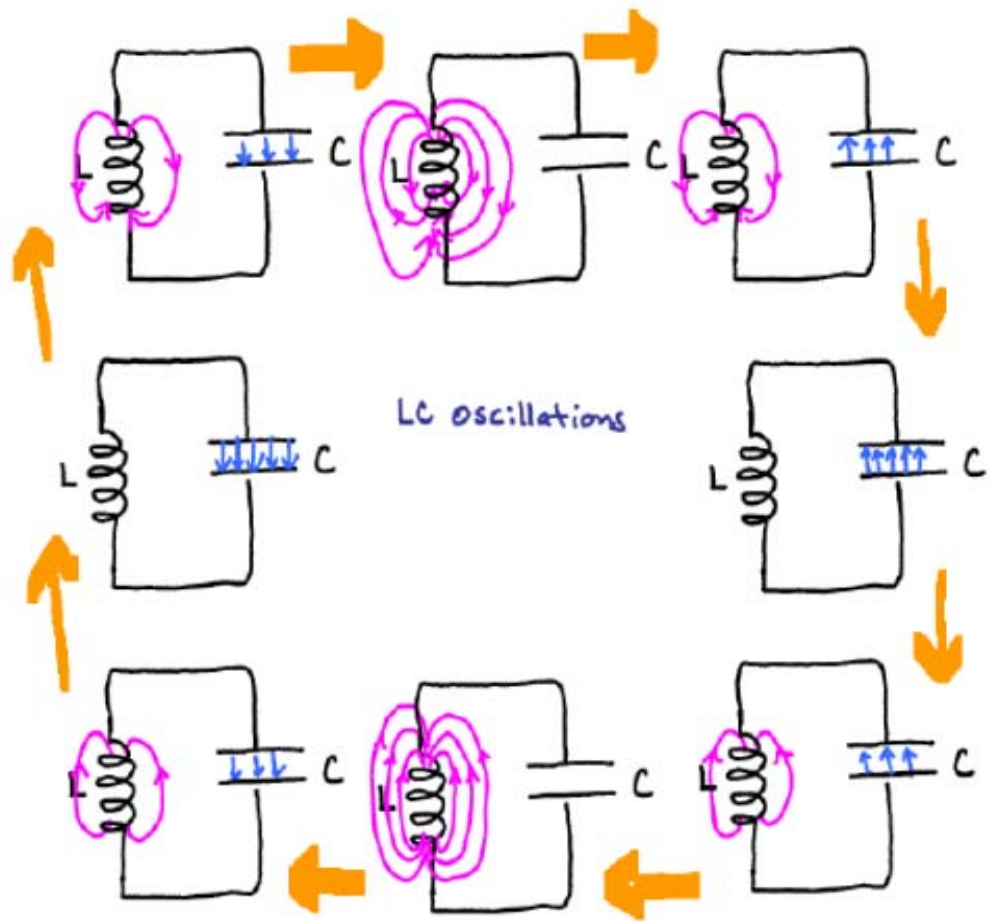

# AC circuits

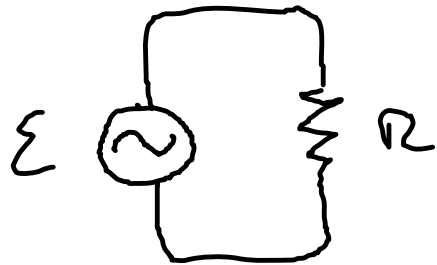


$$\mathcal{E} = \mathcal{E}_{\text{max}} \sin(\omega t)$$

$$\mathcal{E} - IR = 0$$

$$I = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{\text{max}}}{R} \sin(\omega t)$$



INSTANTANEOUS  
POWER
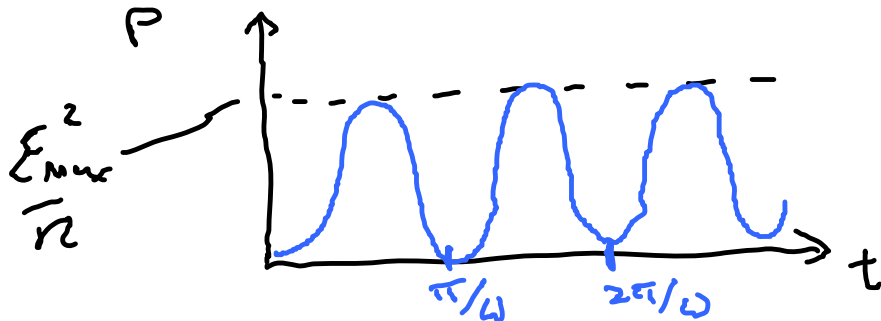
$$P = IV = I\mathcal{E} = \frac{\mathcal{E}_{\text{max}}^2}{R} \sin^2(\omega t)$$




$$\overline{\sin^2 \theta} \rightarrow \frac{1}{2}$$
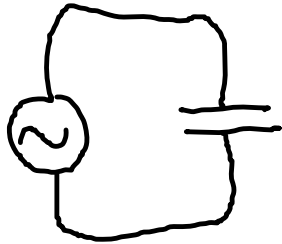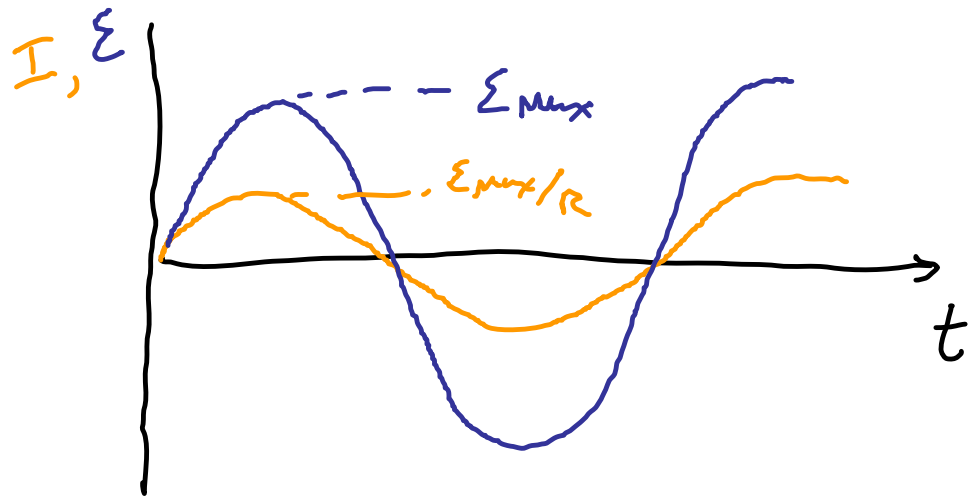
$$\text{Ave Power} = \overline{P} = \frac{\mathcal{E}_{\text{max}}^2}{2R}$$



$$Q = C\epsilon = C\epsilon_{max} \sin \omega t$$
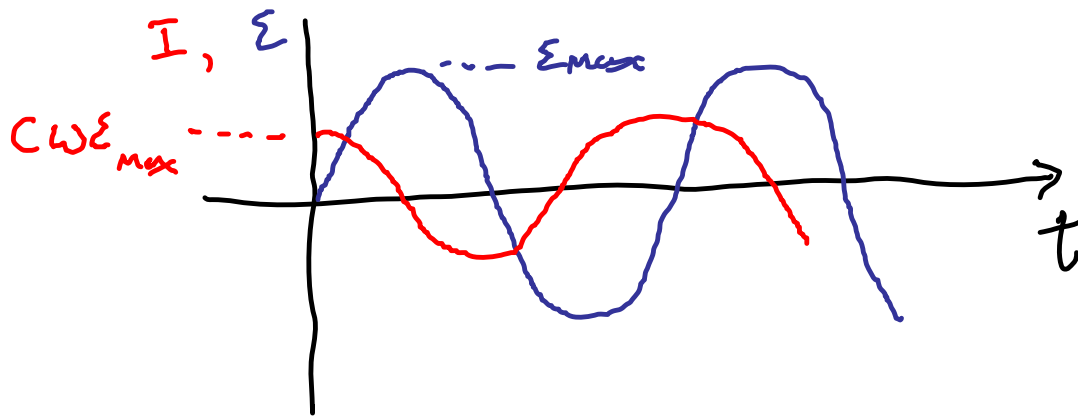
$$I = \frac{dQ}{dt} = C\omega \epsilon_{max} \cos \omega t$$



$I$  "leads"  $\epsilon$   
by  $\frac{1}{4}$  cycle

$$V = IR$$


$$I = \frac{\epsilon}{R}$$

$$I \left( \frac{1}{\omega C} \right) = \epsilon_{max} \cos \omega t$$

$\equiv$  Capacitive  
Reactance  $\equiv X_c$

Think of this as a "resistance"  
in capacitive  
AC circuit

## Inductive AC circuit

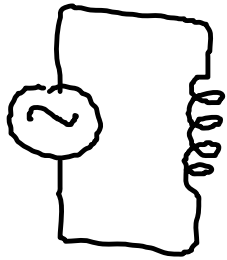


$$\Sigma - L \frac{di}{dt} = 0$$

$$\Sigma = \Sigma_{\max} \sin \omega t$$

$$\Sigma_{\max} \sin \omega t = L \frac{di}{dt}$$

$$I = - \frac{\Sigma_{\max}}{\omega L} \cos \omega t$$
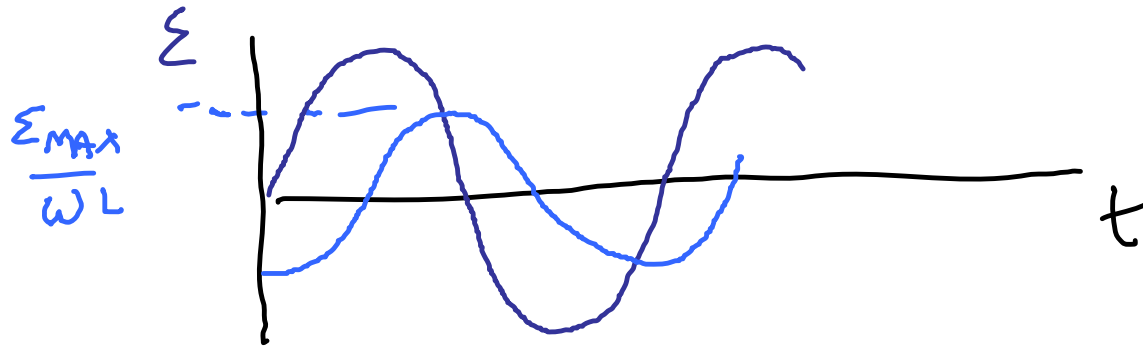
$$\omega L I = - \Sigma_{\max} (\cos \omega t)$$



$\omega L$  acts like resistance  
in Inductive AC circuit

$\omega L \equiv X_L \equiv$  Inductive reactance