

S11 PHY114 Problem Set 4

S. G. Rajeev

Feb 16 2011

Due Monday 21 Feb 2011

1. An isolated capacitor C_1 carries a charge Q_0 . It is then connected by conducting wires to a second capacitor C_2 which was previously uncharged. What is the charge on each capacitor now?

2.

(i) How much energy is needed to transfer a small amount of charge dQ from one plate of a capacitor to the other, if the potential difference between the plates is V ?

(ii) By thinking of the charge on the capacitor as built up from zero to Q in small increments, what is the energy of a capacitor with charge Q ? The capacitance C is constant. Express this energy in terms of C and the final voltage V .

3. Recently there have been advances in developing capacitors with very large capacitances of thousands of Farads. They also have a small internal resistance.

(i) How much electrical energy is stored in a 1200 Farad capacitor charged to 12 Volts?

(ii) It is found that the time it takes for half the charge in this capacitor to be discharged is 0.52s. What is the resistance ?

4. Using the formula for the energy of a parallel plate capacitor, derive a formula for the energy density of the electric field. Assume that the capacitor is made of two parallel conducting plates, each of area A , separated by at a distance d of empty space.

5. A $2.8k\Omega$ and $3.7k\Omega$ resistor are connected in parallel; this combination is then connected in series with a $1.8k\Omega$ resistor. What is the maximum voltage that can be applied across this network if the power dissipated in any one resistor cannot exceed one Watt ?