

Energy stored in an inductor

Turn current on from zero to I in an inductor. To drive the current one must do work against the induced emf of the inductor

$$dW = \mathcal{E} I dt = L I \frac{dI}{dt} dt = \frac{1}{2} L \frac{d(I^2)}{dt} dt$$

$$W = \int dW = \int dt \frac{1}{2} L \frac{d(I^2)}{dt} = \frac{1}{2} L I^2$$

Energy stored in inductor with constant current I flowing is

$$U_L = \frac{1}{2} L I^2$$

(compare to energy stored in capacitor with constant voltage across it. $U_C = \frac{1}{2} C V^2$)

Consider now a long solenoid of length l and cross sectional area A . We previously computed its self inductance

$$L = \frac{4\pi}{c^2} A N^2 l \quad N = \# \text{ turns/length}$$

$$\text{so } U_L = \frac{1}{2} \frac{4\pi}{c^2} A l N^2 I^2$$

$$= \frac{c}{8\pi} \left(\frac{4\pi}{c} N I \right)^2 A l = \frac{1}{8\pi} B^2 (\text{Vol})$$

This is an example of a more general result which we will not prove:


The energy stored in a magnetic field in some volume of space V is

$$U_B = \frac{1}{8\pi} \int_V dV B^2$$

compare to energy stored in an electric field

$$U_E = \frac{1}{8\pi} \int_V dV E^2$$

Transformers

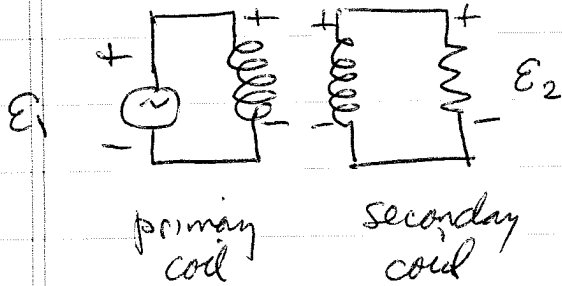

inducting coils configured
so that same magnetic
flux penetrates each
loop of both coils

\mathcal{E}_1 is time varying voltage supply (usually ac source)
 \mathcal{E}_2 is voltage drop across load

primary: $\mathcal{E}_1 - \frac{1}{c} N_1 \frac{d\Phi_1}{dt} = 0 \Rightarrow \mathcal{E}_1 = \frac{1}{c} N_1 \frac{d\Phi_1}{dt}$

Φ_1 is flux through one turn of the coil, N_1 is
total number of turns

secondary: $\mathcal{E}_2 - \frac{1}{c} N_2 \frac{d\Phi_2}{dt} = 0 \Rightarrow \mathcal{E}_2 = \frac{1}{c} N_2 \frac{d\Phi_2}{dt}$

Φ_2 is flux through one turn of the coil,
 N_2 is total number of turns

By construction $\Phi_1 = \Phi_2$ so

$$\boxed{\frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{N_2}{N_1}}$$

if $N_2 > N_1$ then $\mathcal{E}_2 > \mathcal{E}_1$
"step up" transformer
if $N_2 < N_1$ then $\mathcal{E}_2 < \mathcal{E}_1$
"step down" transformer

In an ideal transformer the power delivered to the secondary coil is equal to the power lost in primary coil.

$$\Rightarrow I_1 \varepsilon_1 = I_2 \varepsilon_2$$


↑
power dissipated
in primary coil

↑
power dissipated
in load in secondary coil

$$\Rightarrow \frac{\varepsilon_2}{\varepsilon_1} = \frac{I_1}{I_2}$$

so
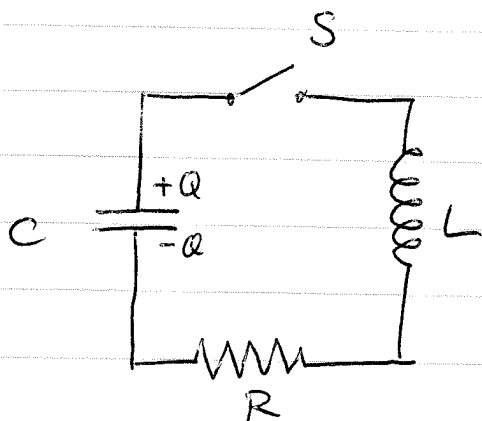
$$\boxed{\frac{I_2}{I_1} = \frac{N_1}{N_2}}$$



Let V be voltage drop across capacitor. $V = \frac{Q}{C}$

When switch S closes, then V will act like an emf driving current I clockwise around loop.

Kirchoff 2nd law

$$\Rightarrow V = L \frac{dI}{dt} + RI$$

Since I results from Q flowing from + plate of capacitor to - plate of capacitor, $I = -\frac{dQ}{dt}$ (as Q decreases, current flows)

$$\text{From } V = \frac{Q}{C} \text{ we have } \frac{dV}{dt} = \frac{1}{C} \frac{dQ}{dt} = -\frac{1}{C} I$$

$$\frac{d^2V}{dt^2} = -\frac{1}{C} \frac{dI}{dt}$$

Substituting in above gives differential eqn for V

$$V = -LC \frac{d^2V}{dt^2} - RC \frac{dV}{dt}$$

$$\text{or } \boxed{\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = 0}$$

just like damped harmonic oscillator

$$m \frac{dx^2}{dt} = -kx - \alpha \frac{dx}{dt} \rightarrow \frac{d^2x}{dt^2} + \frac{\alpha}{m} \frac{dx}{dt} + \frac{k}{m} x = 0$$

\uparrow \uparrow \uparrow
 ma Hook's law friction
 force from spring

Solution is a damped harmonic oscillation

Try

$$V(t) = A e^{-\alpha t} \cos \omega t$$

$$\frac{dV}{dt} = -\alpha A e^{-\alpha t} \cos \omega t - \omega A e^{-\alpha t} \sin \omega t$$

$$\frac{d^2V}{dt^2} = +\alpha^2 A e^{-\alpha t} \cos \omega t + \alpha \omega A e^{-\alpha t} \sin \omega t + \alpha \omega e^{-\alpha t} \sin \omega t - \omega^2 A e^{-\alpha t} \cos \omega t$$

plug in

$$(\alpha^2 - \omega^2) A e^{-\alpha t} \cos \omega t + 2\alpha \omega A e^{-\alpha t} \sin \omega t$$

$$- \frac{R}{L} \alpha A e^{-\alpha t} \cos \omega t - \frac{R}{L} \omega A e^{-\alpha t} \sin \omega t$$

$$+ \frac{1}{LC} A e^{-\alpha t} \cos \omega t = 0$$

$$\Rightarrow \left[\left(\alpha^2 - \omega^2 - \frac{R\alpha}{L} + \frac{1}{LC} \right) \cos \omega t + \left(2\alpha\omega - \frac{R\omega}{L} \right) \sin \omega t \right] A e^{-\alpha t} = 0$$

If above = 0 at all times t , it can only be because coefficients of $\cos \omega t$ and $\sin \omega t$ terms vanish

$$\begin{cases} \textcircled{1} \Rightarrow (\alpha^2 - \omega^2 - \frac{R\alpha}{L} + \frac{1}{LC}) = 0 \\ \textcircled{2} \Rightarrow (2\alpha\omega - \frac{R}{L}\omega) = 0 \Rightarrow \boxed{\alpha = \frac{R}{2L}} \end{cases}$$

sub into ①

$$\frac{R^2}{4L^2} - \omega^2 - \frac{R^2}{2L^2} + \frac{1}{LC} = 0$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{4L^2}$$

$$\boxed{\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}$$

ω real $\Rightarrow \frac{1}{LC} > \frac{R^2}{4L^2} \Rightarrow$ weak damped circuit

Note, if $R=0$, then no dissipation: $\alpha=0$, $\omega = \sqrt{\frac{1}{LC}}$
we have pure harmonic oscillation with freq ω

$$v(t) = V_0 \cos \omega t$$

~~Addy the resistor provide.~~

$$I(t) = -C \frac{dV}{dt} = CV_0 \omega \sin \omega t$$

energy is oscillating between capacitor and inductor
ie between electric field and magnetic field energy


energy capacitor $U_C = \frac{1}{2} CV^2 = \frac{1}{2} CV_0^2 \cos^2 \omega t$

energy inductor $U_L = \frac{1}{2} LI^2 = \frac{1}{2} L C^2 V_0^2 \omega^2 \sin^2 \omega t$

using $\omega^2 = \frac{1}{LC}$, $U_L = \frac{1}{2} CV_0^2 \sin^2 \omega t$

$$\begin{aligned} U_L + U_C &= \frac{1}{2} CV_0^2 (\cos^2 \omega t + \sin^2 \omega t) \\ &= \frac{1}{2} CV_0^2 \quad \text{constant in time} \end{aligned}$$

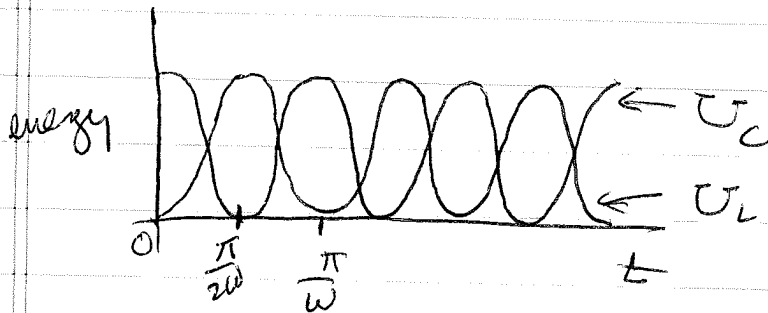Just like energy oscillates between kinetic and potential in the harmonic oscillator



Note: our solution had U_C max at $t=0$.
 But we could always shift the time scale
 $t' = t + t_0$, so $t = t' - t_0$, to get
 solution

$$V(t) = V_0 e^{-\alpha t'} e^{\alpha t_0} \cos(\omega t' - \omega t_0)$$

$$V(t) = V_0' e^{-\alpha t'} \cos(\omega t' - \delta)$$

$$\delta = \omega t_0$$

$$V_0' = V_0 e^{+\alpha t_0}$$

General solution can have the oscillation
 phase shifted by any amount δ .

$$\cos(\omega t - \delta) = \cos \omega t \cos \delta - \sin \omega t \sin \delta$$

or equivalently be any linear combination of
 cosine and sine.

Adding the resistor causes to dissipate energy
(energy goes into heating up the resistor)


$$\text{Now } V(t) = V_0 \cos \omega t e^{-\alpha t}$$

$$I(t) = -C \frac{dV}{dt} = CV_0 \omega \sin \omega t e^{-\alpha t} + \alpha C V_0 \cos \omega t e^{-\alpha t}$$

$$I(t) = C V_0 \omega \left[\sin \omega t + \frac{\alpha}{\omega} \cos \omega t \right] e^{-\alpha t}$$

we can always write $A \sin \omega t + B \cos \omega t = C \sin(\omega t + \delta)$
 $= C \cos \delta \sin \omega t + C \sin \delta \cos \omega t$
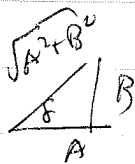
$$\Rightarrow \begin{cases} A = C \cos \delta \\ B = C \sin \delta \end{cases} \Rightarrow \frac{B}{A} = \tan \delta$$



$$\Rightarrow \cos \delta = \frac{A}{\sqrt{A^2 + B^2}} \quad \text{and} \quad C = \frac{A}{\left(\frac{A}{\sqrt{A^2 + B^2}}\right)} = \sqrt{A^2 + B^2}$$

$$\text{So } A \sin \omega t + B \cos \omega t = \sqrt{A^2 + B^2} \sin(\omega t + \delta) \quad \delta = \arctan \frac{B}{A}$$

$$I(t) = C V_0 \omega \sqrt{1 + \left(\frac{\alpha}{\omega}\right)^2} \sin(\omega t + \delta) e^{-\alpha t} \quad \tan \delta = \frac{\alpha}{\omega}$$

$$= C V_0 \sqrt{\omega^2 + \alpha^2} \sin(\omega t + \delta) e^{-\alpha t}$$

$$= C V_0 \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2} + \frac{R^2}{4L^2}} \sin(\omega t + \delta) e^{-\alpha t}$$

$$= \frac{C V_0}{\sqrt{LC}} \sin(\omega t + \delta) e^{-\alpha t}$$

$$U_C = \frac{1}{2} C V_0^2 \cos^2 \omega t e^{-2\alpha t}$$

$$U_L = \frac{1}{2} L I^2 = \frac{1}{2} L \frac{C^2 V_0^2}{LC} \sin^2(\omega t + \delta) e^{-2\alpha t}$$

$$= \frac{1}{2} C V_0^2 \sin^2(\omega t + \delta) e^{-2\alpha t}$$

instead of being $\frac{\pi}{2}$ out of phase, U_C and U_L are now $\frac{\pi}{2} - \delta$ out of phase

Quality factor

$$Q \equiv 2\pi \frac{\text{energy stored at start of one cycle}}{\text{energy lost in one cycle}}$$



The smaller the dissipation from R , the larger Q

energy stored at start of one cycle is $\frac{1}{2} C V_0^2$
 energy stored at end of one cycle is $\frac{1}{2} C V_0^2 e^{-2\alpha T}$
 where $T = \frac{2\pi}{\omega}$ is period of oscillation

$$Q = 2\pi \frac{\frac{1}{2} C V_0^2}{\frac{1}{2} C V_0^2 (1 - e^{-2\alpha T})} = \frac{2\pi}{(1 - e^{-2\alpha T})}$$

For weak damping $\alpha T = \frac{\alpha 2\pi}{\omega} \ll 1$
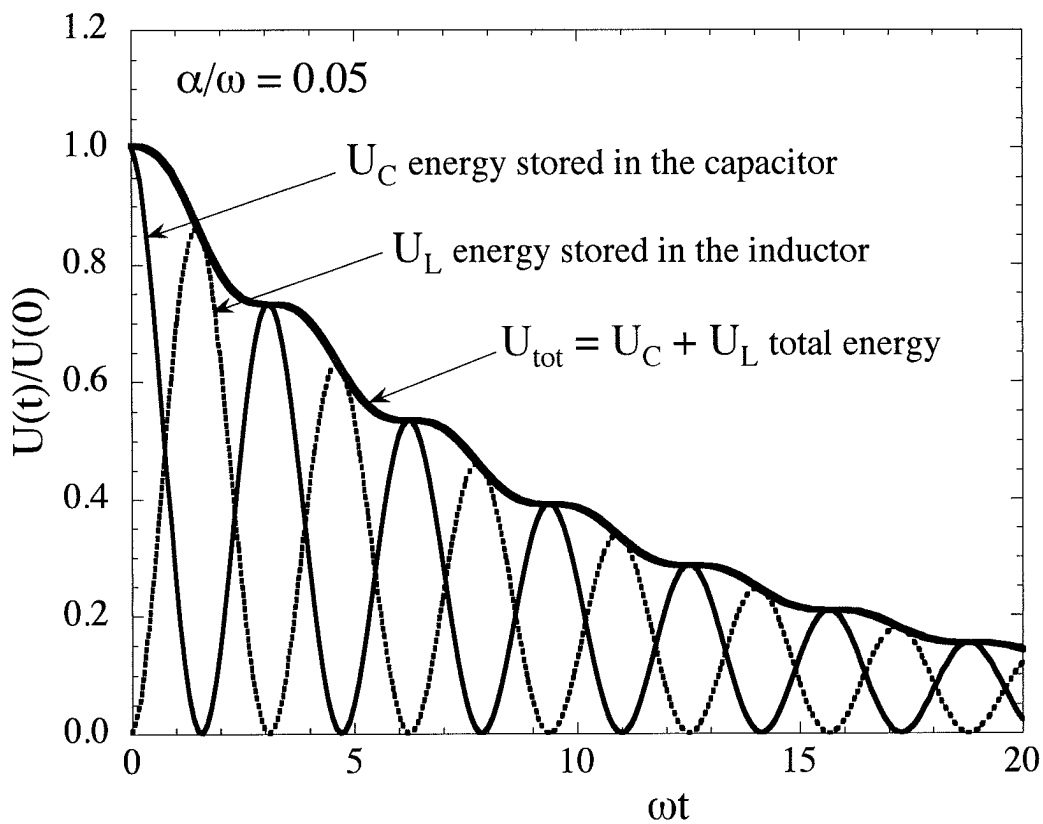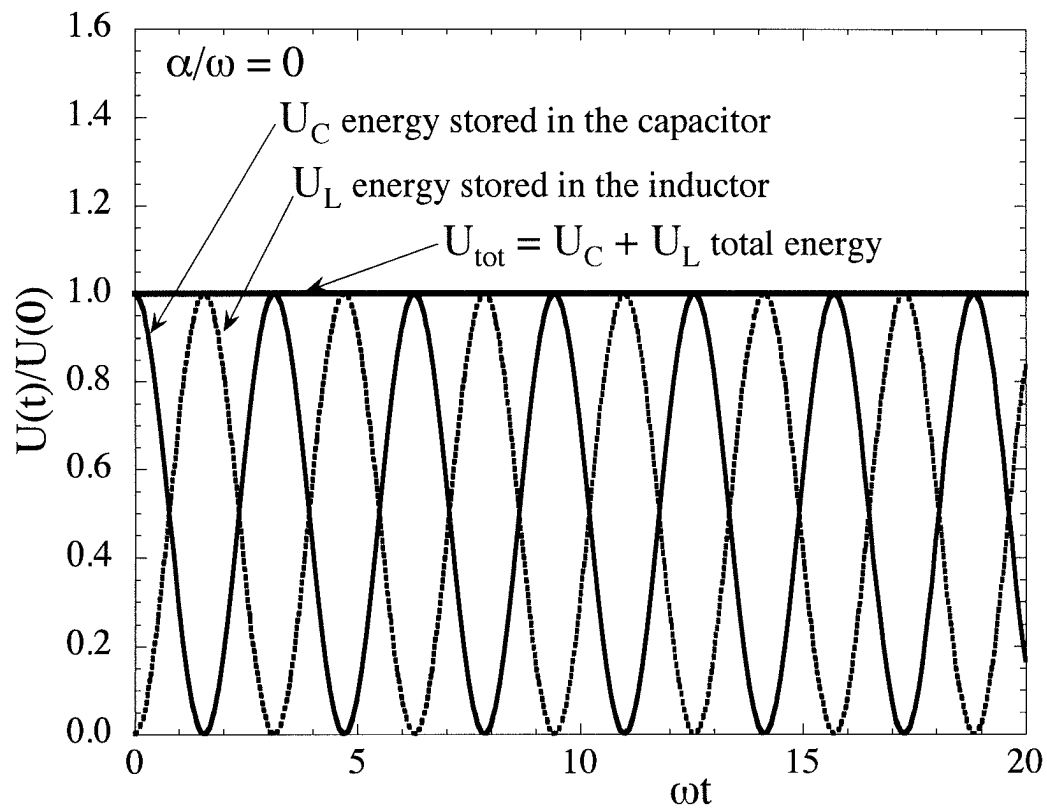
$$Q \approx \frac{2\pi}{1 - (1 - 2\alpha T)} = \frac{2\pi}{2\alpha T} = \frac{2\pi \omega}{2\alpha 2\pi} = \frac{\omega}{2\alpha}$$



$$Q = \frac{\omega}{2\alpha} = \frac{\omega}{\left(\frac{2R}{2L}\right)} = \frac{L}{R} \omega$$

recall $\frac{L}{R}$ is decay time of L-R circuit

Over damped oscillation

What if $\frac{L}{LC} < \frac{R^2}{4L^2}$ so that ω is imaginary?

$$\text{Solution is } v(t) = Ae^{-\beta_1 t} + Be^{-\beta_2 t}$$

$$\frac{dv}{dt} = -\beta_1 A e^{-\beta_1 t} - \beta_2 B e^{-\beta_2 t}$$

$$\frac{d^2v}{dt^2} = \beta_1^2 A e^{-\beta_1 t} + \beta_2^2 B e^{-\beta_2 t}$$

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

$$\Rightarrow \left(\beta_1^2 - \beta_1 \frac{R}{L} + \frac{1}{LC} \right) A e^{-\beta_1 t} + \left(\beta_2^2 - \beta_2 \frac{R}{L} + \frac{1}{LC} \right) B e^{-\beta_2 t} = 0$$

$$\Rightarrow \beta_{1,2} = \frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

If $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$ then

$$v(t) = (A + Bt) e^{-\beta t}$$