

As long as all I_i and V_i oscillate at the same single frequency, circuit analysis is greatly simplified by the use of complex representation based on use of the mathematical identity

$$e^{i\theta} = \cos\theta + i\sin\theta$$

It then follows that

$$V_i = V_{i0} \cos(\omega t + \theta_i)$$

$$= \operatorname{Re} \left[V_{i0} e^{i(\omega t + \theta_i)} \right]$$

↑
real part of complex number

$$= \operatorname{Re} \left[V_{i0} e^{i\theta_i} e^{i\omega t} \right]$$

We then call $V_{i0} e^{i\theta_i}$ the "complex" voltage representing the voltage oscillation on link i

The convenience of using this notation is that addition of oscillations with phase shifts just becomes addition of complex numbers;

$$I_1 + I_2 = I_{10} \cos(\omega t + \varphi_1) + I_{20} \cos(\omega t + \varphi_2)$$

do this the trigonometric way:

$$= I_{10} \cos\varphi_1 \cos\omega t - I_{10} \sin\varphi_1 \sin\omega t$$

$$+ I_{20} \cos\varphi_2 \cos\omega t - I_{20} \sin\varphi_2 \sin\omega t$$

$$= (I_{10} \cos\varphi_1 + I_{20} \cos\varphi_2) \cos\omega t - (I_{10} \sin\varphi_1 + I_{20} \sin\varphi_2) \sin\omega t$$

one way to prove this is to do a Taylor expansion of each function and then compare real and imaginary terms

$$I_1 + I_2 = \sqrt{(I_{10} \cos \phi_1 + I_{20} \cos \phi_2)^2 + (I_{10} \sin \phi_1 + I_{20} \sin \phi_2)^2} \cos(\omega t + \delta)$$

$$\text{where } \tan \delta = \frac{I_{10} \sin \phi_1 + I_{20} \sin \phi_2}{I_{10} \cos \phi_1 + I_{20} \cos \phi_2}$$

Now do it the complex number way:

$$I_1 + I_2 = \text{Re} \left[I_{10} e^{i\phi_1} e^{i\omega t} + I_{20} e^{i\phi_2} e^{i\omega t} \right]$$

$$= \text{Re} \left[(I_{10} e^{i\phi_1} + I_{20} e^{i\phi_2}) e^{i\omega t} \right]$$

$$= \text{Re} \left[\left((I_{10} \cos \phi_1 + I_{20} \cos \phi_2) + i (I_{10} \sin \phi_1 + I_{20} \sin \phi_2) \right) e^{i\omega t} \right]$$

For a complex number $z = x + iy$

$$z = \sqrt{x^2 + y^2} e^{i\delta} \quad \text{with } \tan \delta = \frac{y}{x}$$

$$I_1 + I_2 = \text{Re} \left[\sqrt{(I_{10} \cos \phi_1 + I_{20} \cos \phi_2)^2 + (I_{10} \sin \phi_1 + I_{20} \sin \phi_2)^2} e^{i\delta} e^{i\omega t} \right]$$

gives same result as trig method.

So when we apply Kirchhoff's laws to an ac circuit, we just apply it to addition of complex numbers

$$\sum_{\text{in}} I_{\text{in}} = \sum_{\text{out}} I_{\text{out}}$$

$$\sum_{\text{loop}} V_c = 0$$

Moreover, the relation between I_c and V_c for any circuit element is easily expressed in terms of this complex notation.

Resistor : $V = IR$

$$\Rightarrow \text{For } I = I_0 \cos(\omega t + \varphi) = \text{Re} [I_0 e^{i\varphi} e^{i\omega t}]$$

$$V = I_0 R \cos(\omega t + \varphi) = \text{Re} [I_0 R e^{i\varphi} e^{i\omega t}]$$

Complex current $I = I_0 e^{i\varphi}$

Complex voltage $V = RI_0 e^{i\varphi}$ or $V = RI$

Inductor $V = L \frac{dI}{dt}$

$$\text{For } I = I_0 \cos(\omega t + \varphi) = \text{Re} [I_0 e^{i\varphi} e^{i\omega t}]$$

$$V = L \frac{dI}{dt} = -\omega L I_0 \sin(\omega t + \varphi)$$

$$= \text{Re} [i\omega L I_0 e^{i\varphi} e^{i\omega t}]$$

Complex current $I = I_0 e^{i\varphi}$

Complex voltage $V = i\omega L I_0 e^{i\varphi}$ or $V = i\omega L I$

Capacitor

$$V = \frac{Q}{C} \Rightarrow C \frac{dV}{dt} = I \text{ or } V = \frac{1}{C} \int dt I$$

$$\text{For } I = I_0 \cos(\omega t + \varphi) = \text{Re} [I_0 e^{i\varphi} e^{i\omega t}]$$

$$V = \frac{1}{\omega C} I_0 \sin(\omega t + \varphi) = \text{Re} [\frac{-i}{\omega C} I_0 e^{i\varphi} e^{i\omega t}]$$

Complex current $I = I_0 e^{i\varphi}$

Complex voltage $V = \frac{-i}{\omega C} I_0 e^{i\varphi}$ or $V = \frac{-i}{\omega C} I$

So the I-V relations of inductors and capacitors instead of being differential relations become just multiplication of complex numbers!

resistor	$V = RI$
inductor	$V = i\omega L I$
capacitor	$V = \frac{-i}{\omega C} I$

In this complex representation, the ratio V/I of an circuit element is called its impedance Z .
 Its inverse $\frac{I}{V}$ is called its admittance Y .

$$Y = \frac{1}{Z}$$


	impedance Z	admittance Y
resistor	R	$\frac{1}{R}$
inductor	$i\omega L$	$\frac{-i}{\omega L}$
capacitor	$\frac{-i}{\omega C}$	$i\omega C$

$$V = ZI \quad \text{or} \quad I = YZ$$

Examples

$$E = E_0 \cos \omega t$$

①

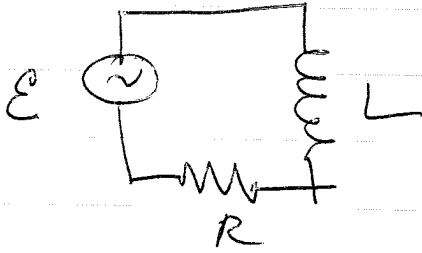

$$E = V_L + V_R$$

$$E_0 = Z_L I + Z_R I \quad \text{complex}$$
$$= i\omega L I + R I$$

$$I = \frac{E_0}{R + i\omega L}$$

$$= \frac{E_0 (R - i\omega L)}{R^2 + \omega^2 L^2}$$

$$= \frac{E_0}{R^2 + \omega^2 L^2} (R^2 + \omega^2 L^2)^{1/2} e^{-i\delta}$$

$$\tan \delta = \frac{+\omega L}{R}$$


$$I(t) = \text{Re} \left[\frac{E_0}{\sqrt{R^2 + \omega^2 L^2}} e^{i\delta} e^{i\omega t} \right]$$

$$= \frac{E_0}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \delta)$$

Same answer we found earlier

for real a, b , use $a + ib = \sqrt{a^2 + b^2} e^{i\delta}$
 $\tan \delta = \frac{b}{a}$

②

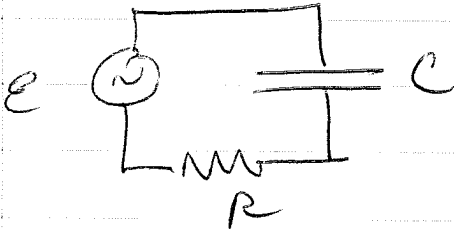

$$E = E_0 \cos \omega t$$

$$\begin{aligned} E_0 &= Z_C I + Z_R I \\ &= \frac{-j}{\omega C} I + R I \end{aligned}$$

$$I = \frac{E_0}{R - \frac{j}{\omega C}} = \frac{E_0 (R + \frac{j}{\omega C})}{R^2 + (\frac{1}{\omega C})^2}$$

$$R + \frac{j}{\omega C} = \sqrt{R^2 + (\frac{1}{\omega C})^2} e^{j\delta}$$


$$= \frac{E_0}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} e^{j\delta} \quad \text{where } \tan \delta = \frac{1}{\omega R C}$$

$$I(t) = \operatorname{Re} \left[\frac{E_0}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} e^{j\delta} e^{j\omega t} \right]$$

$$= \frac{E_0}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \cos(\omega t + \delta)$$

same result as earlier

③

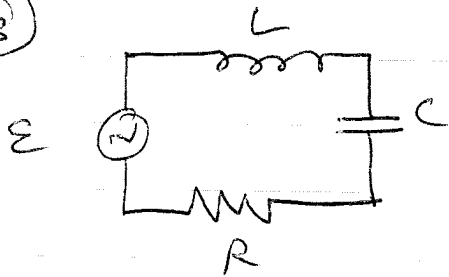

$$e = \epsilon_0 \cos \omega t$$

$$\epsilon_0 = Z_L I + Z_C I + Z_R I$$

$$= i\omega L I - \frac{i}{\omega C} I + R I$$

$$I = \frac{\epsilon_0}{R + i(\omega L - \frac{1}{\omega C})} = \frac{\epsilon_0 (R - i(\omega L - \frac{1}{\omega C}))}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{\epsilon_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{i\delta}$$

$$\text{where } \tan \delta = \frac{-\omega L + \frac{1}{\omega C}}{R}$$

$$I(t) = \text{Re} \left[\frac{\epsilon_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} e^{i\delta} e^{i\omega t} \right]$$

$$= \frac{\epsilon_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \cos(\omega t + \delta)$$

$$\tan \delta = \frac{\frac{1}{\omega C} - \omega L}{R}$$

same answer as found earlier!

Power and Energy

If voltage across resistor R is $V_0 \cos \omega t$
then P is ^{instantaneous} power, i.e. the rate at which
energy is being dissipated is

$$P(t) = I^2 R = \frac{V_0^2 \cos^2 \omega t}{R}$$



The average power, averaged over one cycle is

$$\begin{aligned} \bar{P} &= \frac{1}{T} \int_0^T dt \frac{V_0^2 \cos^2 \omega t}{R} \quad \text{where } T = \frac{2\pi}{\omega} \text{ is} \\ &= \frac{1}{2} \frac{V_0^2}{R} \quad (\text{since average of } \cos^2 \omega t \text{ is } \frac{1}{2}) \end{aligned}$$

one period of oscillation

One defines the root-mean-square (rms) value
of the voltage by

$$\begin{aligned} V_{\text{rms}} &= \left[\frac{1}{T} \int_0^T dt (V(t))^2 \right]^{1/2} \\ &= \left[\frac{1}{T} \int_0^T dt V_0^2 \cos^2 \omega t \right]^{1/2} \\ &= \left[\frac{1}{2} V_0^2 \right]^{1/2} \end{aligned}$$

$$V_{\text{rms}} = \frac{1}{\sqrt{2}} V_0 = \frac{\text{Amplitude of oscillation}}{\sqrt{2}}$$


In terms of V_{rms} ,

$$P = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{rms}^2}{R}$$

When one gives the values of an ac voltage or current, it is customary to give the rms value $V_{rms} = \frac{1}{\sqrt{2}} V_0$ or $I_{rms} = \frac{1}{\sqrt{2}} I_0$, rather than the amplitude of the oscillation V_0 or I_0 .

In general, the instantaneous power delivered to any circuit element is

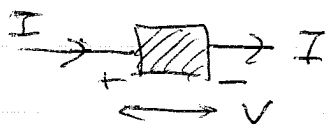
$$P(t) = V(t) I(t) \quad \text{where } V(t) \text{ is voltage drop across the element}$$



(This follows since QdV is the work done moving Q across the voltage drop V so the ~~work done~~ ^{power} to move one charge Q is $Q\vec{v} \cdot \vec{E}$ \vec{v} is velocity \vec{E} is electric field. Total power ~~done~~ ^{done} $(mAL)Q\vec{v} \cdot \vec{E}$ where A is area, L length, m charge density of element so mAL is numbr of charges.

$$\begin{aligned} (mALQ\vec{v} \cdot \vec{E}) &= mAQv \left(+\frac{V}{L} \right) \\ &= mAQvV = IV \end{aligned}$$

Consider the LR circuit

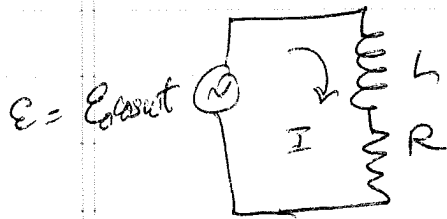

we found $I(t) = I_0 \cos(\omega t + \phi)$

$$I_0 = \frac{E_0}{\sqrt{R^2 + \omega^2 L^2}} \quad \tan \phi = -\frac{\omega L}{R}$$

The power delivered to the LR combination is


$$\begin{aligned} P(t) &= E(t) I(t) = E_0 I_0 \cos \omega t \cos(\omega t + \phi) \\ &= E_0 I_0 (\cos \omega t)(\cos \omega t \cos \phi - \sin \omega t \sin \phi) \\ &= E_0 I_0 (\cos \phi \cos^2 \omega t - \sin \phi \sin \omega t \cos \omega t) \\ &= E_0 I_0 (\cos \phi \cos^2 \omega t - \sin \phi \frac{\sin 2\omega t}{2}) \end{aligned}$$

When we integrate over one period of oscillation, $\cos^2 \omega t$ averages to $\frac{1}{2}$ while $\sin 2\omega t$ averages to zero.

$$\bar{P} = \frac{1}{2} E_0 I_0 \cos \phi = E_{\text{rms}} I_{\text{rms}} \cos \phi$$

In this circuit, all the energy dissipated is dissipated in the resistor R.
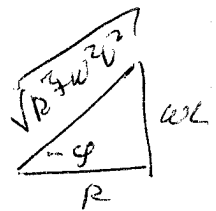
$$\begin{aligned} V_R &= IR = I_0 R \cos \omega t \\ P_R(t) &= I V_R = I_0^2 R \cos^2 \omega t \\ \bar{P}_R &= \frac{1}{2} I_0^2 R \end{aligned}$$



$$\text{Compare to } \bar{P} = \frac{1}{2} E_0 I_0 \cos \phi = \frac{1}{2} \frac{E_0}{\sqrt{R^2 + \omega^2 L^2}} I_0^2 \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{2} I_0^2 R$$

whereas the energy dissipated in the inductor is


$$V_L = L \frac{dI}{dt} = -\omega L I_0 \sin(\omega t + \varphi)$$

$$P_L(t) = \int V_L = -\omega L I_0^2 \sin(\omega t + \varphi) \cos(\omega t + \varphi)$$

$$= -\frac{1}{2} \omega L I_0^2 \underbrace{\sin 2(\omega t + \varphi)}_{\text{averages to zero}}$$


$$\overline{P}_L = 0$$

so all energy is dissipated in R .

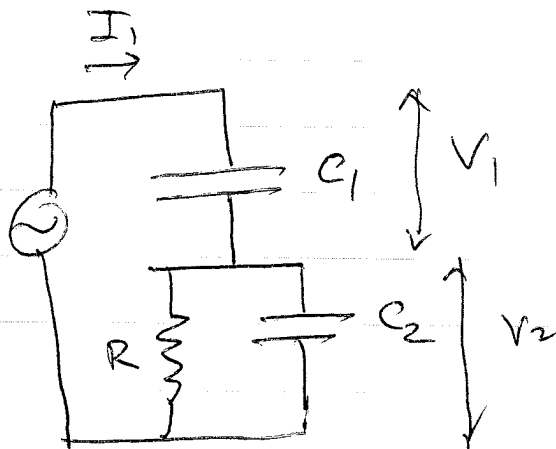

for parallel elements $\frac{1}{Z_{\text{eff}}} = \frac{1}{Z_1} + \frac{1}{Z_2}$

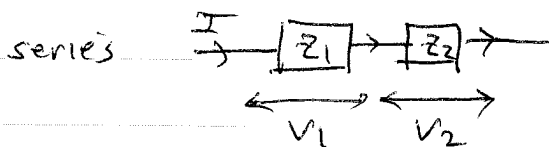for series elements $Z_{\text{eff}} = Z_1 + Z_2$



we have $V = V_1 + V_2$


$$= IZ_1 + IZ_2$$

$$= I(Z_1 + Z_2)$$

$$= I Z_{\text{eff}}$$

$$\Rightarrow Z_{\text{eff}} = Z_1 + Z_2$$

parallel

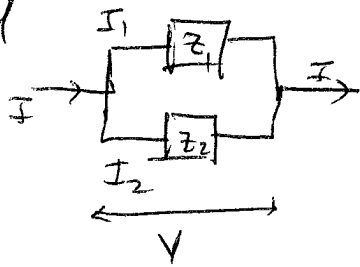

we have $V = I_1 Z_1$

$$V = I_2 Z_2$$

$$I_1 + I_2 = I$$


$$\Rightarrow \frac{V}{Z_1} + \frac{V}{Z_2} = \frac{V}{Z_{\text{eff}}}$$

$$\Rightarrow \frac{1}{Z_{\text{eff}}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

we have $Z_R = R$, $Z_{C_2} = \frac{-i}{\omega C_2}$, $Z_{C_1} = \frac{-i}{\omega C_1}$

replace R and C_2 in parallel by
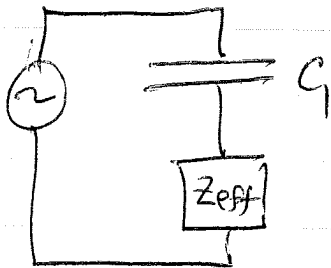
$$Z_{\text{eff}} = \frac{Z_R Z_{C_2}}{Z_R + Z_{C_2}} = \frac{R \left(\frac{-i}{\omega C_2} \right)}{R + \left(\frac{-i}{\omega C_2} \right)}$$



now replace C_1 and Z_{eff} in series by

$$Z_{\text{tot}} = Z_{\text{eff}} + \frac{-i}{\omega C_1}$$

$$= \frac{\frac{-iR}{\omega C_2}}{R - \frac{i}{\omega C_2}} - \frac{i}{\omega C_1}$$

$$= \frac{-iR}{\omega C_2 R - i} - \frac{i}{\omega C_1}$$

$$= \frac{R}{1 + i\omega C_2 R} - \frac{i}{\omega C_1}$$

$$= \frac{R(1 - i\omega C_2 R)}{1 + \omega^2 C_2^2 R^2} - \frac{i}{\omega C_1}$$

$$Z_{tot} = \frac{R}{1 + \omega^2 C_2^2 R^2} - i \left(\frac{\omega C_2 R^2}{1 + \omega^2 C_2^2 R^2} + \frac{1}{\omega C_1} \right) = Z_1 + i Z_2$$

Z_1, Z_2 real

If the voltage is $E(t) = E_0 \cos \omega t$, then the current is

~~$I_1 = E_0 \cos \omega t$~~

$$I_1 = \frac{E_0}{Z_{tot}} = I_0 \cos(\omega t + \varphi)$$

where $I_0 = \frac{E_0}{(Z_1^2 + Z_2^2)^{1/2}}$ $\tan \varphi = \frac{Z_2}{Z_1}$

Power dissipated is $\bar{P} = \frac{1}{2} I_0 E_0 \cos \varphi$

so $\bar{P} = \frac{1}{2} I_0^2 (Z_1^2 + Z_2^2)^{1/2} \frac{Z_1}{\sqrt{Z_1^2 + Z_2^2}}$

$$\cos \varphi = \frac{Z_1}{\sqrt{Z_1^2 + Z_2^2}}$$

$$\bar{P} = \frac{1}{2} I_0^2 Z_1$$

↑ real part of the total impedance