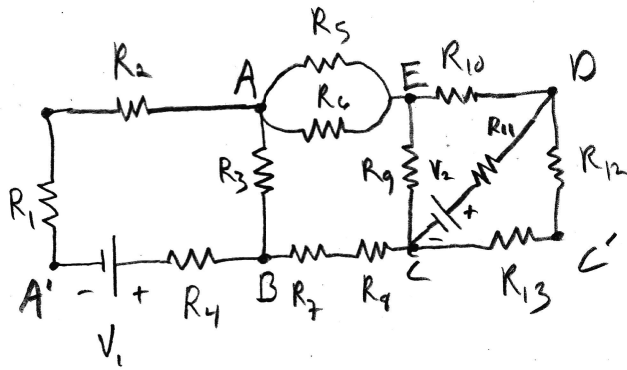


7-11-08

7.

$\vec{I}_1$



For this, I'm using step 0; reduce using addition rules for resistors!

Given:  $V_1, V_2$ , all  $R_L$

0) Add resistors,  $R_1 + R_2$  combine in series

$$R_A = R_1 + R_2$$

$R_5 + R_6$  in parallel


$$R_B = \frac{1}{1/R_5 + 1/R_6}$$

$R_7 + R_8$  in series

$$R_C = R_7 + R_8$$

$R_{12} + R_{13}$  in series

$$R_D = R_{12} + R_{13}$$

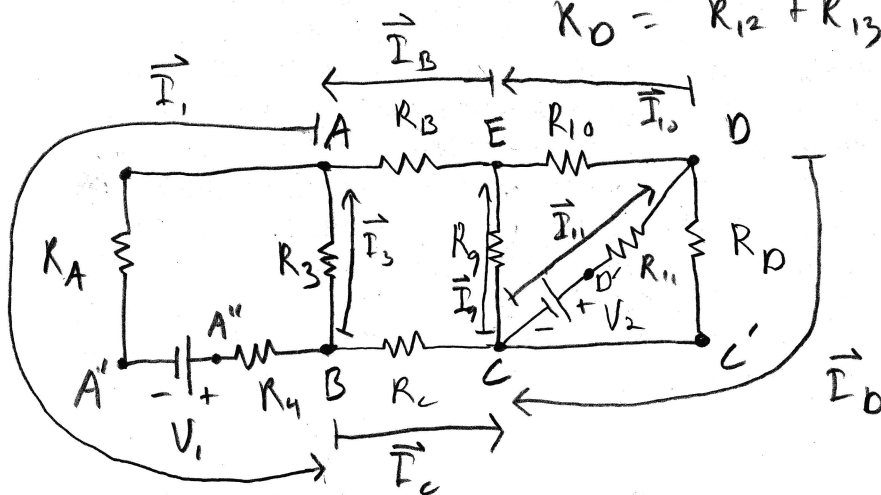

7-11-08

8.

1) Label currents. I've named currents for one of the resistors they pass through. There are 8 of them.

2) Identify unknowns. All the currents:

$I_1, I_3, I_B, I_c, I_g, I_{II}, I_D$

3) Apply junction rule. Notice that I've labeled slightly fewer points this time. My gut reading of the diagram tells me that using all 5 A, B, C, D, E will be useful. Why? There are 8 unknown currents and only 5 equations, so the whole thing still has a lot of freedom.

$$\begin{array}{l} \text{A: } I(\text{BA}'\text{A}) = -I_1 \\ \quad + I(\text{EA}) = I_B \\ \quad + I(\text{BA}) = I_3 \\ \hline \quad \quad \quad 0 \end{array} \quad \left. \begin{array}{l} \text{eq. 1} \\ I_1 = I_B + I_3 \end{array} \right\}$$

$$\begin{array}{l} \text{B: } I(\text{AA}'\text{B}) = I_1 \\ \quad + I(\text{AB}) = -I_3 \\ \quad + I(\text{CB}) = -I_c \\ \hline \quad \quad \quad 0 \end{array} \quad \left. \begin{array}{l} I_1 = I_c + I_3 \end{array} \right\}$$

eq. 2.

$$\boxed{I_B = I_c}$$

use  $I_B$  for both now.

$$\begin{array}{l} \text{C: } I(\text{BC}) = I_B \\ \quad + I(\text{EC}) = -I_g \\ \quad + I(\text{DC}'\text{C}) = I_D \\ \quad + I(\text{DC}) = -I_{II} \\ \hline \quad \quad \quad 0 \end{array} \quad \left. \begin{array}{l} \text{eq. 3} \\ I_g + I_{II} = I_B + I_D \end{array} \right\}$$

$$\begin{array}{lcl}
 D: & I(CC'D) = -I_0 \\
 & + I(CD) = I_{11} \\
 & + I(EO) = -I_{10} \\
 \hline
 & 0
 \end{array} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \text{eq. 4} \quad I_{11} = I_0 + I_{10}$$

$$\begin{array}{lcl}
 E: & I(DE) = I_{10} \\
 & + I(CE) = I_9 \\
 & + I(AE) = -I_B \\
 \hline
 & 0
 \end{array} \quad \left. \begin{array}{l} \\ \\ \\ \end{array} \right\} \text{eq. 5} \quad I_B = I_9 + I_{10}$$

4) Apply Loop Rule. We need 3 more equations. One choice of 3 that covers every thing is:

$$\textcircled{1} \quad \underline{AA'A''BCC'DEA}, \quad \textcircled{2} \quad \underline{BC, D, E, A, B}, \quad \textcircled{3} \quad \underline{CDE}$$

Loop

$$\begin{array}{lcl}
 \underline{AA'A''BCC'DEA}: & -AA': & I_1 R_A \\
 & +A'A'': & V_1' \\
 & -A''B: & I_1 R_4 \\
 & -BC: & I_B R_C \\
 & -CC': & 0' \\
 & -C'D: & -I_0 R_0' \\
 & -DE: & I_{10} R_{10} \\
 & -EA: & I_B R_B \\
 \hline
 & 0
 \end{array} \quad \left. \begin{array}{l} \\ \\ \\ \\ \\ \\ \\ \end{array} \right\} \text{eq. 6}$$

$$V_1 + I_0 R_0 = I_1 (R_A + R_4) + I_B (R_B + R_C) + I_{10} R_{10}$$

Loop

$$\begin{array}{lcl}
 \underline{BCD'DEAB}: & -BC: & I_B R_C \\
 & +CD': & V_2' \\
 & -D'D: & I_{11} R_{11} \\
 & -DE: & I_{10} R_{10} \\
 & -EA: & I_B R_B \\
 & -AB: & -I_3 R_3' \\
 \hline
 & 0
 \end{array} \quad \left. \begin{array}{l} \\ \\ \\ \\ \\ \end{array} \right\} \text{eq. 7}$$

$$V_2 + I_3 R_3 = I_B (R_B + R_C) + I_{10} R_{10} + I_{11} R_{11}$$

Loop

C'D'DEL

$$\begin{array}{l}
 \text{C'D': } V_2 \\
 - \text{D'D: } I_{11} R_{11} \\
 - \text{DE: } I_{10} R_{10} \\
 - \text{EC: } -I_9 R_9 \\
 \hline
 0
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{C'D': } V_2 \\ - \text{D'D: } I_{11} R_{11} \\ - \text{DE: } I_{10} R_{10} \\ - \text{EC: } -I_9 R_9 \end{array}} \right\} \text{eq. 8}$$

$$V_2 + I_9 R_9 = I_{10} R_{10} + I_{11} R_{11}$$

5) Solve equations. First, simplify the currents down a bit.

$$\text{eq. 5} \rightarrow \text{eq. 3} \quad I_9 + I_{10} + I_D = I_9 + I_{11}$$

$$I_{11} = I_D + I_{10}$$

This is the same as eq. 4!

This means we have a redundancy in our equations, so we are 1 short! Let's push on for now, and see if we can later identify a loop to help us. In the mean time, I am retiring eq. 3.

$$\text{eq. 5} \rightarrow \text{eq. 1} \quad I_1 = I_9 + I_{10} + I_3$$

So to summarize what we know from junctions:

$$\begin{array}{l}
 I_1 = I_9 + I_{10} + I_3 \\
 I_D = I_C = I_9 + I_{10} \\
 I_{11} = I_D + I_{10}
 \end{array}$$

This means if I find  $I_3, I_9, I_{10}, I_D$  then we get  $I_1, I_D, I_C$ , and  $I_{11}$ .

7-11-05

111

Now use loop eqs.

eq. 8  $\rightarrow$  eq. 7

$$\cancel{I_6 R_6} + \cancel{I_{11} R_{11}} - I_9 R_9 = I_B (R_B + R_C) + \cancel{I_{10} R_{10}} + \cancel{I_{11} R_{11}} - I_3 R_3$$

$$I_B = \frac{I_3 R_3 - I_9 R_9}{R_B + R_C}$$

---

We can continue on like this but you've gotten the idea. This example is much more involved than any I will give, but demonstrates the techniques.