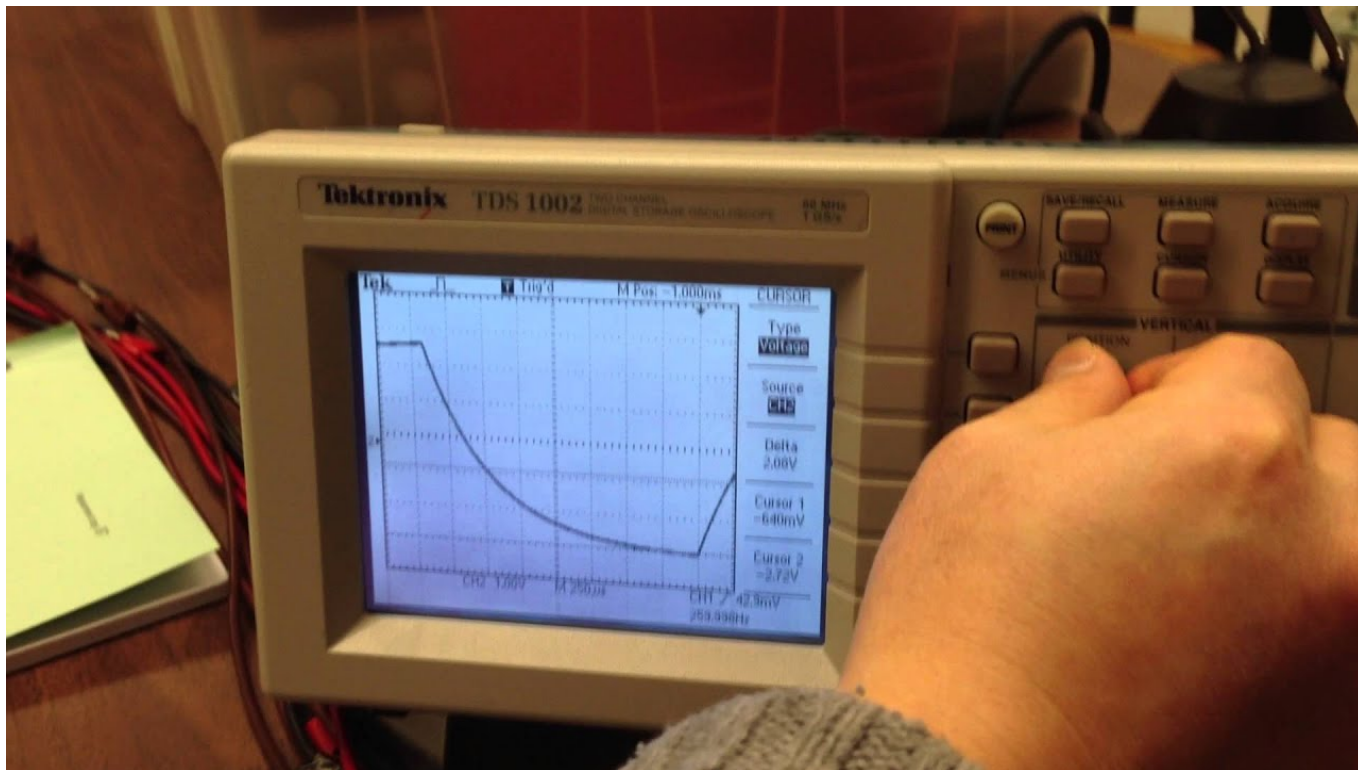



# Today in Physics 122: Kirchhoff's rules and $RC$ circuits

- ❑ The  $RC$  time constant
- ❑ Using the Kirchhoff rules in  $RC$  circuits
- ❑ Dielectric relaxation


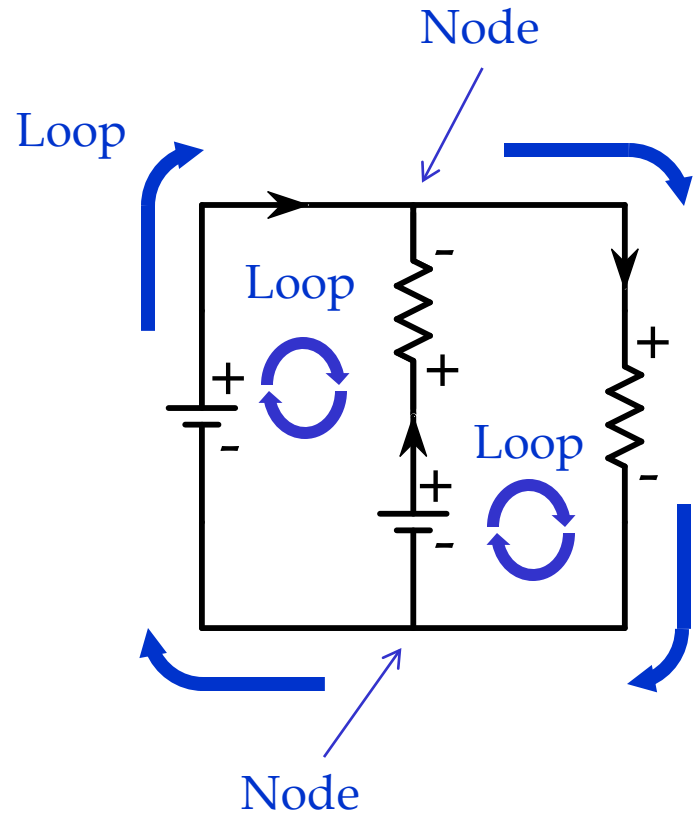
# Recap: Kirchhoff's Rules

- ❑ Charge conservation: the sum of the currents into any node is zero; as much current flows in as out.
- ❑ Energy conservation: the sum of the voltage drops for a complete loop through the circuit is zero.



---


## Recap: use of Kirchhoff's Rules

- ❑ Identify the unknown quantities –  $N$ , say – in the circuit, and count them.
- ❑ Write the node rule and/or the loop rule to generate as many relations between the voltages and currents as there are unknowns ( $N$ ).
  - Use both the node rule and the loop rule, at least once each.
- ❑ This gives a system of  $N$  equations in  $N$  unknowns, solvable with algebra.
- ❑ Important point: it **doesn't matter whether you correctly guess the direction of each current**. If you guess wrong, your answer will just be a negative number. You will still know which way the current flows.
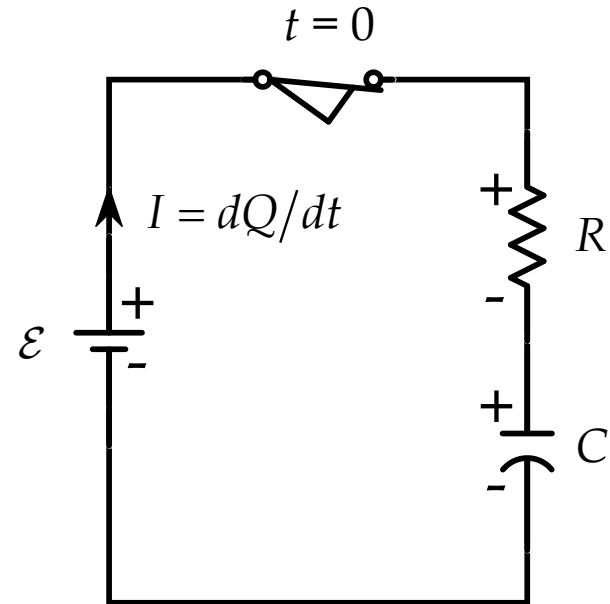
## RC circuits and the RC time constant

In a steady state, ideal capacitors draw no current. But if a circuit is assembled and switched on, one will observe that it takes time for the capacitor to receive its full charge.

- Key: since capacitors accumulate a charge  $Q$ , the resistors in series with them carry a current  $I = dQ/dt$ .
- The current in the series  $R$  should decrease to zero as  $C$  reaches its full charge.



Note:  $dQ/dt$  is presumed to have the direction that increases  $+Q$ .


## RC circuits and the RC time constant (continued)

Let's apply the loop rule to this simple circuit, in which the switch is closed at  $t = 0$ .

$$V_0 - IR - \frac{Q}{C} = 0$$

$$RC \frac{dQ}{dt} = CV_0 - Q$$
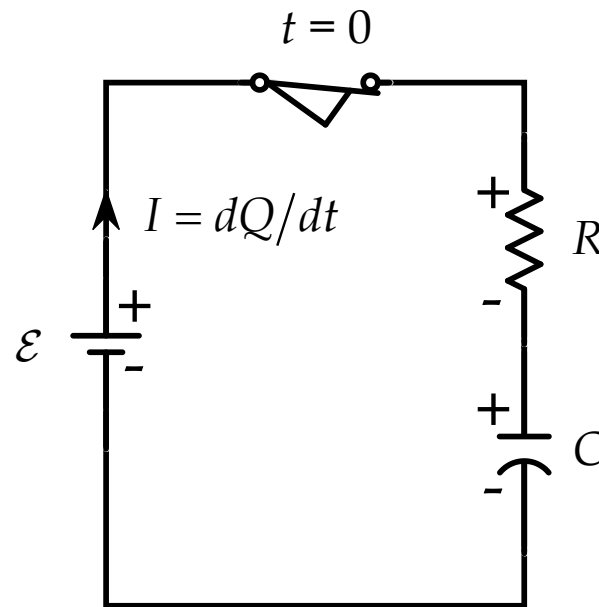
$$\int_0^Q \frac{dQ'}{CV_0 - Q'} = \frac{1}{RC} \int_0^t dt'$$



Change variables:  $q = CV_0 - Q'$   $dq = -dQ'$

As  $Q' = 0 \rightarrow Q$ ,  $q = CV_0 \rightarrow CV_0 - Q$ .

## RC circuits and the RC time constant (continued)

Thus the integral is an old friend:


$$- \int_{CV_0}^{CV_0 - Q} \frac{dq}{q} = \frac{t}{RC}$$

$$\ln q \Big|_{CV_0}^{CV_0 - Q} = \ln \frac{CV_0 - Q}{CV_0} = -\frac{t}{RC}$$

$$CV_0 - Q = CV_0 e^{-t/RC}$$

$$Q(t) = CV_0 (1 - e^{-t/RC})$$
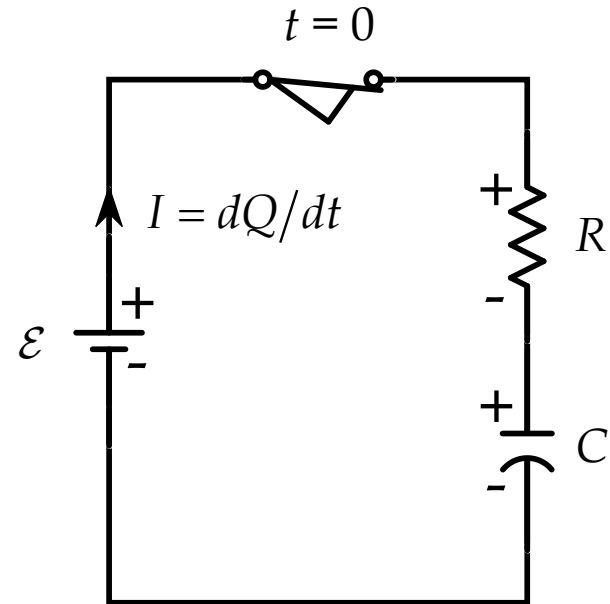
$$I(t) = \frac{dQ}{dt} = \frac{CV_0}{RC} e^{-t/RC}$$




## RC circuits and the RC time constant (continued)

The results are plotted at right.

- ❑ The current in the resistor eventually drops to zero; it reaches  $1/e$  of its initial value in  $t = RC$ .
- ❑ The charge on the capacitor eventually reaches  $CV_0$ ; it comes within  $1/e$  of this value at  $t = RC$ .

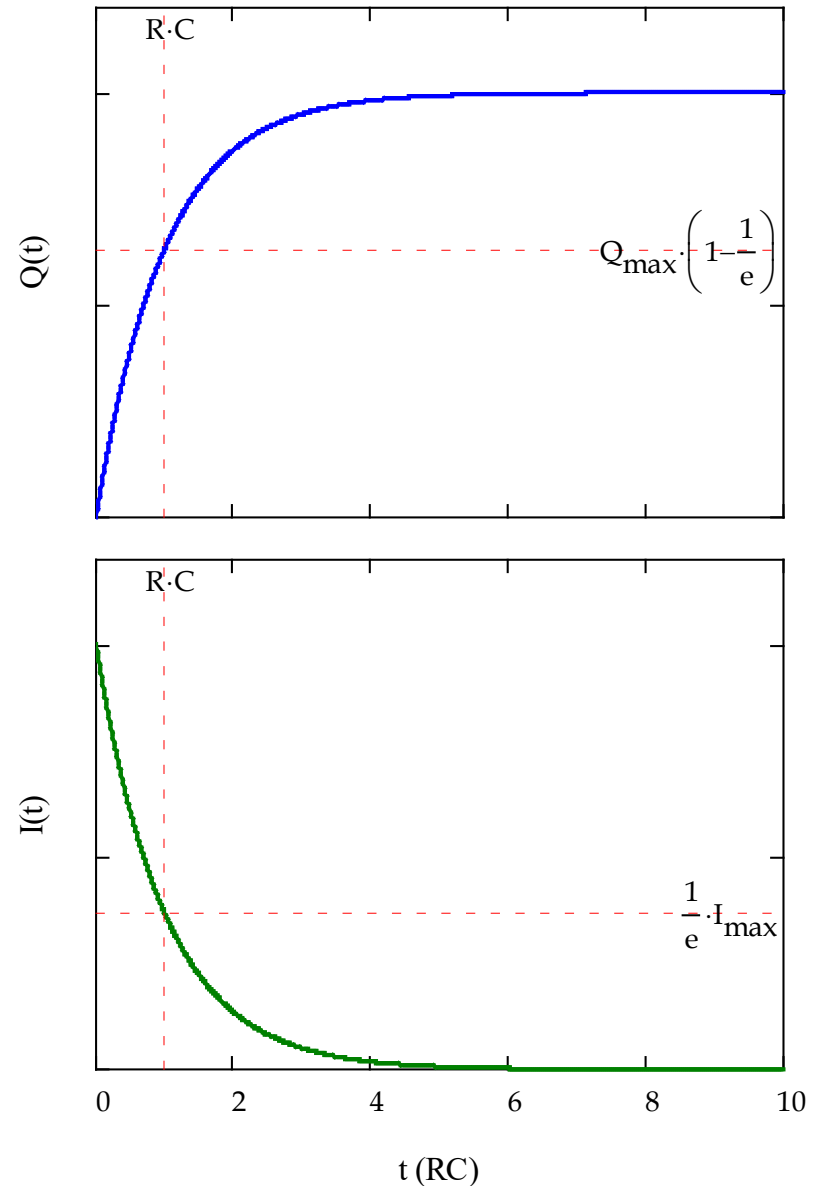The quantity  $\tau = RC$  is called the circuit's **time constant**, and is a handy measure of how long it takes to charge the capacitor.




## C with series and parallel R

In more complex circuits with capacitors one can still use Kirchhoff's rules confidently in much the same way as with purely resistive circuits.

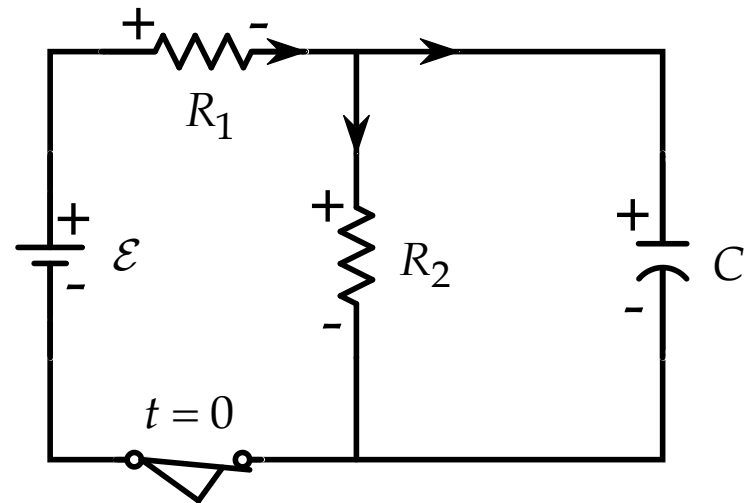- **Example 1:** *Determine the time constant, and the maximum charge on the capacitor, in this circuit.*

[Intuitively, we can tell that the maximum charge should be that for which all the current flows through the resistors; in this case the voltage across C would be  $\mathcal{E}R_1/(R_1 + R_2)$ , and the charge  $Q = C \mathcal{E}R_1/(R_1 + R_2)$ .]



## C with series and parallel R (continued)


- Like the other three-branch circuits we've dealt with, we use the node equation once and the loop equation twice:

$$I_1 - I_2 - dQ/dt = 0$$

$$V_0 - I_1 R_1 - I_2 R_2 = 0$$

$$I_2 R_2 - Q/C = 0$$

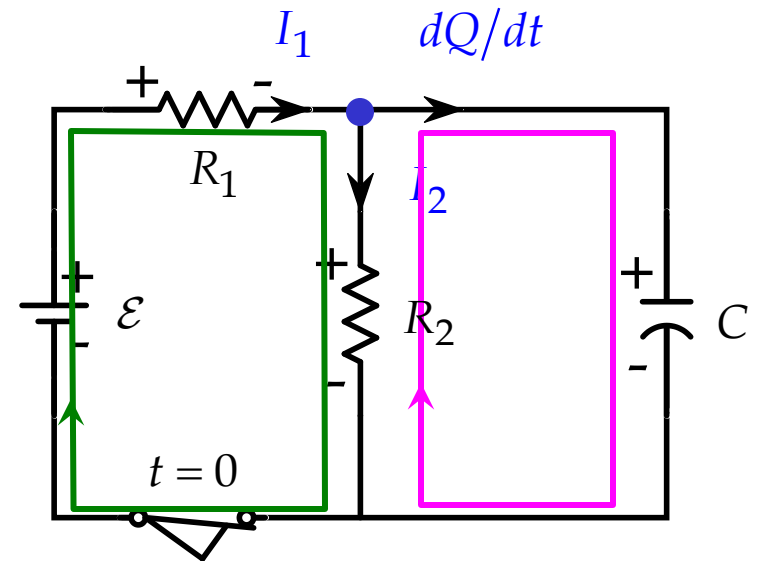- As before, the algebra strategy is to target one variable, and substitute out the other two in its favor. This time we target  $Q$ .



Three unknown currents.

Note:  $dQ/dt$  is presumed to have the direction that increases  $+Q$ .

## C with series and parallel R (continued)

- Second loop equation:


$$I_2 = \frac{Q}{R_2 C}$$

- Node equation:

$$I_1 = I_2 + \frac{dQ}{dt} = \frac{Q}{R_2 C} + \frac{dQ}{dt}$$

- Results into first loop equation, now in  $Q$  alone.
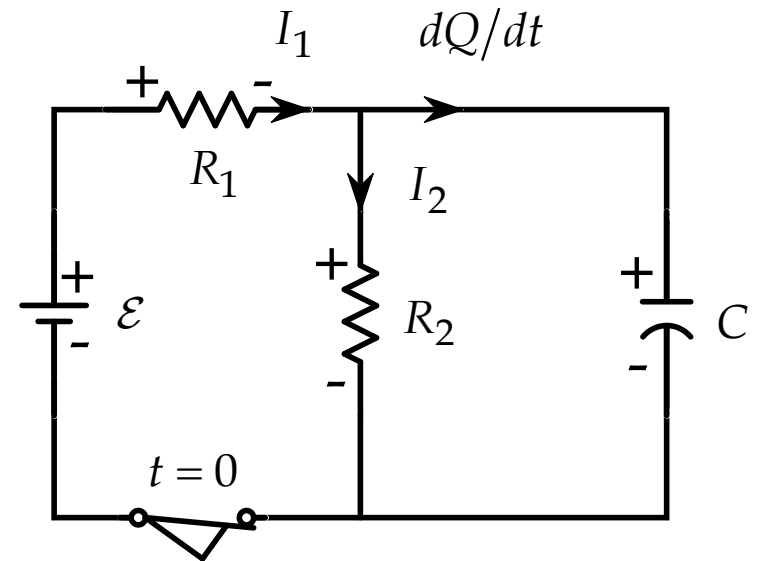
$$V_0 - R_1 \left( \frac{Q}{R_2 C} + \frac{dQ}{dt} \right) - \frac{Q}{C} = 0$$




## C with series and parallel R (continued)

□ Solve for  $dQ/dt$ :

$$\begin{aligned}\frac{dQ}{dt} &= \frac{V_0}{R_1} - \left( \frac{Q}{R_2 C} + \frac{Q}{R_1 C} \right) \\ &= \frac{V_0}{R_1} - Q \left( \frac{R_1 + R_2}{R_1 R_2 C} \right) \\ &= \frac{1}{R_1 C} \left( C V_0 - \frac{R_1 + R_2}{R_2} Q \right)\end{aligned}$$

□ Separate and integrate:
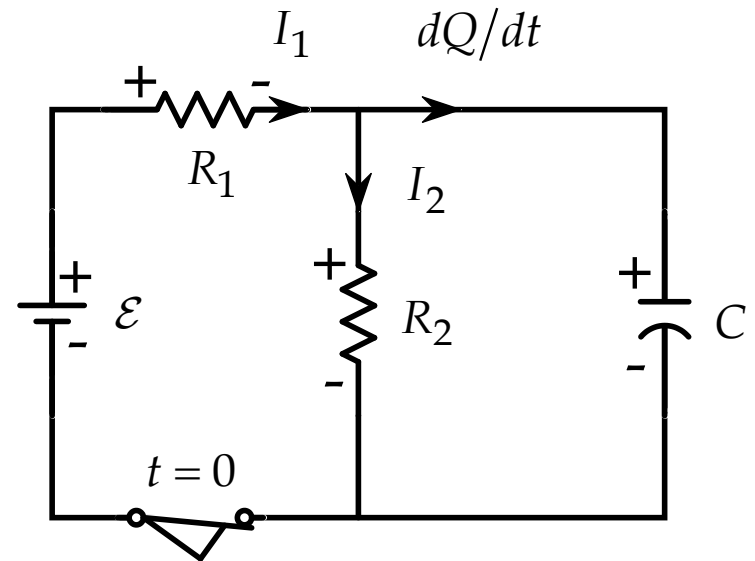
$$\int_0^Q \frac{dQ'}{C V_0 - \frac{R_1 + R_2}{R_2} Q'} = \frac{1}{R_1 C} \int_0^t dt'$$



## C with series and parallel R (continued)

□ Same integral as before. Change variables:


$$q = CV_0 - \frac{R_1 + R_2}{R_2} Q'$$

$$dq = -\frac{R_1 + R_2}{R_2} dQ'$$

As  $Q' = 0 \rightarrow Q$ ,

$$q = CV_0 \rightarrow CV_0 - \frac{R_1 + R_2}{R_2} Q:$$
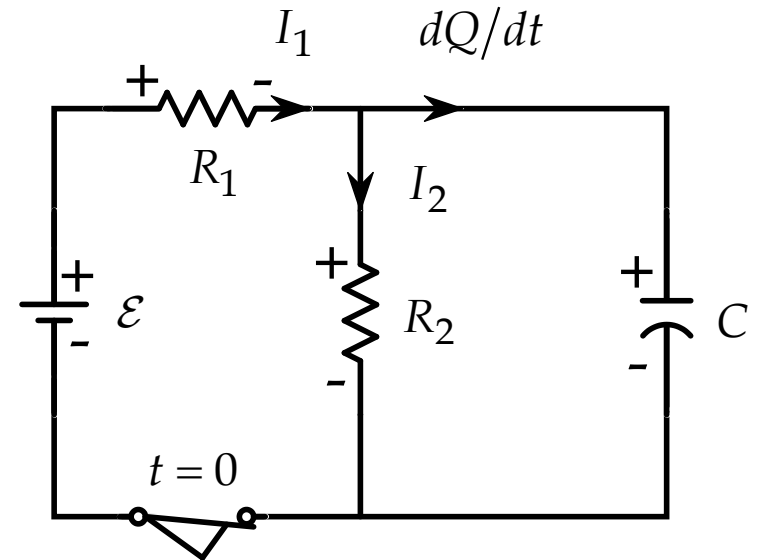
$$-\frac{R_2}{R_1 + R_2} \int_{CV_0}^{CV_0 - \frac{R_1 + R_2}{R_2} Q} \frac{dq}{q} = \frac{t}{R_1 C}$$




## C with series and parallel R (continued)

$$\ln q \Big|_{CV_0}^{CV_0 - \frac{R_1 + R_2}{R_2} Q} = -\frac{R_1 + R_2}{R_1 R_2 C} t \equiv -\frac{t}{R_{\parallel} C}$$

$$\ln \frac{CV_0 - \frac{R_1 + R_2}{R_2} Q}{CV_0} = -\frac{t}{R_{\parallel} C}$$

$$\frac{CV_0 - \frac{R_1 + R_2}{R_2} Q}{CV_0} = e^{-t/R_{\parallel} C}$$
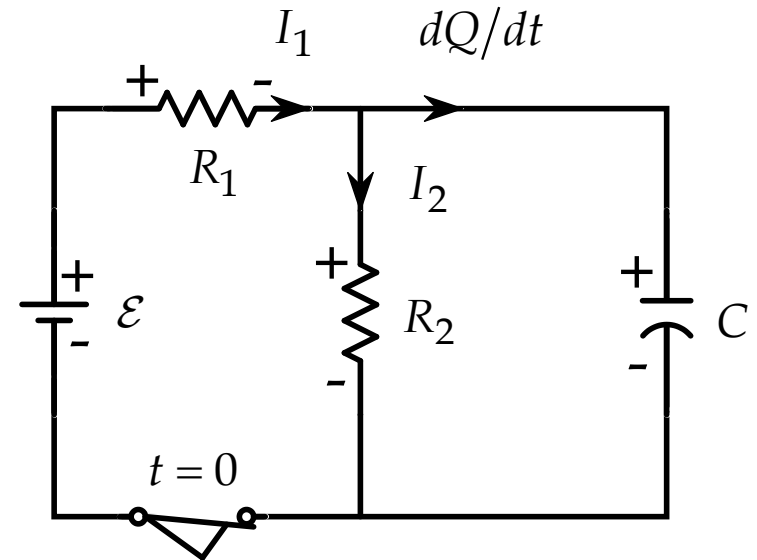
$$Q(t) = \frac{R_2}{R_1 + R_2} CV_0 \left( 1 - e^{-t/R_{\parallel} C} \right)$$



## C with series and parallel R (continued)

Comments on the solution:

- Indeed the maximum charge on the capacitor comes out to


$$Q_{\max} = \lim_{t \rightarrow \infty} Q(t) = \frac{R_2}{R_1 + R_2} CV_0,$$

as we expected.

- The time constant is

$$\tau = -\frac{t}{R_{\parallel}C} = \frac{R_1 + R_2}{R_1 R_2 C} t,$$

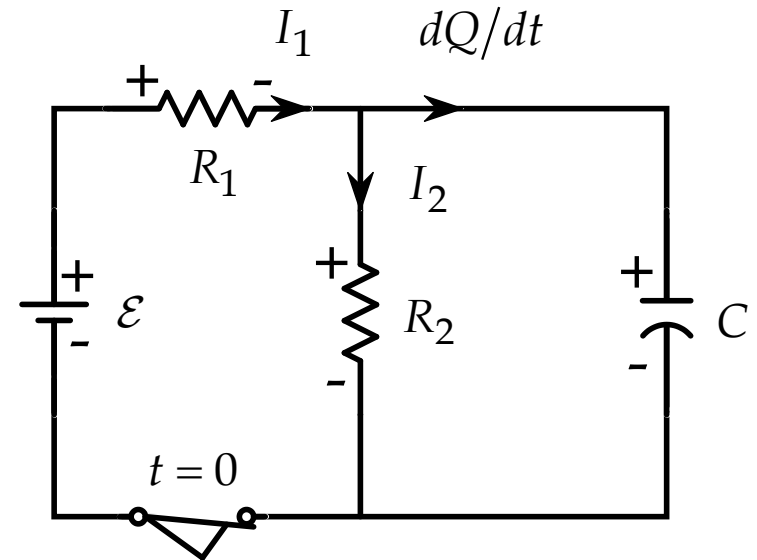as if determined by the **parallel** combination of the  $R$ s.




# Dielectric relaxation

An **application** of  $RC$  circuits to the physics of imperfect conductors/insulators:

Materials that have very large – but not infinite – resistivity can exhibit significant polarization, characterized by a dielectric constant  $> 1$ .

- ❑ Even the “bad” conductors out of which resistors are made, like graphite, have resistivity small enough that polarization effects are small:  $\kappa = 1$ .

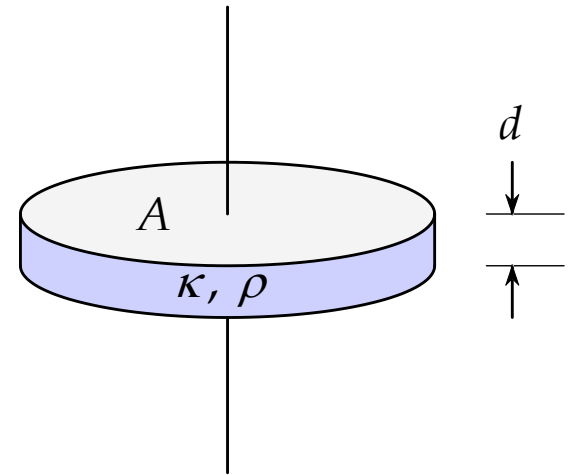Consider a parallel-plate capacitor (area  $A$ , separation  $d$ ) filled with such material (dielectric constant  $K$ , resistivity  $\rho$ ). At  $t = 0$  it has charge  $Q$ . What is the time constant with which the charge leaks away?




## Dielectric relaxation (continued)

Solution:

- We worked out the capacitance and resistance of this arrangement before, on [25 September](#) and [27 September](#) respectively:

$$C = \frac{\kappa\epsilon_0 A}{d} \quad , \quad R = \frac{\rho d}{A} \quad ,$$

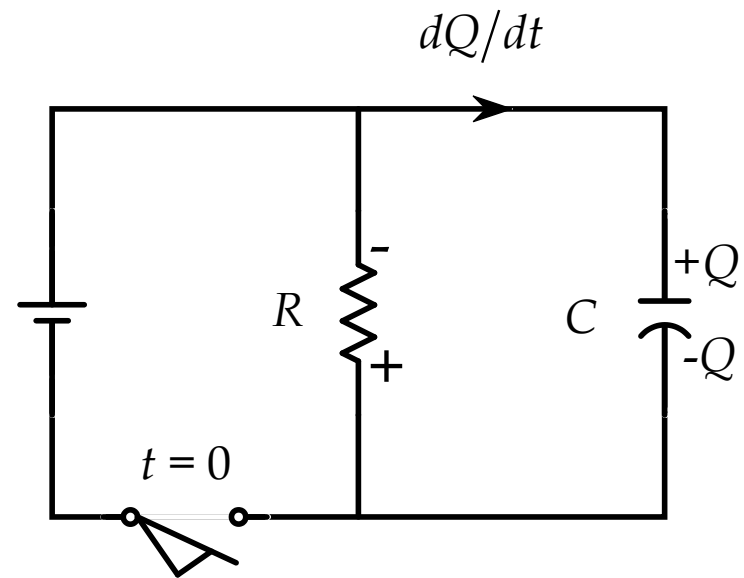and we noted that the  $R$  and  $C$  could be considered to be in parallel in the circuit-element sense.



Note:  $dQ/dt$  is presumed to have the direction that increases  $+Q$ .

## Dielectric relaxation (continued)


- Only one Kirchhoff Rule equation here, and it's a loop:

$$R \frac{dQ}{dt} + \frac{Q}{C} = 0$$

$$\int_{Q_0}^{Q(t)} \frac{dQ'}{Q'} = -\frac{1}{RC} \int_0^t dt'$$

$$\ln\left(\frac{Q(t)}{Q_0}\right) = -\frac{t}{RC}$$

$$Q(t) = Q_0 e^{-t/RC}$$

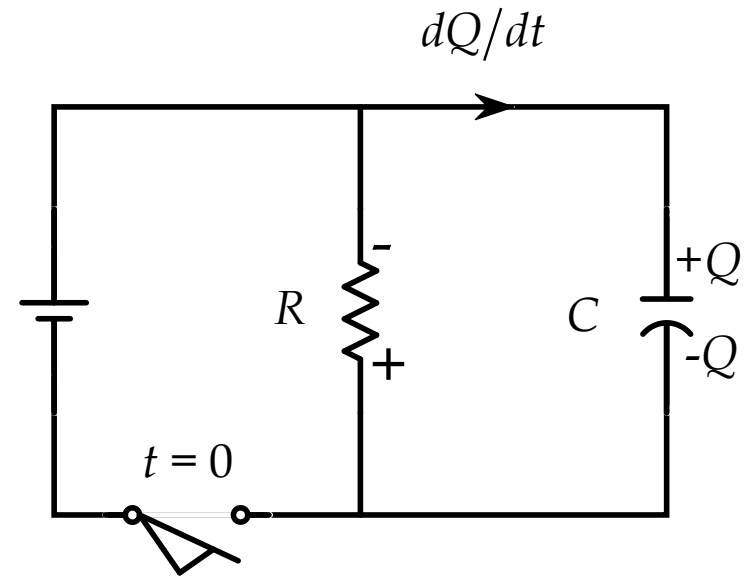

so  $\tau = RC$ , as we might have expected.

---

## Dielectric relaxation (continued)

- What's interesting about this result – at least to physicists, materials scientists, and electrical engineers – is that everything having to do with the shape of the capacitor vanishes from the expression for the time constant:

$$\tau = RC = \frac{\rho d}{A} \frac{\kappa \epsilon_0 A}{d} = \rho \kappa \epsilon_0. \quad \text{cf. Exam \#1, problem 1d.}$$

- Check with cylindrical capacitor ([25 September](#)) and resistor ([27 September](#)):

$$\tau = RC = \frac{\rho}{2\pi L} \ln\left(\frac{R_2}{R_1}\right) \frac{2\pi\kappa\epsilon_0 L}{\ln(R_2/R_1)} = \rho\kappa\epsilon_0.$$

- That is, this time constant is a property of the material, not of the shape: it is the time constant associated with how quickly charges can be moved around in high-resistivity material. That there is a limit to how quickly, is a phenomenon called **dielectric relaxation**.