

Highlights of the New Material for Midterm #4

CAVEAT EMPTOR

I strongly advise that you do not take this to be a substitute for your own gathering of the material in your mind because that won't work. Rather, I suggest that you look over these topics and make sure you've thought about and understood these before the exam.


Also, please note that I am only attempting to summarize the most important points in the material. Nowhere am I implying that you need only know these items. You are still responsible for all that is covered in classes, workshops and assigned reading and problems.

New Material

- **Magnetic Materials**
 - **Faraday's Law**
 - **Mutual and Self Inductance**
 - **LR Circuits**
 - **AC Circuits**
-
- **TA Review Before Next Midterm**
 - **December 1st, 8:30pm, B&L 109**

Magnetic Materials Review

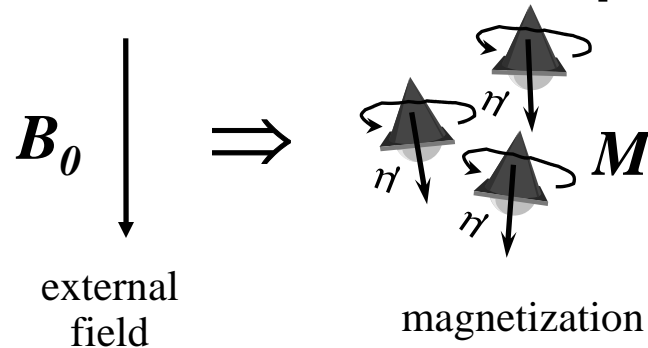- In response to an external magnetic field, materials develop internal magnetization



$$\begin{aligned}
 B_{total} &= B_0 + \mu_0 M \\
 &= (1 + \chi_m) B_0 \\
 &= \kappa_m B_0
 \end{aligned}$$

- **Paramagnetism**

- weak alignment of M and B, $0 < \chi_m \ll 1$

- **Diamagnetism**

- weak anti-alignment of M and B, $-1 \ll \chi_m < 0$

- **Ferromagnetism**


- strong alignment of M and B, $\chi_m \gg 1$

these are
way weak
effects!

very strong.
magnetization
dominates field!

It's the Floating Frog!

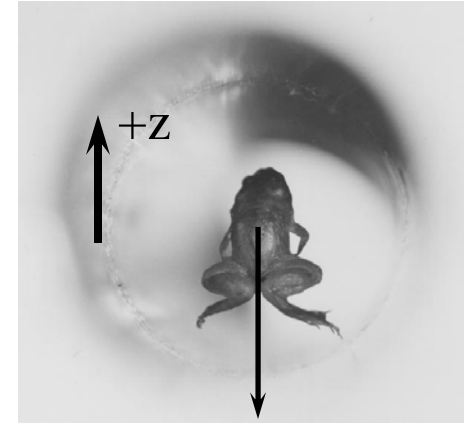- A diamagnetic frog levitates in a strong magnetic field as shown at right
- If gravity causes a downwards force in the picture at right, where is the magnitude of the field greatest?
At the bottom of the page.
- Better be able to explain why... this brings together a lot of key ideas.



$$U = -\vec{\mu} \cdot \vec{B}(z) = |\chi_m| |\vec{B}(z)|^2$$

$$F_z = -\frac{dU}{dz} = -(-\chi_m) 2B \frac{dB}{dz}$$

$$\therefore F_z > 0 \text{ if } \frac{dB}{dz} < 0$$

If potential energy is highest at bottom of page, then the frog feels an upward force.

Therefore, B is largest at bottom of the page.

The Big Picture

which you should be able to explain...

- **Electrostatics**
 - motion of “ q ” in external E-field
 - E-field generated by Σq_i
- **Magnetostatics**
 - motion of “ q ” and “ I ” in external B-field
 - B-field generated by “ I ”
- **Electrodynamics**
 - time dependent B-field generates E-field
 - ac circuits, inductors, transformers, etc
 - our last topic (not this exam)
time dependent E-field generates B-field
 - electromagnetic radiation - *light*

Faraday's and Lenz's Laws

- a changing magnetic flux through a loop induces a current in that loop

$$\varepsilon = - \frac{d\Phi_B}{dt}$$

need to understand what magnetic flux is. (Like electric flux)

negative sign indicates that the induced EMF opposes the change in flux

- Need to also understand Faraday's Law in terms of Electric Field
- It does need a loop of wire to be true!
This field can accelerate free charges not in a wire!

$$\oint \vec{E} \cdot d\vec{l} = - \frac{d\Phi_B}{dt}$$


Applications

- should be able to explain how a generator works


$$\mathcal{E} \equiv \frac{-d\Phi_B}{dt} = -\frac{d}{dt}[BA \cos \omega t] = BA\omega \sin \omega t$$




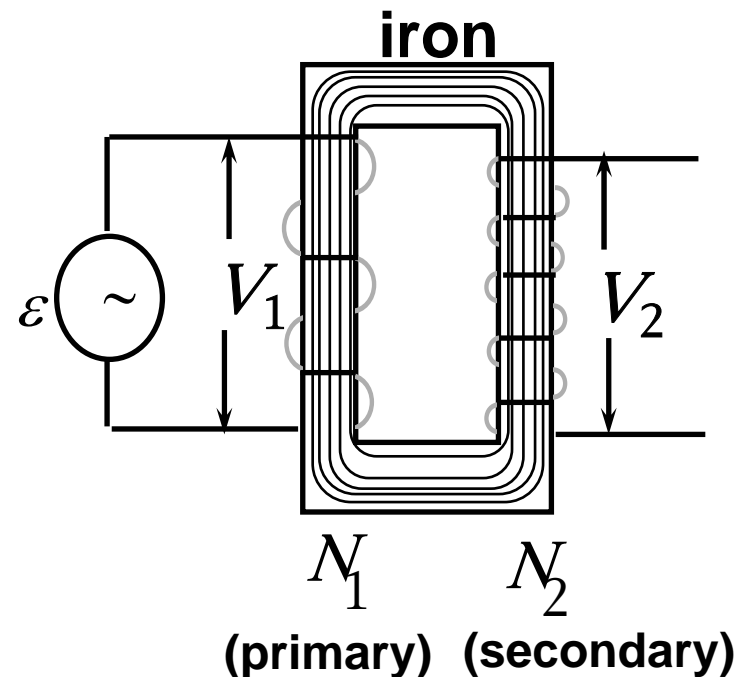- should be able to explain how a transformer works




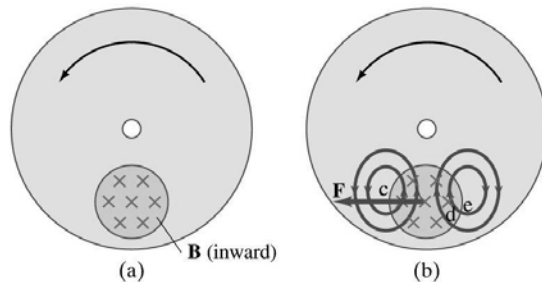
- should be able to explain our eddy current demonstrations done in class




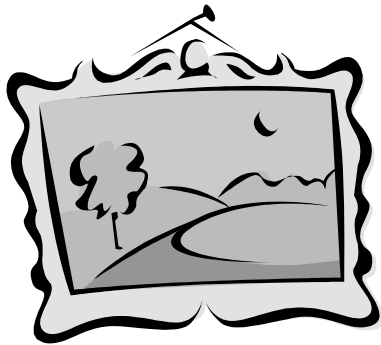

Big Picture of Inductance

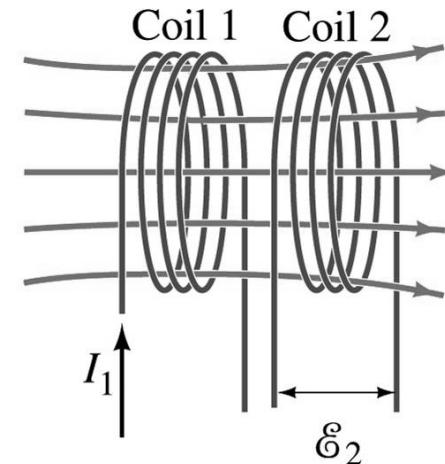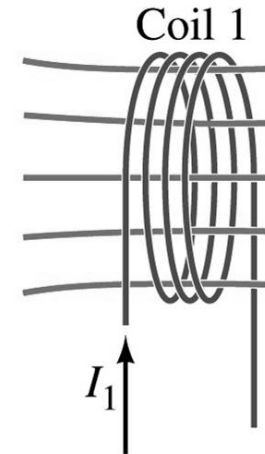- A coil produces a magnetic field
- That magnetic field produces magnetic flux in that coil and adjacent coils
- If current changes in Coil 1, flux changes in Coils 1 and 2
- That change of flux causes an EMF which induces current!
 - in Coil 2 “Mutual Inductance”;
 - in Coil 1, “Self Inductance”



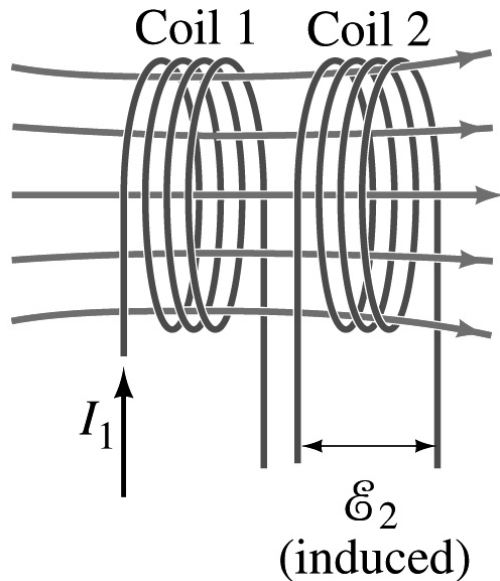

Inductors

- Current in Coil 1 causes
 - Magnetic flux in Coils 1 & 2
- *Changing current...*
 - Induces EMF in Coils 1 & 2
 - Self and Mutual Inductance
- Depends on geometry only!
 - Unit is *Henry*, $\text{T}\cdot\text{m}^2/\text{A} \equiv \Omega\cdot\text{s}$

- Mutual Inductance

$$M \equiv \frac{\Phi_B^{\text{through a from b}}}{I_b} = \frac{\Phi_B^{\text{through b from a}}}{I_a}$$


- Self-Inductance

$$L \equiv \frac{\Phi_B}{I}$$

- Self-Inductance for Solenoid $L = \mu_0 \frac{N^2}{l} \pi r^2$
- L increases with Ferromagnetic core $\mu_0 \rightarrow \mu = \kappa_M \mu_0$

Summary so far...

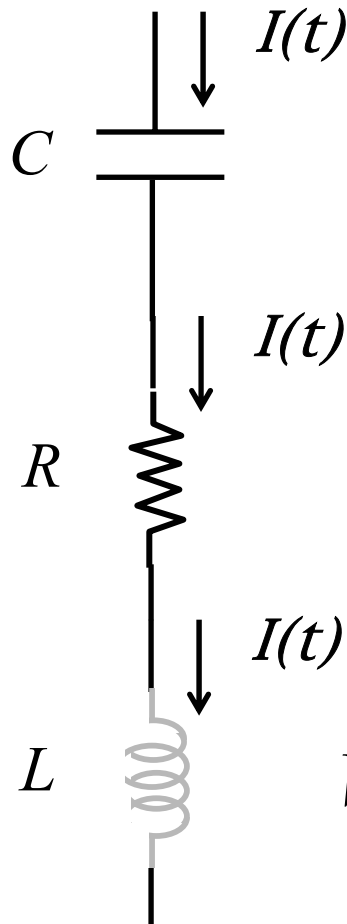Want to find voltage given a current, or find current if given a voltage.



$$V = \frac{Q}{C} = \frac{\int I dt}{C}$$

Voltage determined by *integral* of current and capacitance

capacitor "resists" integrated current

$$V = IR$$

Voltage determined by *current itself* and resistance


resistor "resists" current

$$V = L \frac{dI}{dt} = L \frac{d^2 Q}{dt^2}$$


Voltage determined by *derivative* of current and inductance

inductor "resists" change in current

Rules of Thumb for Inductors in Circuits

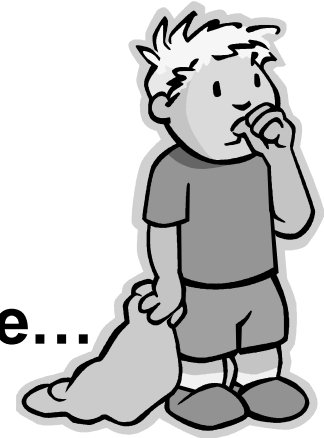

- After circuit has had a long time to settle...
 - What is di/dt ? Zero
 - So the EMF across the inductor is? Zero
 - So it acts like a wire (no potential difference)
- When something changes in the circuit
 - How much should I be allowed to change instantaneously? Not a lick!
 - What is the mechanism for opposing change? Provide an EMF!
 - How much EMF? IR
 - Change is exponential in time, $\tau = L/R$

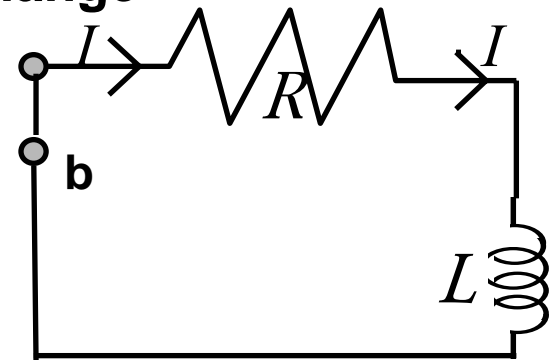


Energy in the *Electric* and *Magnetic* Fields

Energy stored in a capacitor ...

$$U = \frac{1}{2} C V^2$$

... energy density ...

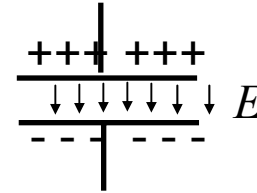


$$u_{\text{electric}} = \frac{1}{2} \epsilon_0 E^2$$

Energy stored in an inductor


$$U = \frac{1}{2} L I^2$$

... energy density ...

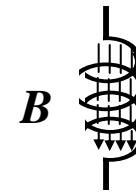

$$u_{\text{magnetic}} = \frac{1}{2} \frac{B^2}{\mu_0}$$

LC Oscillations

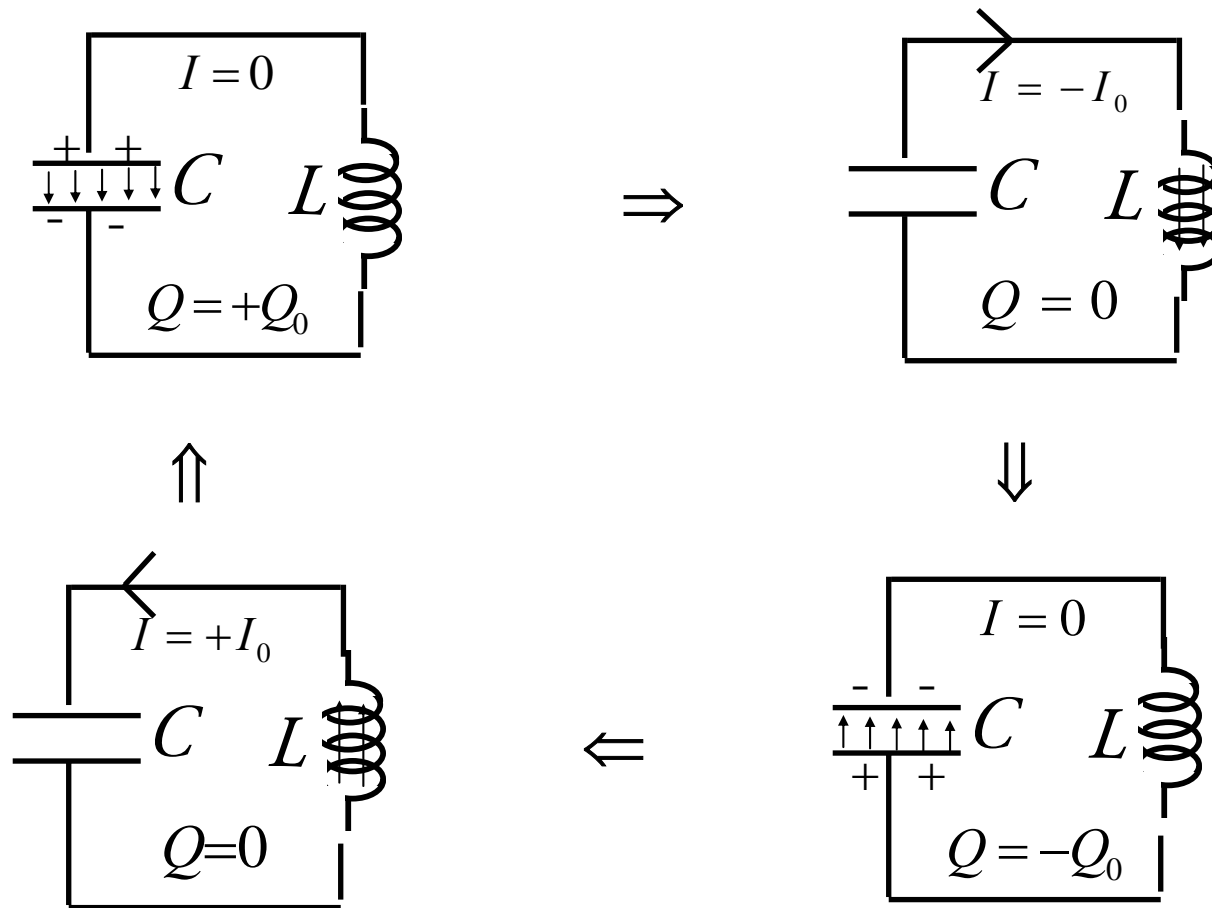

$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0 \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Response to an AC Voltage

- **R:** $V_R = RI_R = \varepsilon_m \sin \omega t \Rightarrow I_R = \frac{\varepsilon_m}{R} \sin \omega t$
 V in phase with I
- **C:** $V_C = \frac{Q}{C} = \varepsilon_m \sin \omega t \Rightarrow I_C = \omega C \varepsilon_m \sin(\omega t + 90^\circ)$
- **L:** $V_L = L \frac{dI_L}{dt} = \varepsilon_m \sin \omega t \Rightarrow I_L = \frac{\varepsilon_m}{\omega L} \sin(\omega t - 90^\circ)$
 V lags I by 90°
- **Voltage/Current relationship across a single circuit element can be divided into:** V leads I by 90°
 - magnitude

$I = \frac{\varepsilon_m}{\text{"X"}} \sin(\omega t - \phi)$

$X_L \equiv \omega L$

$X_R \equiv R$

$X_C \equiv \frac{1}{\omega C}$
 - relative phase
 - » leading, lagging

ELI the ICE man





Impedance Networks

$$Z_R = R = R(e^{i0}) \qquad Z_C = \frac{1}{i\omega C} = \frac{-i}{\omega C} = \frac{e^{-i\pi/2}}{\omega C}$$

$$Z_L = i\omega L = \omega L e^{i\pi/2}$$

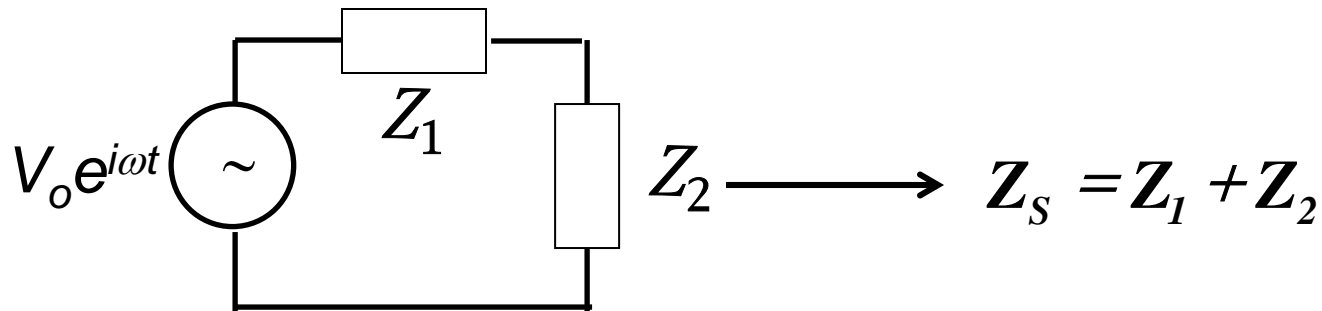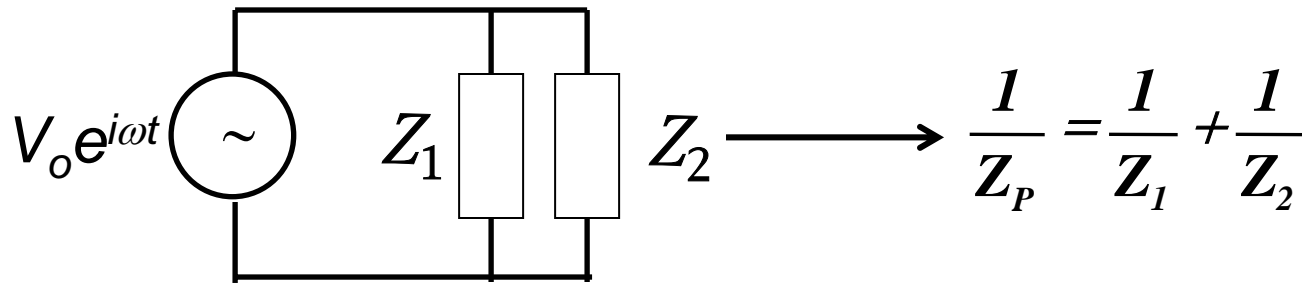- **Combining impedances in series and parallel is just as simple as it was with resistors**
 - But here impedances are complex numbers!




Resonance in LRC Series Circuit

$$V_{\max} = I_{\max} |Z_{eq}|$$

- So when does the current reach a maximum if the voltage and R , L , C are fixed?

$$|Z_{eq}| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

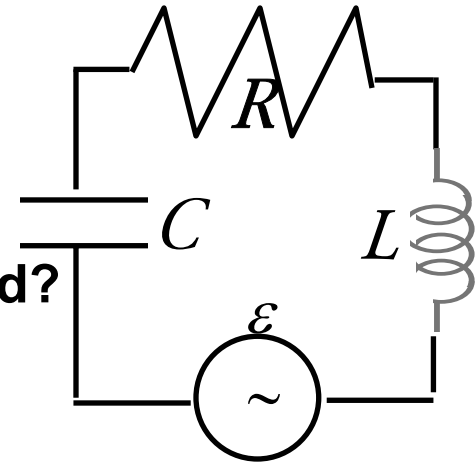

- The current I_{\max} will be a maximum at the resonant frequency ω_0 which makes the impedance Z purely real (R only)!

$$\text{i.e.: when } \omega_0 L - \frac{1}{\omega_0 C} = 0 \quad \text{or} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Power in LRC Circuit

- The power supplied by the *emf* in a series LRC circuit depends on the frequency ω (maximum power is supplied at the resonant frequency ω_0).
- Can calculate from either power supplied by generator or power dissipated in resistor

$$P(t) = \varepsilon(t)I(t) = (\varepsilon_m \sin \omega t)(I_m \sin(\omega t - \phi))$$

- average power delivered in a cycle.

$$\langle P(t) \rangle = \varepsilon_m I_m \langle \sin \omega t \sin(\omega t - \phi) \rangle$$

$$\varepsilon_{rms} \equiv \frac{1}{\sqrt{2}} \varepsilon_m$$

$$I_{rms} \equiv \frac{1}{\sqrt{2}} I_m$$

\Rightarrow

$$\langle P(t) \rangle = \varepsilon_{rms} I_{rms} \cos \phi$$

- so power delivered also depends on relative phase of voltage and current in the generator