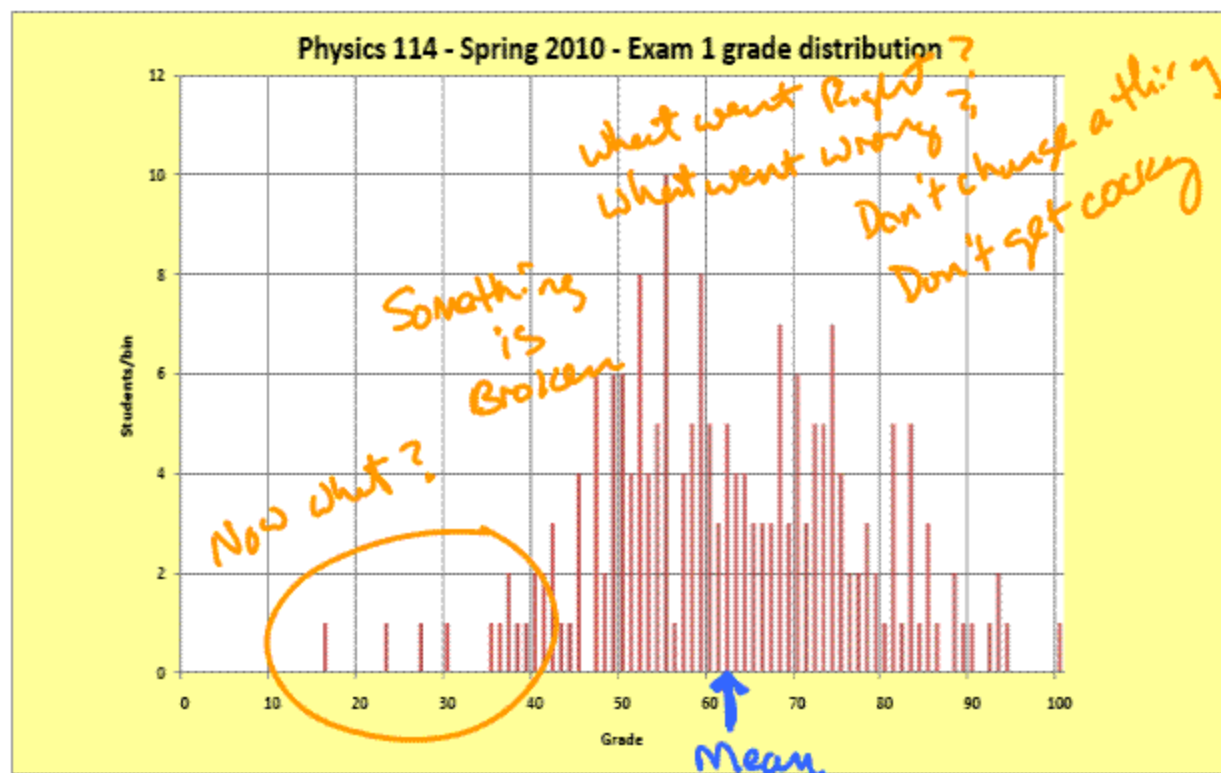


Physics 114 - February 18, 2010

- Feb 16 online lecture ... problems?
- Exam 1 graded - Pick up at end of class

mean ~ 62



- Solutions posted
- Trouble-Shooting guide
- Regrade policy
- EXAMS NOT picked up here → in box
by my office
- Syllabus provides some flexibility
but if change needed
change now

Last Time

$$\text{Energy required to charge a capacitor} = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV = U$$

Energy
density in
Electric field

$$u = \frac{\epsilon_0}{2} E^2$$

Linear dielectrics

$$\vec{E}_{\text{in Material}} = \frac{\vec{E}_{\text{external}}}{K}$$


Permittivity
of
free space

$$K\epsilon_0 \equiv \epsilon \equiv \text{permittivity}$$

$K > 1$
Dielectric constant

K, ϵ are
material
dependent

Was MISTAKE in this example - fixed now

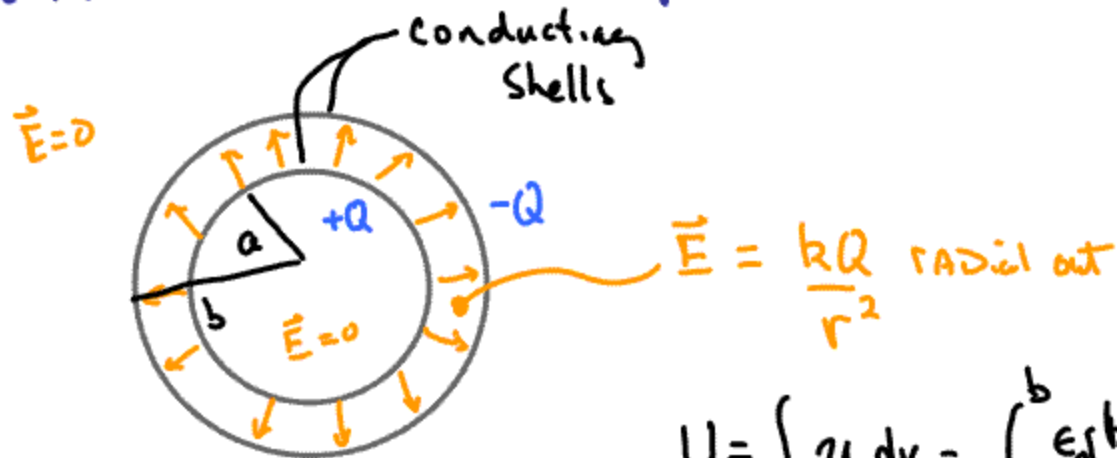

$$U = \int_{\text{Vol}} u \, dv = \int_a^b \frac{\epsilon_0}{2} \left[\frac{kQ}{r^2} \right]^2 4\pi r^2 dr$$

Total Energy Stored
in this configuration


$$U = \frac{\epsilon_0}{2} k^2 Q^2 4\pi \int_a^b r^{-2} dr$$

$$U = \frac{\epsilon_0}{2} k^2 Q^2 4\pi \left[-r^{-1} \right]_a^b$$

$$U = \frac{\epsilon_0}{2} k^2 Q^2 4\pi \left(\frac{1}{a} - \frac{1}{b} \right)$$

use $k = \frac{1}{4\pi\epsilon_0}$
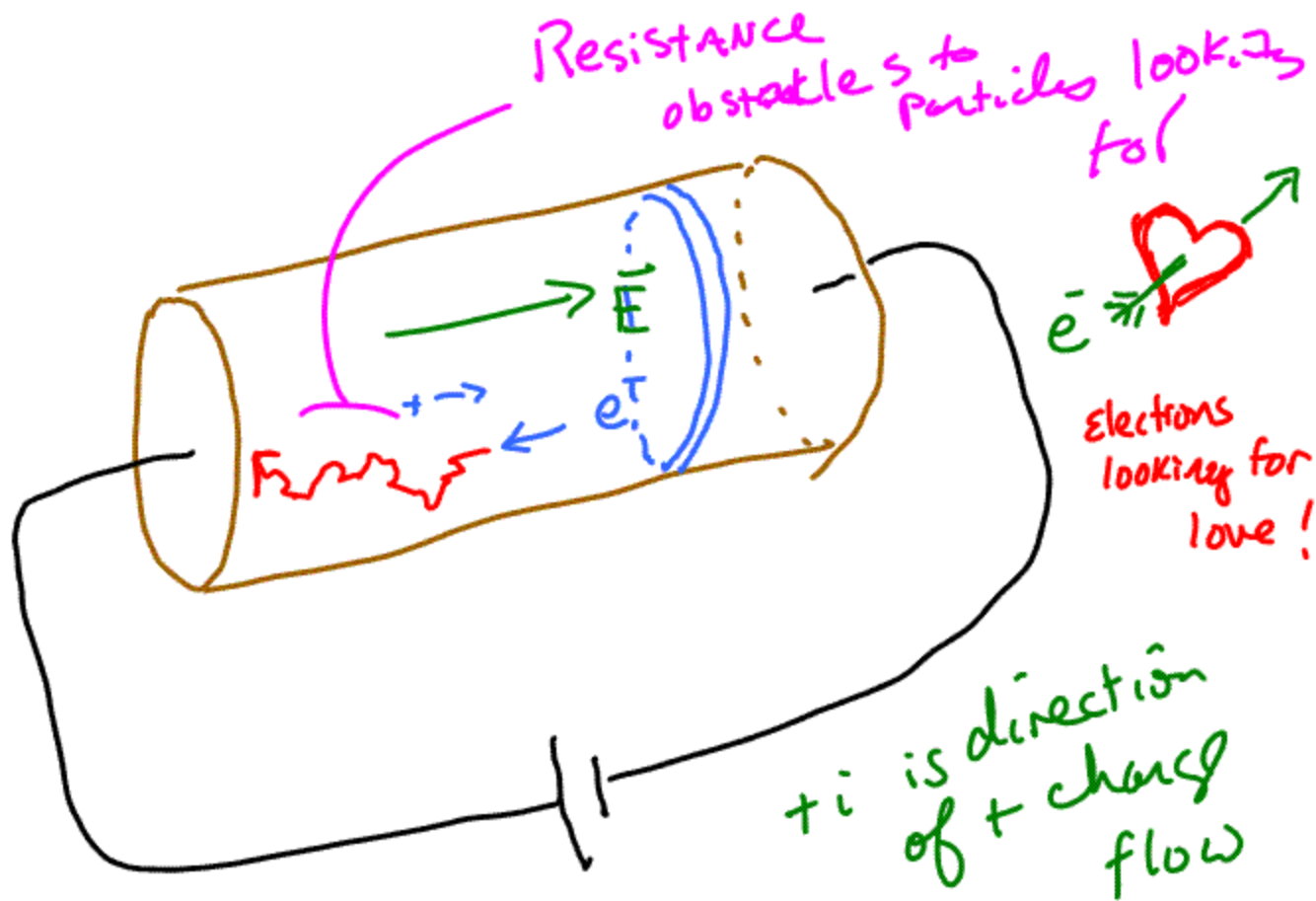
$$U = \frac{kQ^2}{2} \left(\frac{1}{a} - \frac{1}{b} \right)$$



$$\text{charges flow} = \frac{dq}{dt} \equiv i \equiv \text{current}$$


or I

$$\text{unit of Ampere} \equiv \frac{1 \text{ Coul}}{1 \text{ second}}$$



André Marie Ampère
(1775 - 1836)

French { mathematician
chemist
physicist

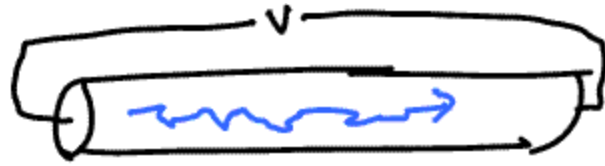


$$I \propto V$$

$$RI = V$$

$$V = IR$$

const of
proport.

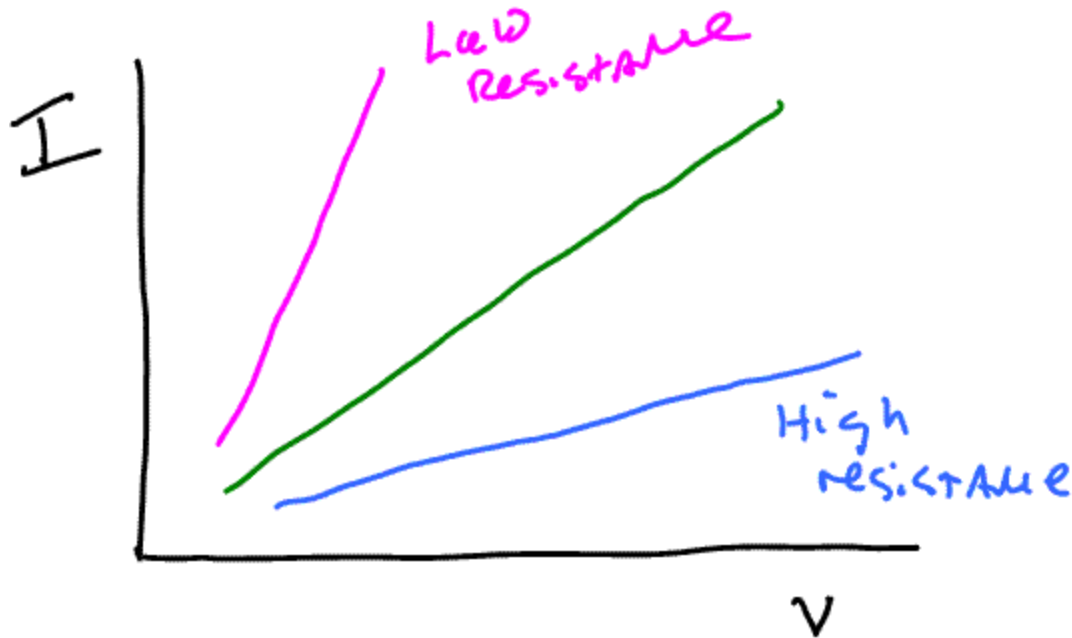

$$R = \Omega \equiv \text{ohm}$$

ohm's law

$$V = IR$$

Ohm's Law


Georg
Ohm



Resistance
Measured
in
Ohms

1 Ohm = 1 $\frac{\text{volt}}{\text{Ampere}}$
 Ω

1789-1854
German

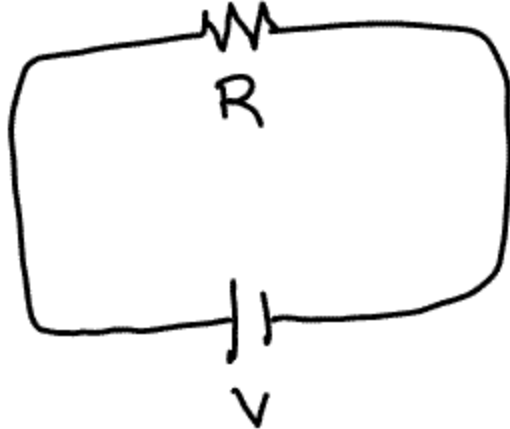

$$V = iR$$

$$V = \frac{W}{q} \quad \text{to get } q \text{ across resistor}$$

Voltage drop across resistor

$$W = qV \quad i \text{ thru resistor}$$

$$P \equiv \frac{dW}{dt} = \frac{dq}{dt} V = iV$$

Power $\left\{ \begin{array}{l} \text{rate work done to} \\ \text{shove } i \text{ thru resistor} \end{array} \right.$

Power Spent in resistor

→ heat and/or light

$$P = iV$$

$$V = iR$$

$$P = \frac{V^2}{R}$$

$$P = i^2 R$$

Resistors in Series




$$V = V_1 + V_2 + V_3 = iR_1 + iR_2 + iR_3 = i(R_1 + R_2 + R_3)$$

$$V = iR$$

$$R = R_1 + R_2 + R_3$$

$$R = \sum_i R_i$$

resistors
in
series

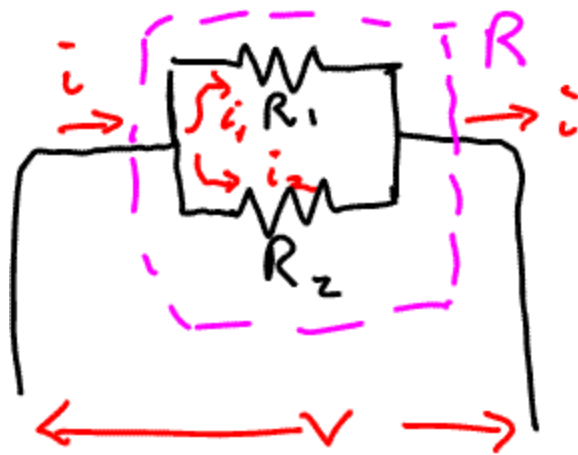

$$V = iR$$

$$V = i_1 R_1$$

$$V = i_2 R_2$$

$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R} = \sum_i \frac{1}{R_i}$$

Resistors
in
parallel

Gotchas
capacitors

$$\frac{1}{C} = \sum_i \frac{1}{C_i}$$

$$C = \sum_i C_i$$


series

Resistors

$$R = \sum R_i$$

$$\frac{1}{R} = \sum \frac{1}{R_i}$$

parallel

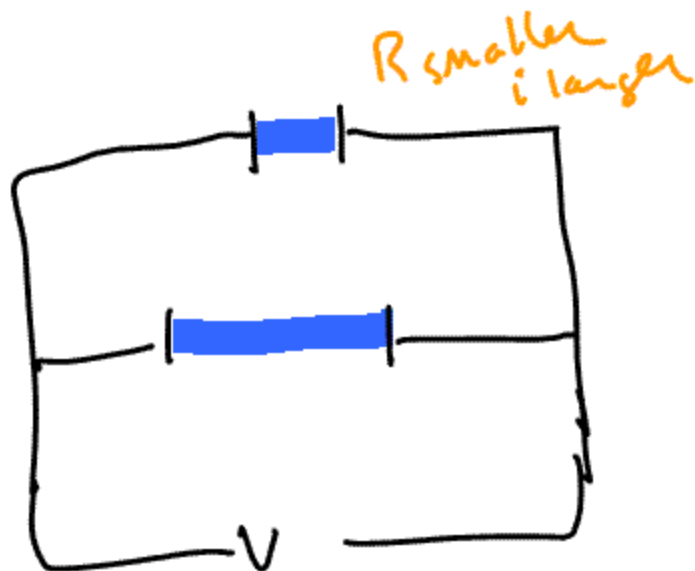

$$V = iR$$

$$P = i^2 R$$

Make V large — Which resistor (Nail)
Melts 1st?