

Physics 142 - October 27, 2005

Lenz's Law, mutual/self inductance

LR Circuits, LC circuits, AC Circuits

E-Mail

Class Web Server

Problem Set 7

What to do if ...

Last Time -

$$\mathcal{E} = \oint \vec{E} \cdot d\vec{\ell} = - \frac{d\Phi_m}{dt}$$

Important


$$\Phi_m \equiv \int_{\text{loop}} \vec{B} \cdot d\vec{A}$$

Faraday's Law


Lenz's Law - The induced current opposes the change that creates it



what is direction of induced current?

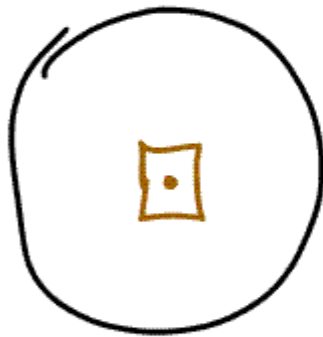

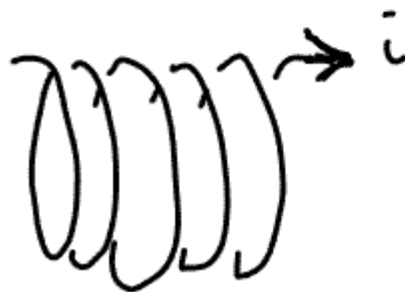magnet coming toward you
(on other side of board)



unit Henry


$$\Phi_m \propto i$$

self inductance

$$\Phi_m = L i$$

$$\mathcal{E} = - \frac{d\Phi_m}{dt} = - L \frac{di}{dt}$$

Circuit itself fights changes

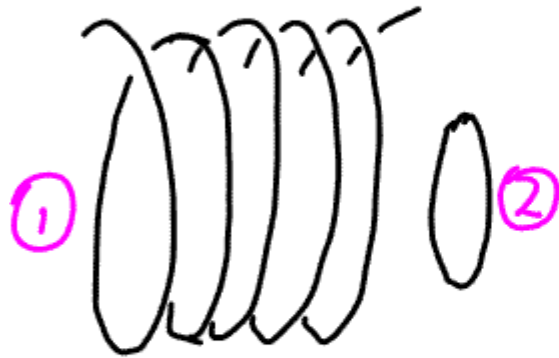

Δi in ①


ΔB in ②

L induces $\mathcal{E}$ ②

$$\phi_{m\text{②}} \propto i_{\text{①}} = L i$$

constant of
mutual inductance

Energy and Magnetic field

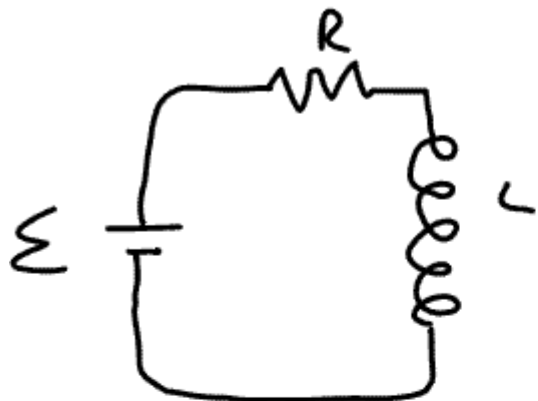

$$\mathcal{E} = iR + L \frac{di}{dt}$$

$$\mathcal{E}i = i^2 R + L i \frac{di}{dt}$$

Power out
of
EMF

Power
dissipated
in
Resistor

Power
in or out
of
inductor

$\mathcal{E}$ Stored in B field of inductor ↙

inductor $\frac{dU_B}{dt} = L i \frac{di}{dt}$

$$dU_B = L i di$$

$$U_B = \int_0^I L i di = \frac{1}{2} L I^2$$

Analogous
 $\frac{1}{2} C V^2$ from capacitors

Solenoid w/ i , n turns/length

Find Energy density of B field

$$B_{\text{solenoid}} = \mu_0 n i \quad (\text{inside})$$

$$= 0 \quad (\text{outside})$$

$$u_B \equiv \text{Energy density in } B \text{ field}$$

$$= \frac{U_B}{A l} = \frac{\frac{1}{2} L i^2}{A l}$$

$$\phi_m = L i \quad L = \frac{\phi_m}{i} = \frac{(BA)(nl)}{i}$$

$$L = \frac{\mu_0 n i A n l}{i} = \mu_0 n^2 A l$$


$$u_B = \frac{1}{2} \frac{\mu_0 n^2 A l i^2}{A l} = \frac{1}{2} \mu_0 i^2 n^2 = \frac{B^2}{2\mu_0}$$

Important

$$u_B = \frac{B^2}{2\mu_0}$$

Analogous to
 $u_E = \frac{1}{2} \epsilon_0 E^2$

LR Circuit

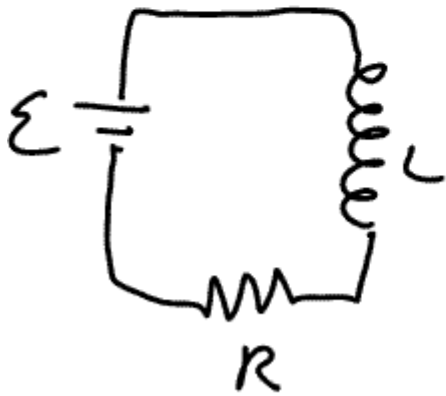


$$\mathcal{E} - L \frac{di}{dt} - iR = 0$$

$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-\frac{tR}{L}} \right)$$


Similar to RC charging
 circuit

$$RC = \tau_c$$

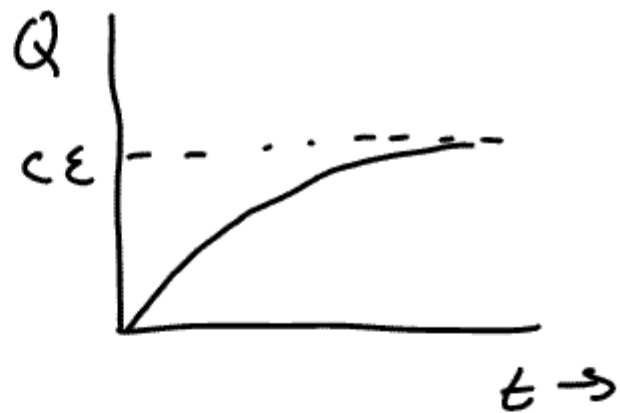

$$Q = c\epsilon (1 - e^{-t/RC})$$

LR circuit

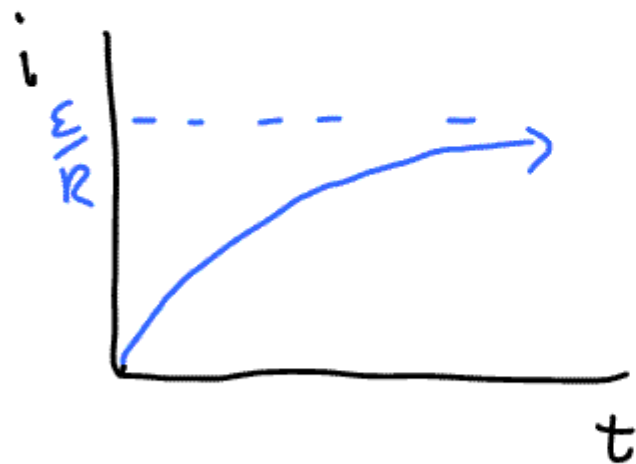

Inductive
Time Constant

$$\frac{L}{R} = \tau_L$$

$$V = iR$$

across inductor


$$V = \epsilon (1 - e^{-\frac{tR}{L}}) = \epsilon (1 - e^{-t/\tau_L})$$

Remove EMF, Short L across R




$$0 = iR + L \frac{di}{dt}$$
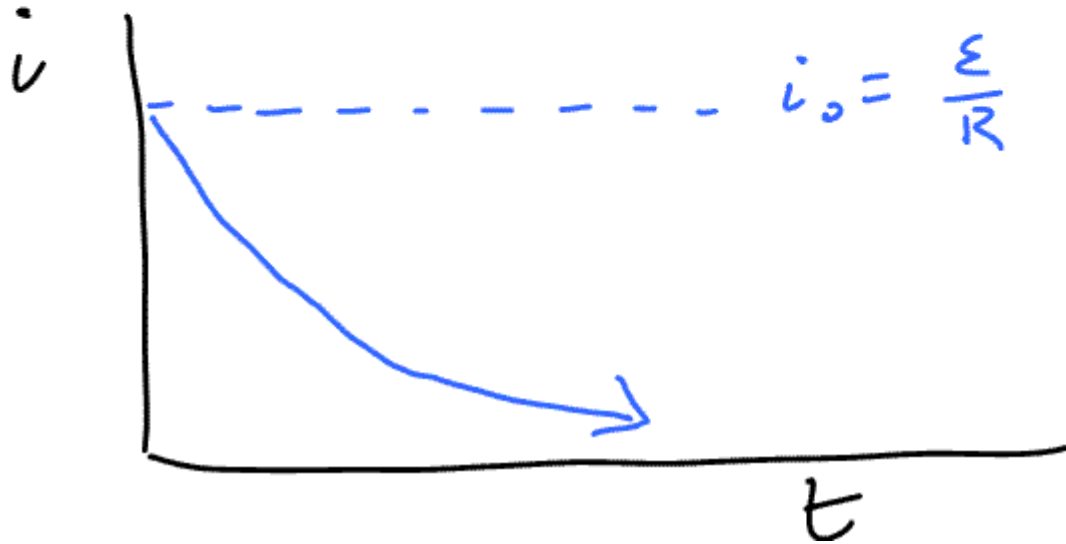
$$i = \frac{\mathcal{E}}{R} e^{-t/\tau_L} = i_0 e^{-t/\tau_L}$$



LC circuit

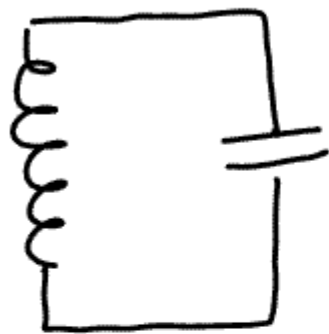

$$U = U_B + U_E = \frac{1}{2} Li^2 + \frac{q^2}{2C}$$

R in circuit $\rightarrow 0$

$$\frac{dU}{dt} = 0 = \frac{1}{2} L 2i \frac{di}{dt} + \frac{2q}{2C} \frac{dq}{dt}$$

$$0 = L \frac{dq}{dt} \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt}$$

$$0 = L \frac{d^2 q}{dt^2} + \frac{q}{C}$$

differential Eqn

$$\text{Soln} \rightarrow q(t) = Q \cos(\omega t + \phi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$

Harmonic dependence

Energy flow

$$U_E = \frac{q^2}{2C} = \frac{Q^2}{2C} \cos^2(\omega t + \phi)$$

$$\frac{dq}{dt} = i = -Q\omega \sin(\omega t + \phi)$$

$$U_B = \frac{1}{2} L i^2 = \frac{L}{2} Q^2 \omega^2 \sin^2(\omega t + \phi)$$

