


Physics 142 - October 4, 2005

Current Kirchhoff's Laws

EXAM 1 - Thurs. Oct 6, 2005 at 0800, B+L109

Last Time -

- Dielectrics

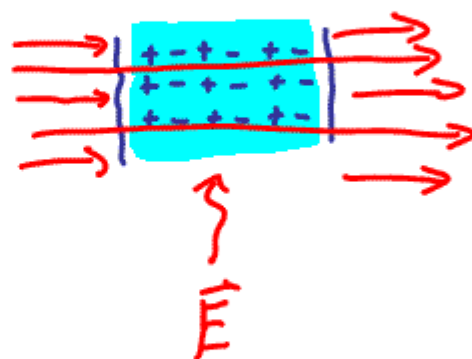

$\vec{E}_0$
Sometimes called
"free" field

$$\vec{E} = \frac{\vec{E}_0}{K}$$

$K \equiv$ dielectric constant > 1

$$\frac{1}{K} = \epsilon \equiv \text{permittivity}$$

- current

$$I \text{ or } i = \frac{dq}{dt}$$

+ is direction of + charge
flow

- Resistance

$$V = IR$$

Ohm's
Law

Resistance

Impedes electrons "Looking" for love 

Pass current thru resistor - Energy lost as heat
or light


Power dissipated $\equiv P = iV = i^2R = i^2R$ Mostly

$$P = i^2R$$

$$V = iR$$


$$i = V/R$$

$$P = \frac{V^2}{R}$$

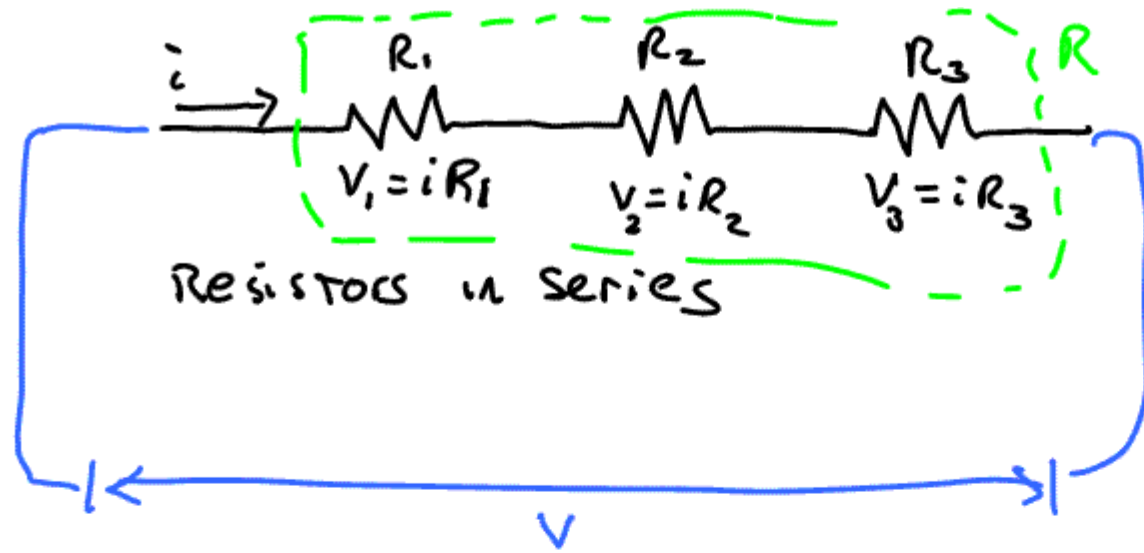

$$V = V_1 + V_2 + V_3 = iR_1 + iR_2 + iR_3 = i(R_1 + R_2 + R_3) = iR$$

Resistors
in
Parallel

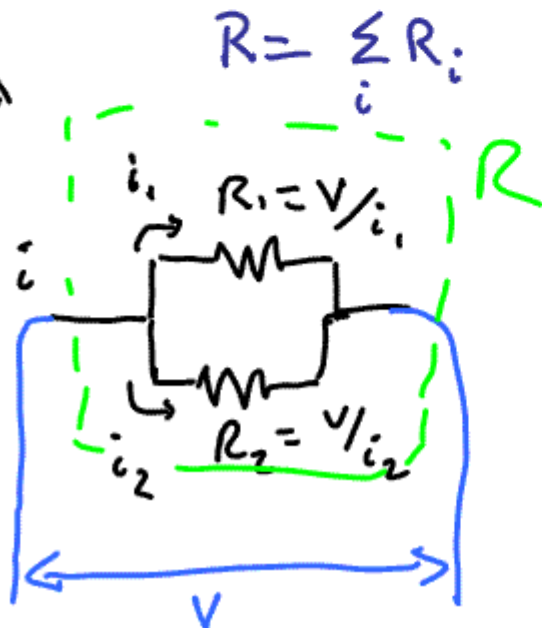


$$V = iR \quad \frac{i}{V} = \frac{1}{R}$$

$$i = i_1 + i_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$\frac{1}{R} = \sum \frac{1}{R_i}$$

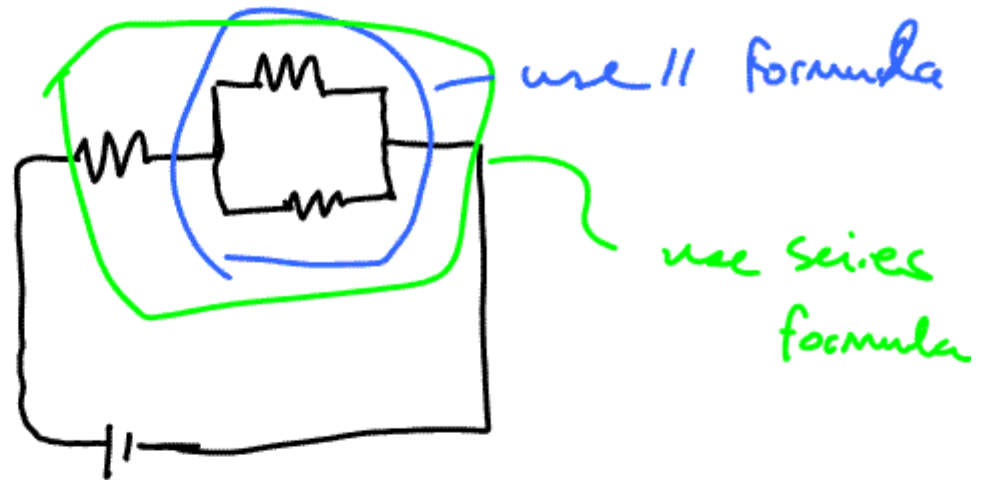

Batteries + EMF $\equiv$ Electromotive force
Generators

Maintain constant V across terminals

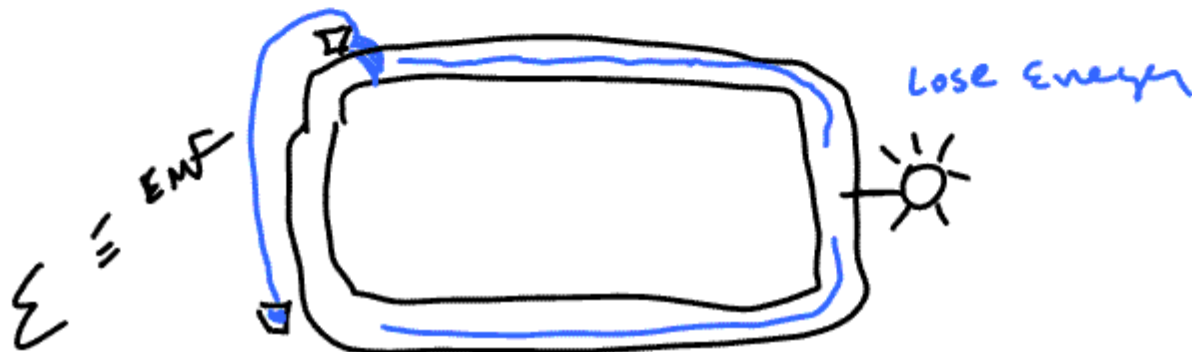

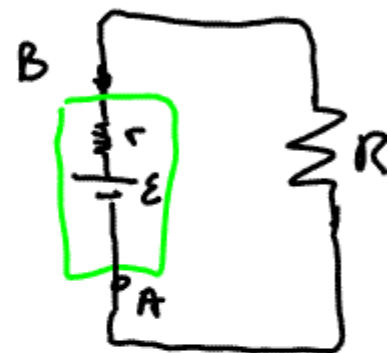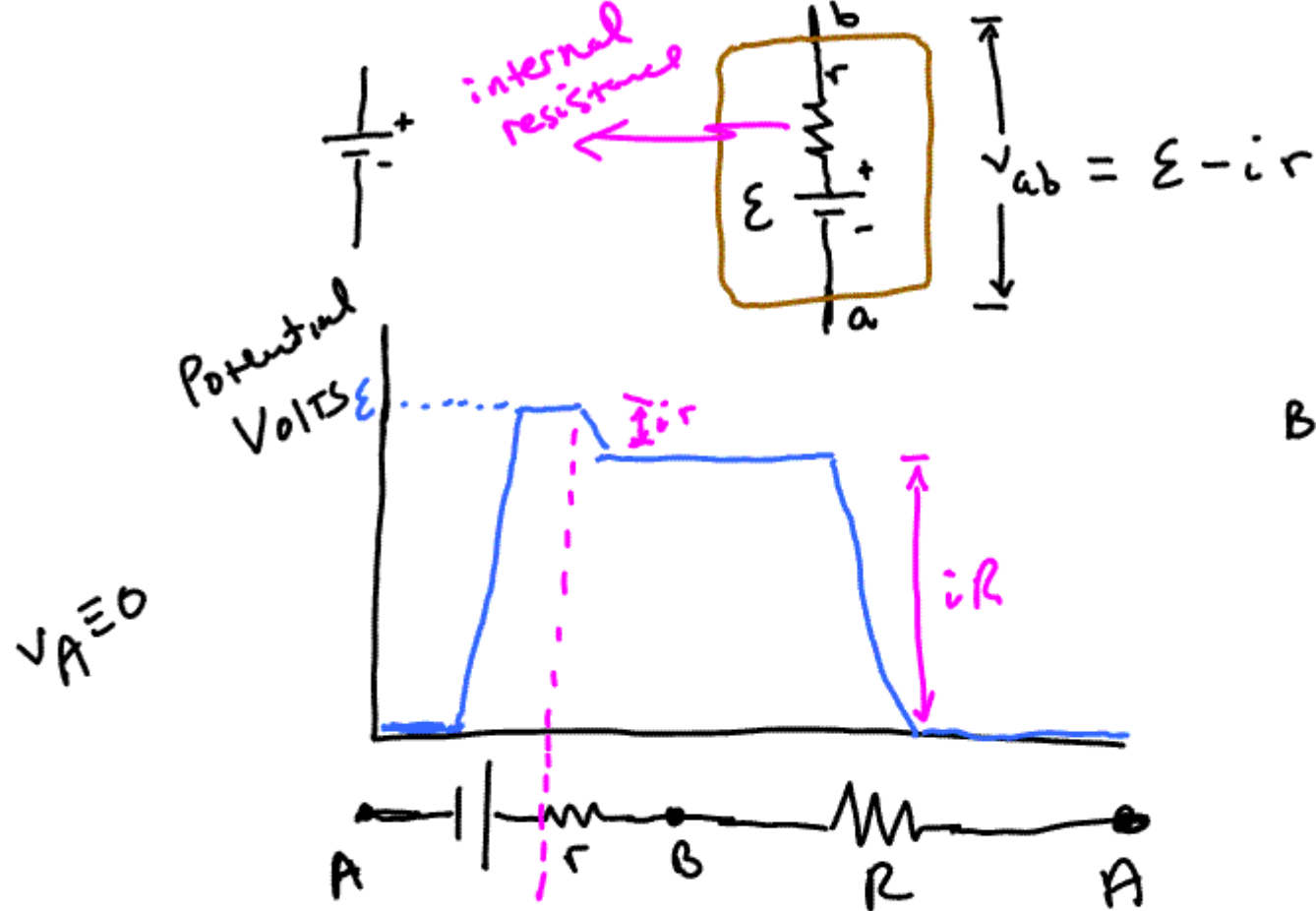

DC circuits


Direct Current

V is STATIC

AC circuit

Alternating current

later

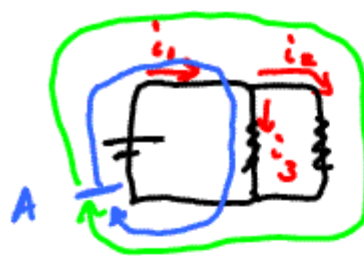

$$i_1 = i_2 + i_3$$

Kirchoff's rules:



- 1) When any closed-circuit loop is traversed, the algebraic sum of the changes in potential encountered along the way is zero.
- 2) At any point where current can divide, current is conserved.

Conventions

ΣV across loop in circuit = 0

$$\mathcal{E} - iR = 0$$

$$\mathcal{E} = iR$$

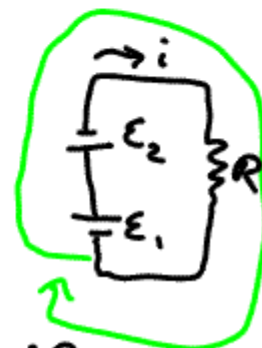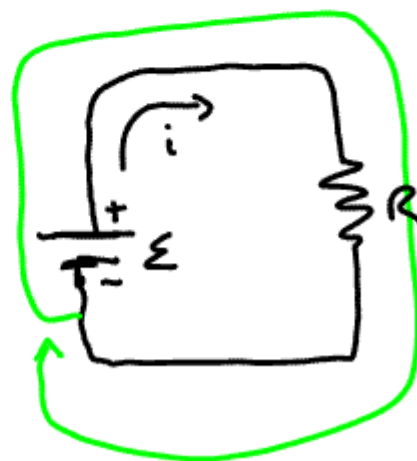


$$\mathcal{E}_1 - \mathcal{E}_2 - iR = 0$$

chosen loop

- TRAVERSE $\mathcal{E}$ in direction of $\mathcal{E} \rightarrow \mathcal{E} \text{ is } \oplus$
- " " in opposite " " $\rightarrow \mathcal{E} \text{ is } \ominus$
- TRAVERSE R in direction of current thru resistor
then "ir drop" or iR comes in as $\ominus$
- " " R in opposite direction of current " "
" " iR comes in as $\oplus$

ohmian p 711 - Branch Method

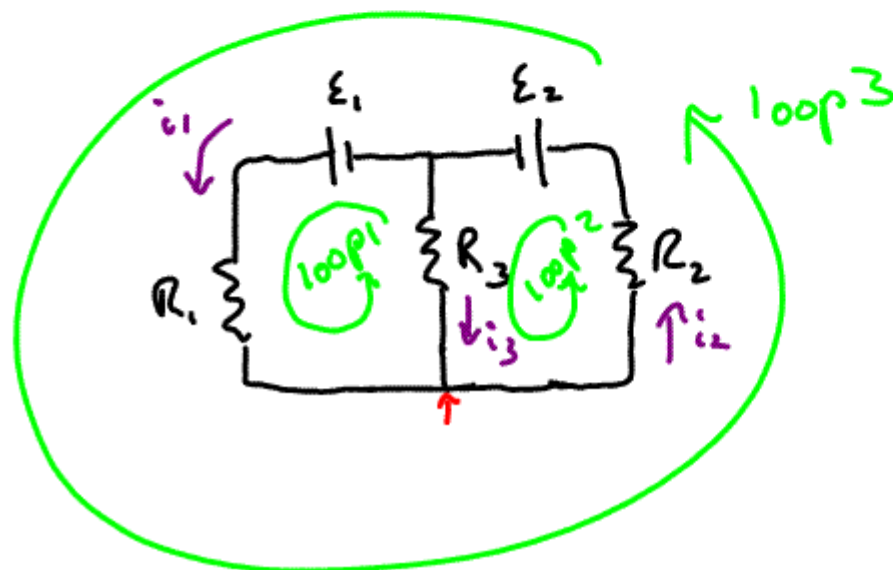

KNOW $\mathcal{E}_1, \mathcal{E}_2$

R_1, R_2, R_3

WANT currents
throughout
circuit

K's Second Law at red arrow

$$\sum \dot{i}_i = i_1 + i_3 - i_2 = 0$$

1 eqn

K's 1st Law

loop 1
start lower left
corner

$$i_3 R_3 + \mathcal{E}_1 - i_1 R_1 = 0$$

Eqn 2

~~Loop 2~~

$$-\mathcal{E}_2 - i_3 R_3 - i_2 R_2 = 0$$

Eqn 3