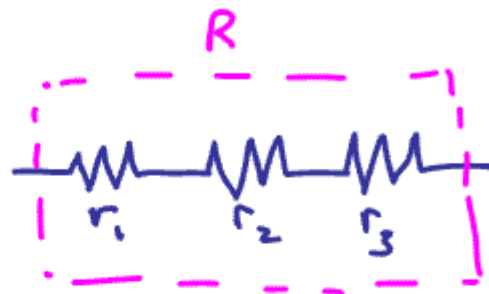


Physics 142 - October 6, 2005

DC circuits, Relativity


Last Time -

Resistors in Series



$$R = \sum r_i$$

Resistors in Parallel

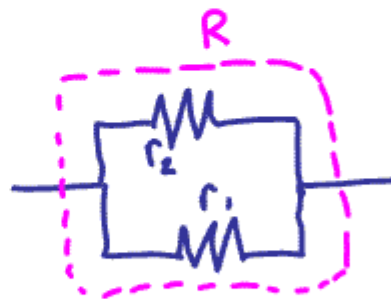

$$\frac{1}{R} = \sum \frac{1}{r_i}$$

Kirchoff's Rules:

- ① $\sum V = 0$ around closed loop in circuit
- ② current is conserved at any BRANCH point in circuit

use these rules to create N independent equations
to solve for N unknowns

Convention [told this is opposite that of ECE 210]
↳ no matter if consistent

Choose currents in each branch (arbitrary)

Sum ΔV across each circuit component as you go
around an imaginary closed loop in the circuit

$\Delta V -$ if 

$\mathcal{E} +$ if 

$\Delta V +$ if 

$\mathcal{E} -$ if 

Get N eqns, N unknowns and solve

Tedious $\rightarrow$ must be careful and consistent
w/ conventions and signs

Voltmeter - Meas. pot. difference between 2 pts in


a circuit



(V) has a huge resistance

Always connected in //

Ammeter - Meas. current flow in circuit

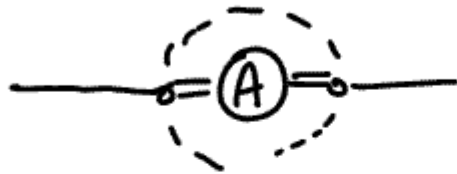


low resistance

All current passes thru

RC circuit (still DC)


Resistor

Capacitor

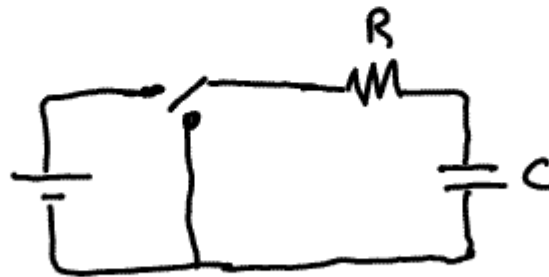

Switch in up position
charging capacitor

$$\sum V = 0$$




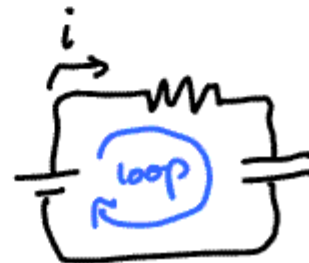



$$\underbrace{\varepsilon}_{V_R} - i \underbrace{R}_{V_C} - \frac{q}{C} = 0$$

$$q(t), \quad i = \frac{dq}{dt}$$

$$\varepsilon = \frac{dq}{dt} R + \frac{q}{C} \quad \rangle \text{ differential Equation}$$

$$q = C\varepsilon(1 - e^{-t/RC})$$

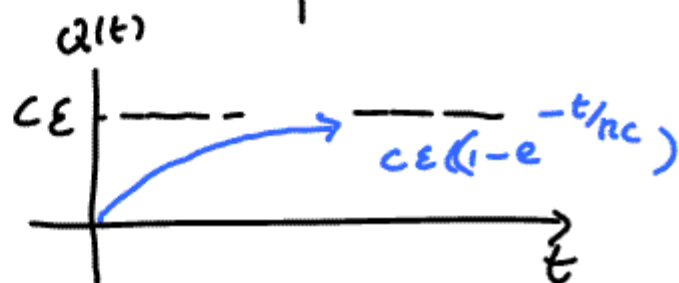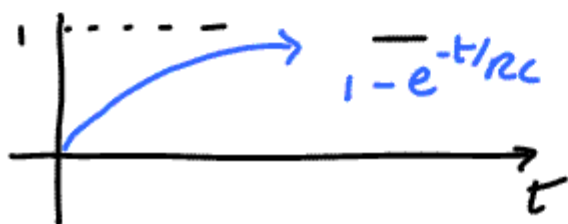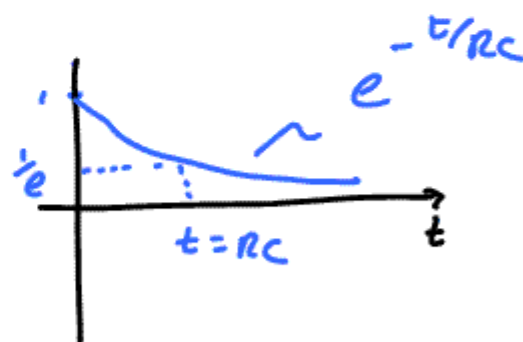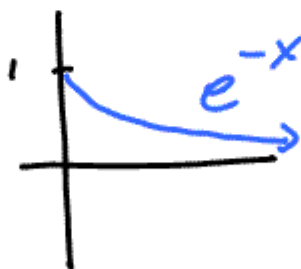

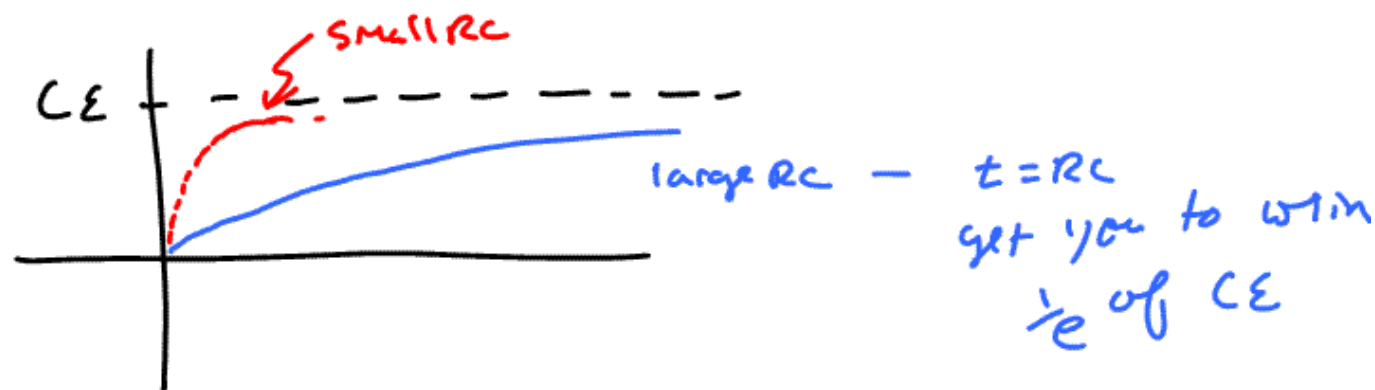

$RC \equiv$ Time Constant of circuit

Throw switch down after C is charged




SAME thing as earlier but $\epsilon = 0$

$$\frac{q}{C} = - \frac{dq}{dt} R$$

$$\int_0^t \frac{dt}{RC} = - \int_{q_0}^q \frac{dq}{q}$$

$$\frac{t}{RC} = - \ln \frac{q}{q_0}$$

$$q_0 e^{-t/RC} = q$$

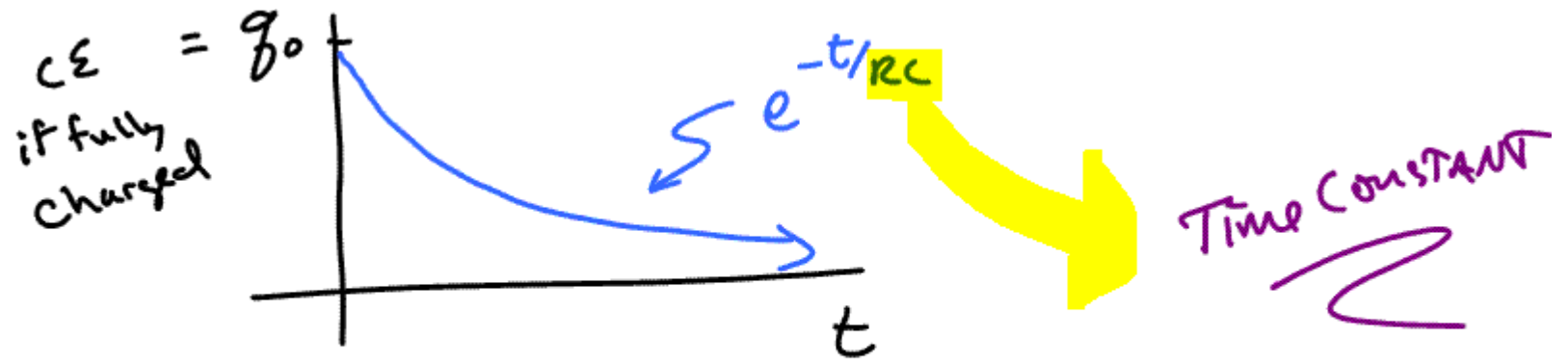

Relativity - See introductory ppt files