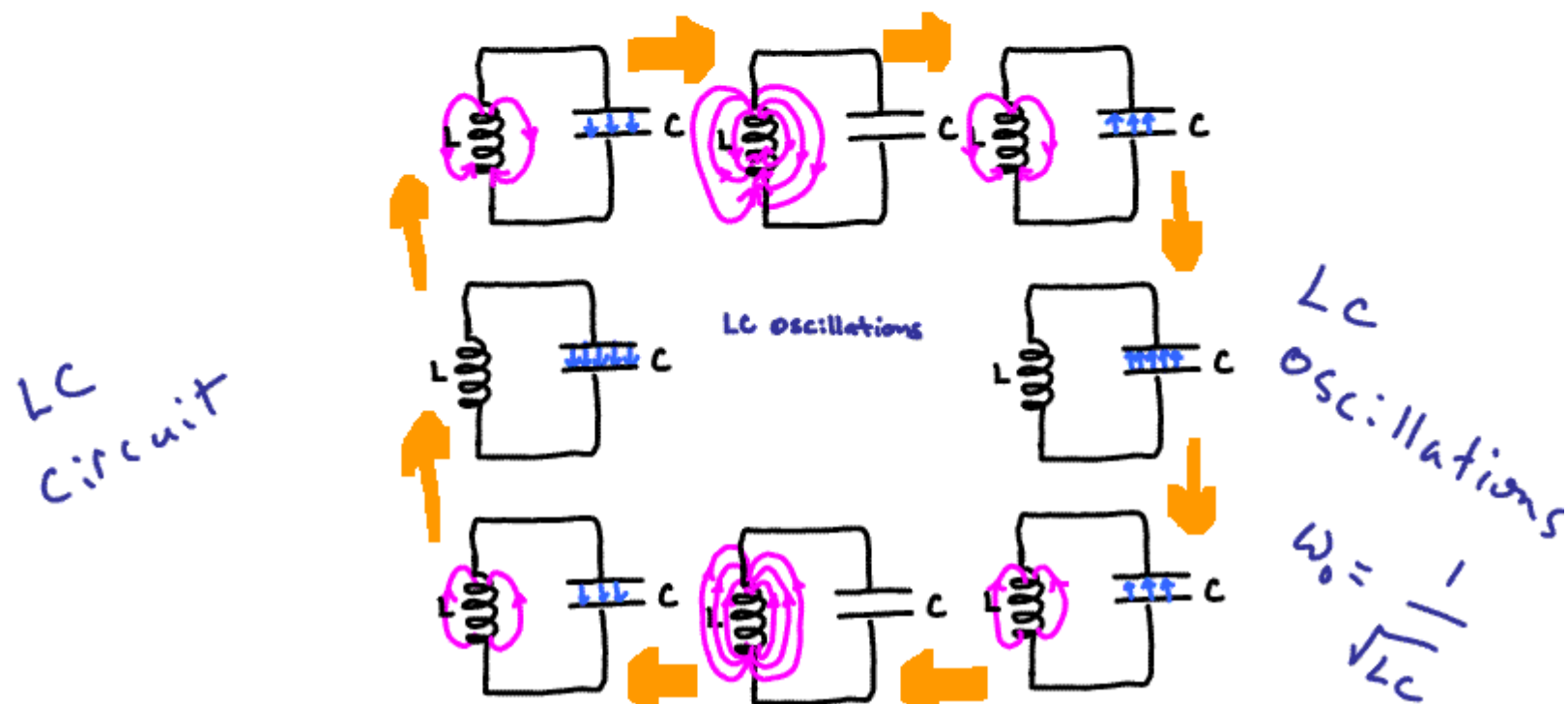


Physics 142 - November 1, 2005

AC circuits, Magnetic fields in Materials

Last time - U_B = Energy density in B field

$$U_B = \frac{B^2}{2\mu_0}$$



AC Circuits



$$\mathcal{E} = \mathcal{E}_{\max} \sin \omega t$$


Kirchoff

$$\mathcal{E} - IR = 0$$

$$I = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{\max} \sin \omega t}{R}$$


Instantaneous
Power
Dissipation
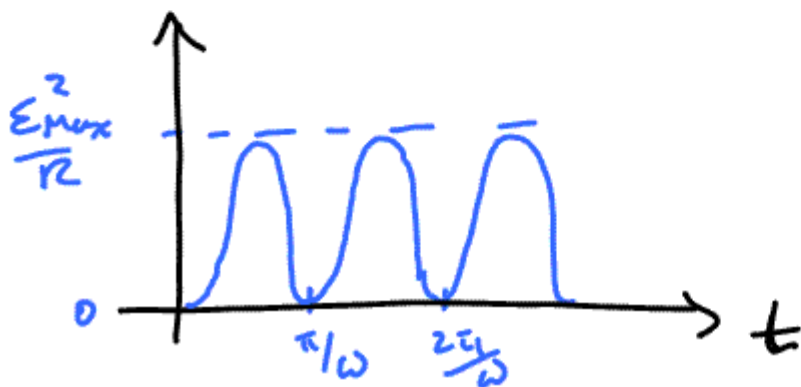
$$P = IV = I\mathcal{E} = \frac{\mathcal{E}_{\max}^2}{R} \sin^2 \omega t$$



$$\overline{\sin^2 \theta} \rightarrow \frac{1}{2}$$
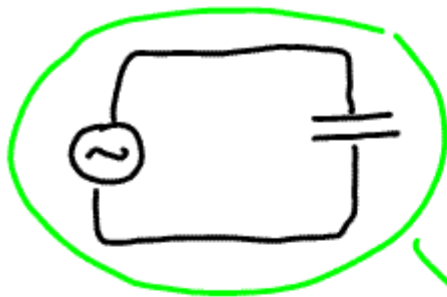
$$\text{Ave power} \quad \bar{P} = \frac{\mathcal{E}_{\max}^2}{2R}$$





$$Q = C \varepsilon = C \varepsilon_{\max} \sin \omega t$$

$$I = \frac{dQ}{dt} = \omega C \varepsilon_{\max} \cos \omega t$$



ε, I in phase

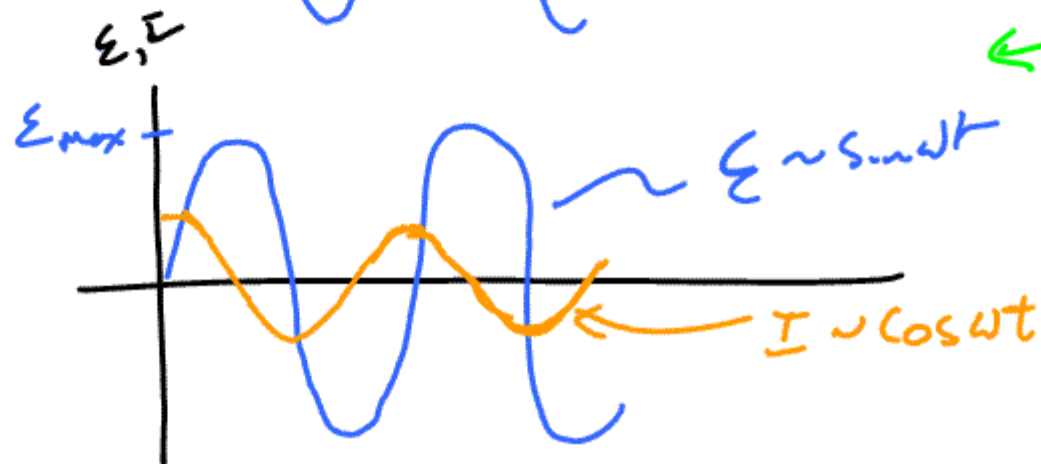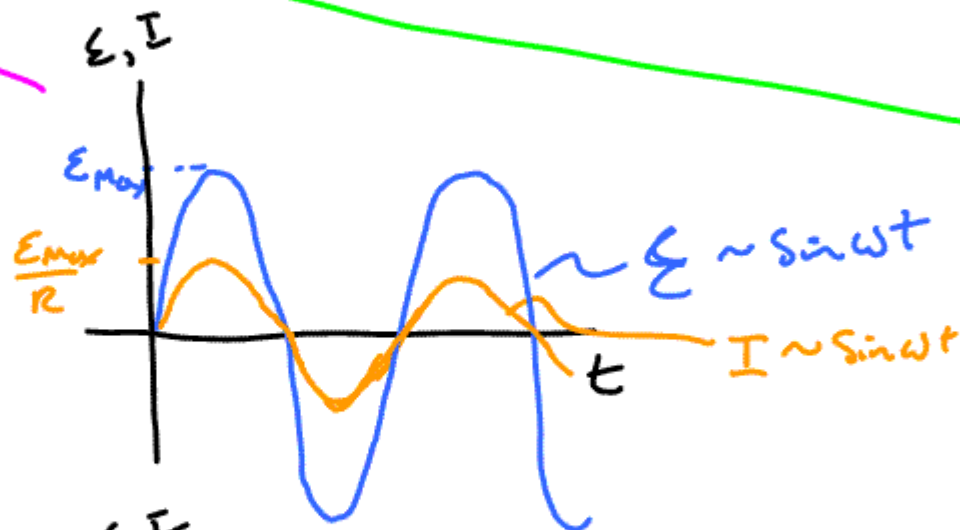

I leads ε by $\frac{1}{4}$ period

$$\frac{I}{\omega C} = \varepsilon_{\max} \cos \omega t \quad \leftarrow \text{plays role of } R \text{ in Capacitive AC Circuit}$$


$$\frac{1}{\omega C} \equiv X_C = \text{Capacitive Reactance}$$




$$\varepsilon - L \frac{dI}{dt} = 0$$

$$\frac{d\varepsilon}{dt} = \frac{\varepsilon_{\max}}{L} \sin \omega t$$

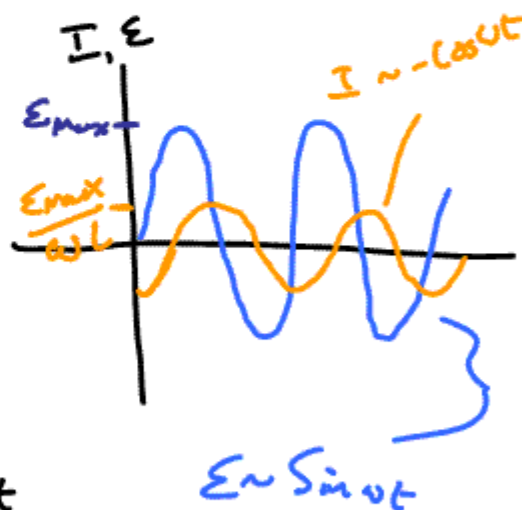
$$I = - \frac{\varepsilon_{\max}}{\omega L} \cos \omega t$$


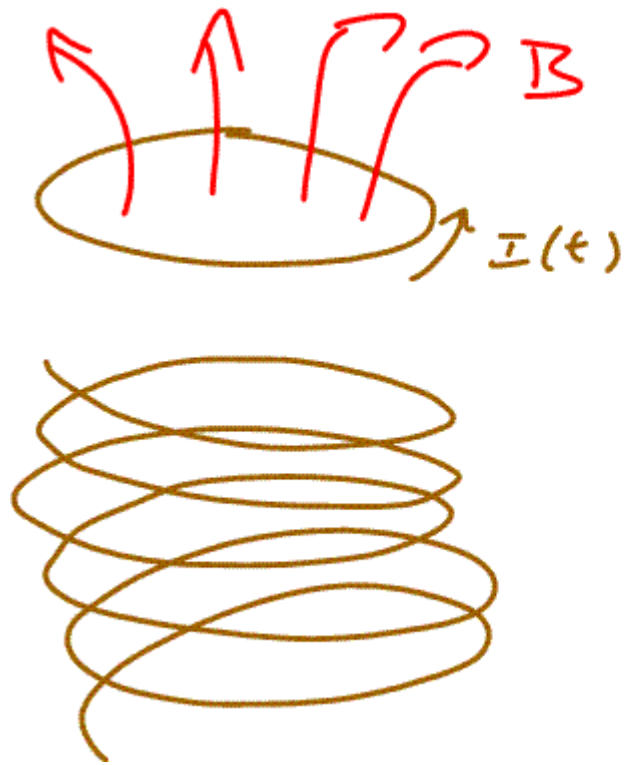
$$X_L \equiv \omega L \equiv \text{Inductive Reactance}$$



Transformer

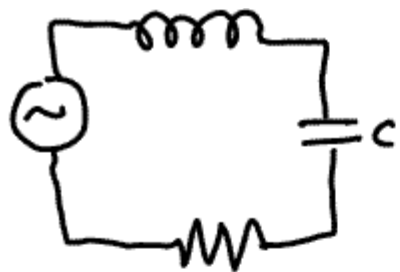

LRC circuit

$$\mathcal{E} = \mathcal{E}_{\max} \sin \omega t$$

$$I = I_{\max} \sin(\omega t + \phi)$$

$$\mathcal{E} = \Delta V_R + \Delta V_C + \Delta V_L$$

$$I_{\max} R \sin(\omega t + \phi)$$

$$+ X_C I_{\max} \cos(\omega t + \phi)$$

$$+ X_L I_{\max} \cos(\omega t + \phi)$$

Math  Trig ID's

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$I_{\max} = \frac{\varepsilon_{\max}}{\sqrt{R^2 + (X_L + X_C)^2}}$$

$\equiv Z \equiv \text{Impedance} \rightsquigarrow$ plays role of R in LRC circuit


$$\textcircled{2} \rightarrow \omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{Natural frequency}$$

$$\omega \rightarrow \omega_0$$

$$Z \rightarrow \frac{\varepsilon_{\max}}{\sqrt{R^2 + \left(\frac{L}{\sqrt{LC}} - \frac{\sqrt{LC}}{C} \right)^2}}$$

$$\rightarrow 0$$

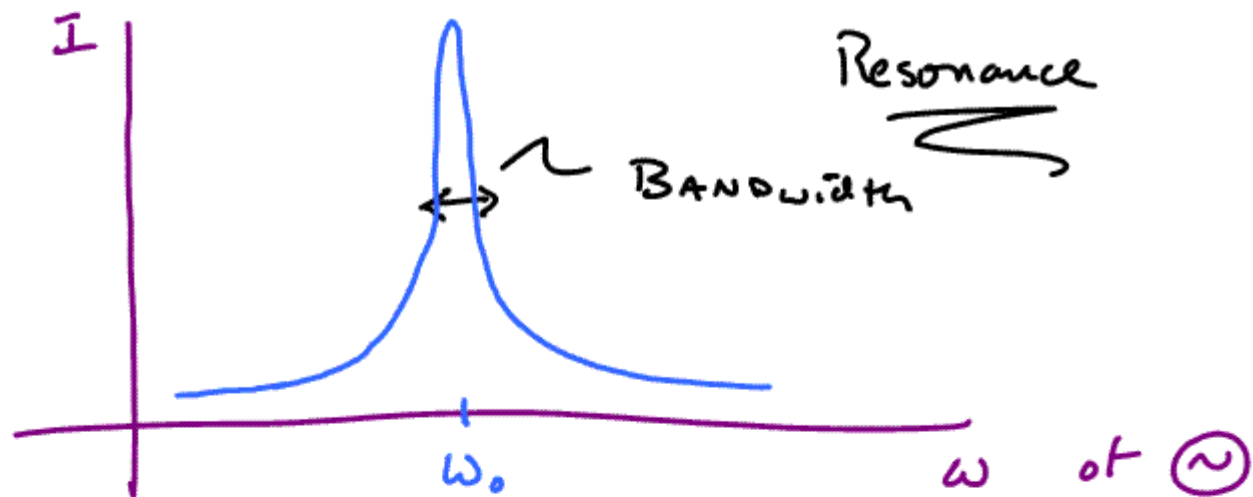

Magnetic fields in Matter



$$I = \frac{e}{2\pi r/v} = \frac{ev}{2\pi r}$$

$$\text{Current loop (Area } A) \equiv \mu \equiv \text{Magnetic Moment} \\ = IA$$

↳ x-sectional Area
current subtends

$$\mu_e = \frac{ev}{2\pi r} (\pi r^2) = \frac{evr}{2}$$

$$L \equiv \text{Angular Momentum} = mvr \quad \mu_e = \frac{eL}{2m_e}$$

$$\text{Bohr} \rightarrow L = 0, \hbar, 2\hbar, \dots$$

$$\mu_e = \# \frac{e\hbar}{2m_e} \cdot$$

Bohr Magneton