

15. LCR Oscillators

S. G. Rajeev

March 17, 2009

We studied how direct current flows in a circuit that has a resistance and a capacitor. As we turn the circuit on, the current decreases to zero rapidly. We will study a new kind of circuit where the current oscillates: it increases to a positive value then decreases to a negative value and so on, back and forth in time. These oscillators are the basis of many devices that we use every day. The tuner in your TV or radio is an example, as are electronic watches. In most modern devices, the oscillations are regulated using additional components like transistors or crystals. We will study only the most basic example with inductance, capacitance and a resistance.

1 Inductance

We saw that a coil carrying an alternating current can induce an electromotive force on a nearby coil: it can drive a current on it. This e.m.f. on the second coil \mathcal{E}_2 is proportional to the derivative of the current on the first coil: if the current is constant there is no induction. Thus

$$\mathcal{E}_2 = -M \frac{dI_1}{dt}.$$

This constant M is called the mutual inductance of the two coils. Using Faraday's law we can derive a formula for it

$$M = \mu A \frac{N_1 N_2}{l}$$

where A is the cross-sectional area the two coils share, l the length of the coils and N_1, N_2 the number of turns on them. Also, μ is the magnetic permeability of the material inside the coils. Of course, the second coil will induce an e.m.f. on the first as well.

$$\mathcal{E}_1 = -M \frac{dI_2}{dt}.$$

Any time that magnetic flux across the area enclosed by a wire changes, there will be an induced e.m.f. on it. Thus a varying current can induce an e.m.f. even on the wire carrying it: this is called self-inductance. By Lenz's law, the sign of this e.m.f. will be such that it opposes the change of the current. So

$$\mathcal{E} = -L \frac{dI}{dt}.$$

The constant L , called self-inductance (shortened to inductance) has a formula as well, derived from Faraday's law

$$L = \mu A \frac{N^2}{l}.$$

Again N is the number of turns in the coil, l its length and A the area. To have a large inductance, the coil can be filled with a material with a large magnetic permeability (like iron). The unit of inductance is Henry. Clearly a Henry is the same as Volts.(1/Amperes).secs.

1.1 An Example

A 3.81 m-long coil containing 225 loops is wound on an iron core (average $\mu = 1850\mu_0$) along with a second coil of 115 loops. The loops of each coil have a radius of 1.00 cm. The mutual inductance is

$$M = \mu A \frac{N_1 N_2}{l} = 1850 \times 4\pi \times 10^{-7} \pi (0.01)^2 \frac{225 \times 115}{3.81} = 4.96 \times 10^{-3} H$$

The self inductance of the first coil is

$$L_1 = \mu A \frac{N_1^2}{l} = 1850 \times 4\pi \times 10^{-7} \pi (0.01)^2 \frac{225^2}{3.81} = 9.7 \times 10^{-3} H$$

while that of the second coil is

$$L_2 = \mu A \frac{N_2^2}{l} = 1850 \times 4\pi \times 10^{-7} \pi (0.01)^2 \frac{115^2}{3.81} = 2.53 \times 10^{-3} H.$$

2 An LC Circuit

Inductance represents the inertia of an electric current. The more the inductance, the more it will oppose changes in the current. An inductor is happiest (has no induced e.m.f.) when it has a constant current flowing through it.

A Capacitor on the other hand, is in a hurry to get rid of the electric charge stored in it: it is happiest (has zero e.m.f.) when it carries no charge. By putting an inductance and a capacitance together we can trick them into oscillating back and forth between their states of maximum and minimum e.m.f. In any real circuit, the wires carrying the current will have some resistance. But as a first step we ignore this and consider an ideal circuit with only L and C . Also, as a first step we assume there is no external e.m.f. applied: no battery or AC power source.

The e.m.f. of the inductance and the capacitance must add up to zero

$$-L \frac{dI}{dt} + \frac{Q}{C} = 0.$$

But recall that current is the rate of discharge of the charge on the capacitor Q :

$$I = -\frac{dQ}{dt}.$$

Combining these we get

$$\frac{dI}{dt} = \frac{1}{LC}Q$$

$$\frac{dQ}{dt} = -I.$$

This pair of differential equations can be solved in terms of familiar functions. What is a pair of functions so that the derivative of one is a constant times the other? Recall that

$$\frac{d \sin \theta}{d\theta} = \cos \theta$$

$$\frac{d \cos \theta}{d\theta} = -\sin \theta$$

So for a constant ω ,

$$\frac{d \sin \omega t}{dt} = \omega \cos \omega t$$

$$\frac{d \cos \omega t}{dt} = -\omega \sin \omega t$$

This looks a little more like what we want. If we put

$$Q(t) = Q_0 \cos \omega t$$

for some constant Q_0 (you can check that it is the value of the charge at time $t = 0$), we will have

$$I = -\frac{dQ}{dt} = \omega Q_0 \sin \omega t.$$

Continuing with this

$$\frac{dI}{dt} = \omega^2 Q_0 \cos \omega t.$$

In other words

$$\frac{dI}{dt} = \omega^2 Q.$$

This is what we want if we set

$$\omega^2 = \frac{1}{LC}$$

or

$$\omega = \frac{1}{\sqrt{LC}}.$$

Thus the charge and the current oscillate periodically in time. The period is

$$T = \frac{2\pi}{\omega}$$

and the frequency is

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}.$$

At time $t = 0$ the charge is at a maximum value Q_0 . The capacitor discharges. If there was no inductance, the charge would drop to zero very quickly. But the inductance produces an e.m.f. that opposes the change in current. But this causes the capacitor to overshoot and get itself charged in the opposite polarity. It discharges again and overshoots itself so that it a charge of Q_0 again. Then the whole process repeats itself.

It is like having two political parties. Party L always opposes whatever change that Party Q is trying to make.

The country will go back and forth between extremes.

3 Mechanical Analogy

Imagine a mass attached to a spring. When the spring is not extended, the force on the mass is zero: it is in equilibrium. If the mass is displaced by x from this equilibrium point, there is a force $-kx$ acting on it. The sign of the force is in the direction that opposes the displacement. Thus

$$ma = -kx$$

where a is the acceleration. Recall that it is the rate of change of velocity, which is itself the rate of change of position:

$$v = \frac{dx}{dt}$$

$$a = \frac{dv}{dt}.$$

Thus we have

$$v = \frac{dx}{dt}$$

$$\frac{dv}{dt} = -\frac{k}{m}x$$

This is just like what we had above: the charge on the capacitor is like the displacement. The current is like the velocity (more precisely the negative of the velocity). The inductance is like the mass and the reciprocal of capacitance is like the spring constant k . This makes sense because inductance is a form of inertia, according to Lenz's law.

4 Energy in an Oscillator

The energy in a capacitor is $\frac{Q^2}{2C}$. It is a form of potential energy. The energy in an inductor is due to the current flowing through it. Thus it is a form of kinetic energy, due to the motion of electrons. It can also be thought of as the energy of the magnetic field inside the coils. This energy is $\frac{1}{2}LI^2$. The sum of these two is conserved in an ideal LC oscillator (with no resistance).

$$\frac{1}{2}LI^2 + \frac{Q^2}{2C} = \text{constant}.$$

5 Adding Resistance

But in the real world we are always losing energy to heat: the wires that carry the current will have resistance. The oscillations will die out eventually unless this energy is replenished from external sources.

If we include the voltage drop across a resistor,

$$-L\frac{dI}{dt} + \frac{Q}{C} - RI = 0.$$

In other words

$$L\frac{dI}{dt} + RI - \frac{Q}{C} = 0.$$

and still

$$I = -\frac{dQ}{dt}.$$

For small R , there should still be an oscillation, but each cycle, the maximum charge will be a little less than the one before. We can try a guess like

$$Q = Q_0 e^{-\gamma t} \cos \omega' t$$

which would capture this behavior. By putting it into the differential equation we will get

$$\gamma = \frac{R}{2L},$$

and

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}.$$

If the resistance is large ($R > 2\sqrt{\frac{L}{C}}$) there are no oscillations: the charge just decreases to zero exponentially.

6 Phase of Alternating Current

An alternating current is described its maximum current, its frequency and its phase

$$I(t) = I_0 \sin[\omega t + \phi].$$

Across the resistor the emf is proportional to the current. It reaches a maximum when the current is a maximum.

$$RI = RI_0 \sin[\omega t + \phi]$$

But across an inductor, the emf is

$$-L \frac{dI}{dt} = -LI_0 \omega \cos[\omega t + \phi] = (L\omega) I_0 \sin[\omega t + \phi - \frac{\pi}{2}].$$

Thus in addition to multiplying the current by $L\omega$, we must also shift the phase of the current to get the emf: when the current is a maximum, the emf of an inductance is actually zero.

A capacitance also shifts the phase but by the opposite amount. The emf across a capacitor is $\frac{Q}{C}$; and

$$I = -\frac{dQ}{dt}.$$

Thus

$$Q = \frac{1}{\omega} I_0 \cos[\omega t + \phi]$$

and

$$\frac{Q}{C} = \frac{1}{\omega C} I_0 \sin[\omega t + \phi - \frac{\pi}{2}].$$

A *phasor* (not the same as in Star Trek) is an electrical engineer's trick for representing these facts conveniently. A phasor is like a vector: it has a magnitude and a direction. A resistor is represented by a phasor of length R pointing along the horizontal axis. An inductance is a phasor of length $L\omega$ pointed along the vertical axis and a capacitance a phasor of length $\frac{1}{C\omega}$ vertically downward from the origin. Phasors added just like vectors in the plane. Thus an LCR circuit will have a phasor represented by the sum of the components

$$\left(R, \omega L - \frac{1}{\omega C} \right).$$

The magnitude of this phasor is called *impedance*

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}.$$

The direction is found by recalling that the resistance is the horizontal component of a phasor of length Z

$$\cos \theta = \frac{R}{Z}.$$

The impedance relates the rms voltage of an AC circuit to its rms current: there is something similar to Ohm's law

$$V_{rms} = Z I_{rms}.$$

7 Driven Oscillators

Because of resistance an oscillator will lose its current rapidly unless we give it some external emf. If this external is itself periodic we have a driven oscillator. It is similar to a person giving a swing a push at periodic intervals so that the swing keeps oscillating. The frequency of this external emf does not have to be the same as the natural frequency of the circuit.

If we apply an emf of angular frequency ω , the current in an LR circuit is given by

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{V_{rms}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}}.$$

Thus the current is a maximum when the frequency of the driving emf is equal to the natural frequency of the circuit:

$$\omega L = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{\sqrt{LC}}.$$

This is the phenomenon of resonance.